

Chapter 1: Review of Logic Design Fundamentals

1.1

A	B	C	$A \oplus B$	$B' \oplus C$	$(A \oplus B) \cdot C$	$A' \cdot (B' \oplus C)$	F
0	0	0	0	1	0	1	1
0	0	1	0	0	0	0	0
0	1	0	1	0	0	0	0
0	1	1	1	1	1	1	1
1	0	0	1	1	0	0	0
1	0	1	1	0	1	0	1
1	1	0	0	0	0	0	0
1	1	1	0	1	0	0	0

1.2

X	Y	B_{in}	Diff	B_{out}
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

Sum of Products: $Diff = XY'B_{in}' + X'Y'B_{in} + XYB_{in} + X'YB_{in}'$

$$B_{out} = X'B_{in} + X'Y + YB_{in}$$

Product of Sums: $Diff = (X + Y + B_{in})(X + Y' + B_{in}')(X' + Y + B_{in}')(X' + Y' + B_{in})$

$$B_{out} = (Y + B_{in})(X' + B_{in})(X' + Y)$$

1.3


		AB				
		00	01	11	10	
CD	00	0	X	S	0	S = G + H'
	01	X	E	E	X	
	11	1	0	F'	1	
	10	0	0	F'	0	

Set all map-entered variables to 0 to get $MS_0 = B'D$. Set E, F', and S to 1 one at a time and all 1's to X's to get $MS_1 = C'D(E)$, $MS_2 = ABC(F')$, $MS_3 = BC'D'(G + H')$


$$Z = B'D + C'DE + ABCF' + BC'D'G + BC'D'H'$$

- 1.4 (a) $F = A'D' + AC'D + BCD' + A'B'C'E + BD'E$
 (b) $Z = A'CD' + C'D + BC'E + B'DE + CD'F + A'C'G$
 (c) $H = A'CD + A'B'CE + BCDF'$
 (d) $G = C'E'F + DEF + AD'F'$


1.5

 

 A static 1-hazard occurs when $A = 0$, $D = 0$, and C changes. When C changes from 1 to 0; $A'C$ also goes from 1 to 0. The hazard occurs because C' hasn't become 1 yet since it has to go through the inverter; therefore, F goes to 0 momentarily before going to 1. Gate delays are assumed to be 10ns in the timing diagram below.




1.6

 


$$F = bc' + b'd' + a'cd'$$

- 3 hazards: $A=0, C=0, D=0, B$ changes
- $A=1, C=0, D=0, B$ changes
- $A=0, B=1, D=0, C$ changes

 To eliminate the hazards, add the term $c'd'$ (combining the four 1's in the top row) and replace $a'cd'$ with $a'd'$ (combining two 1's from the bottom left with two 1's from the top left.)



1.7 (a)

 

$$\begin{aligned}
 F &= ((ab)'.(a+c)'+(a'+d)')' \\
 &= ab + ((a+c)'+(a'+d)')' \\
 &= ab + (a+c)(a'+d) \\
 &= ab + aa' + ad + a'c + cd;
 \end{aligned}$$

Circle all these terms on the K-map; arc shows nearby 1's not in the same product term, indicating a 1 hazard.


1-hazard $bcd = 110$, a changing $1 \Rightarrow 0$ gates 1,5,3,4,5,
 $0 \Rightarrow 1$ gates 3,4,5,1,5

$$\begin{aligned}
 F &= ab + aa' + ad + a'c + cd \\
 &= ab + a(a' + d) + c(a' + d) \\
 &= ab + (a+c)(a' + d) \\
 &= (ab + a+c)(ab + a' + d) \quad \text{--see Table 1-1 for Boolean laws} \\
 &= (a+c)(a+a'+d)(a'+b+d) \quad \text{-- } a+ab=a; a'+d+ab=(a'+d+a)(a'+d+b)
 \end{aligned}$$


Circle all these terms of 0's in the K-map; arc shows 0's not in same term.

0-hazard $bcd = 000$, a changing $0 \Rightarrow 1$ gates 3,4,5,3,5
 $1 \Rightarrow 0$ gates 3,4,5,2,5

 - (b) We will design a 2-level sum of products circuit because a 2-level sum-of-products circuit has no 0-hazard as long as an input and its complement are not connected to the same AND gate. Avoid 1-hazard by adding product term bc . Use NAND gates as asked in the question.



1.8

 

(a) $Z = A'D' + (A + B)(B' + C')$
 $= A'D' + AB' + AC' + BB' + BC'$

Static 1 hazard (see the arcs between nearby 1's not in the same product term.)
 $ABCD = 0000$ to 1000
 $ABCD = 0010$ to 1010

$$Z = (A'D' + A + B)(A'D' + B' + C')$$

$$= (A' + A + B)(D' + A + B)(A' + B' + C')(D' + B' + C')$$

Static 0 hazard (see the arcs between nearby 0's not in the same term)
 $ABCD = 0111$ to 0011

(b) One can design a hazard-free sum of products circuit as in the previous question. Or, one can design a product of sums (POS) circuit with no hazards. A properly designed 2-level POS circuit has no 1-hazards. Static 0-hazards can be avoided by including loops for all 0's that are adjacent. 4 terms here including the arc:

$$Z = (A + B + D')(A' + B' + C')(D' + B' + C')(C' + D' + A)$$


$$= (D' + A + BC')(A' + B' + C')(D' + B' + C')$$

combining 1st and 4th terms


$$= (D' + A + BC')(B' + C' + A'D')$$

combining 2nd and 3rd terms


1.9 (a)

 

 
(b) From the characteristic equation for a J-K flip-flop ($Q^+ = JQ' + K'Q$):



1.10

 

1.11 (a)

 

Present State	Next State		Output	
	X = 0	1	X = 0	1
Reset	S0	S1	0	0
0	S1	S1	0	0
01	S2	S3	0	0
010	S3	S1	0	1
011	S4	S5	1	0
0101 or 0110	S5	S0	1	1

(b) Guidelines:

- I. (0,1,3),(0,4,5)
- II. (0,1),(1,2),(3,4),(1,5),(0,5)
- III. (0,1,2,3),(4,5),(3,5)

For state assignment:

$$S_0 = 000 \quad S_1 = 001 \quad S_2 = 010 \quad S_3 = 011 \quad S_4 = 100 \quad S_5 = 101$$


Equations for NAND gate network:

$$\begin{aligned} J_1 &= XQ_2 & K_1 &= X + Q_3 \\ J_2 &= XQ_1'Q_3 & K_2 &= X + Q_3 \\ J_3 &= X' & K_3 &= XQ_2' + Q_1 \\ Z &= XQ_2Q_3 + X'Q_1 + Q_1Q_3 \end{aligned}$$

For NOR gate network, use product of sums form:

$$\begin{aligned} K_3 &= (X + Q_1)(Q_2') \\ Z &= (Q_1 + Q_2)(X' + Q_3)(X + Q_2') \end{aligned}$$

1.12 (a)

 

Present State	Next State		Output	
	X = 0	1	X = 0	1
S0	S1	S3	00	00
S1	S1	S2	00	00
S2	S4	S3	10	00
S3	S4	S3	00	00
S4	S5	S2	01	00
S5	S5	S6	00	00
S6	S7	S6	00	00
S7	S5	S6	01	00

(b) Guidelines:

- I. (0,1),(2,3),(4,5,7),(0,2,3),(1,4),(5,6,7)
- II. (1,3),(1,2),2x(3,4),(2,5),2x(5,6),(6,7)
- III. (0,1,3,5,6),(4,7)

For state assignment:

$$\begin{aligned} S_0 &= 000 & S_1 &= 100 & S_2 &= 001 & S_3 &= 101 \\ S_4 &= 111 & S_5 &= 011 & S_6 &= 010 & S_7 &= 110 \end{aligned}$$

Equations for NAND gate network:

$$\begin{aligned} J_1 &= Q_2' + X'Q_3' & K_1 &= XQ_3' + Q_2 \\ J_2 &= X'Q_3 & K_2 &= XQ_1Q_3 \end{aligned}$$

$$J_3 = XQ_2' + X'Q_1Q_2 \quad K_3 = XQ_1'Q_2$$

$$Z_1 = X'Q_1'Q_2'Q_3$$


$$Z_2 = X'Q_1Q_2$$

For NOR gate network, use product of sums form:

$$J_1 = (Q_2' + Q_3')(X' + Q_2') \quad K_1 = (X + Q_2)(Q_2 + Q_3')$$

$$J_3 = (X + Q_2)(X' + Q_2')(X + Q_1)$$

1.13 (a)

 

Present State	Next State		Output	
	X = 0	1	X = 0	1
S0	S1	S1	00	10
S1	S2	S4	10	00
S2	S3	S3	00	10
S3	S0	S0	00	10
S4	S3	S5	10	00
S5	S0	S0	10	01

(b) Guidelines:

- I. (2,4), 2x(3,5)
- II. (2,4), (3,5)
- III. (0,2,3), (1,4,5)

For state assignment:

$$S0 = 000 \quad S1 = 010 \quad S2 = 001 \quad S3 = 101 \quad S4 = 011 \quad S5 = 111$$

Equations for NAND gate network:

$$D_1 = Q_1'Q_3$$

$$D_2 = Q_2'Q_3' + XQ_1'Q_2$$

$$D_3 = Q_1'Q_3 + Q_2Q_3' \text{ or } Q_1'Q_3 + Q_1'Q_2$$

$$S = XQ_2' + X'Q_2$$

$$V = XQ_1Q_2$$


For NOR gate network, use product of sums form:

$$S = (X + Q_2)(X' + Q_2')$$

$$D_2 = Q_1'(Q_2 + Q_3')(X + Q_2')$$

$$D_3 = Q_1'(Q_2 + Q_3)$$

1.14 (a)

 

Present State	Next State		Output	
	X = 0	1	X = 0	1
S0	S1	S1	00	10
S1	S2	S3	10	00
S2	S4	S5	10	00
S3	S5	S5	00	10
S4	S0	S0	11	00
S5	S0	S0	00	10

(b) Guidelines:

- I. (4,5),(2,3)
- II. (2,3),(4,5)
- III. (0,3,5),(1,2,4)

For state assignment:

$$S0 = 000 \quad S1 = 100 \quad S2 = 101 \quad S3 = 001 \quad S4 = 111 \quad S5 = 011$$


Equations for NAND gate network:

$$\begin{aligned} J_1 &= Q_3' & K_1 &= X + Q_2 \\ J_2 &= Q_3 & K_2 &= 1 \\ J_3 &= Q_1 & K_3 &= Q_2 \\ D &= X'Q_1 + XQ_1'Q_3 \\ B &= X'Q_1Q_2 \end{aligned}$$

For NOR gate network, use product of sums form:

$$D = (X' + Q_1')(X + Q_1)(Q_1 + Q_3)$$

1.15

 

Present State	Next State		Output
	X = 0	1	
S0	S0	S1	0
S1	S0	S2	0
S2	S0	S3	0
S3	S4	S3	1
S4	S5	S3	1
S5	S0	S3	1

1.16

Present State ($Q_2Q_1Q_0$)	Next State ($Q_2^+Q_1^+Q_0^+$)
000	001
001	010
010	011
011	100
100	101
101	000


$$\begin{aligned}
 J_2 &= Q_1Q_0 & K_2 &= Q_0 \\
 J_1 &= Q_2'Q_0 & K_1 &= Q_0 \\
 J_0 &= 1 & K_0 &= 1
 \end{aligned}$$

1.17

Present State ($Q_2Q_1Q_0$)	Next State ($Q_2^+Q_1^+Q_0^+$)
001	010
010	011
011	100
100	101
101	110
110	001


$$\begin{aligned}
 D_2 &= Q_1Q_0 + Q_2Q_1' \\
 D_1 &= Q_2'Q_0' + Q_1'Q_0 \\
 D_0 &= Q_0'
 \end{aligned}$$

1.18

 

present state	next state		output	
	X = 0	X = 1	X = 0	X = 1
A	B	G	0	1
B	A	D	1	1
C	F	G	0	1
D	H G	A	0	0
E	G	C	0	0
F	C	D	1	1
G	G	E D	0	0
H	G	D	0	0

1.19 (a)

 

Z should be read just before the rising edge of the clock.

(b) Worst case $t_{xor} + t_p + t_{su} \leq t_{clk}$
 $20\text{ns} + 10\text{ns} + 5\text{ns} \leq t_{clk}$
 $t_{clk} \geq 35\text{ns}$
 Clock Rate = 28.6 MHz

However, the input X changes at the same time as the falling edge of the clock. Data is clocked into D flip-flop at the rising edge of the clock. Therefore, the time t between the falling edge and the rising edge of the clock should satisfy the gate delay of XOR and also the setup time

$$t_{clk} \geq 20\text{ns} + 5\text{ns}$$

$$t_{clk} \geq 50\text{ns}$$

Clock Rate = 20 MHz

For proper synchronous operation, both condition 1 and condition 2 should be satisfied.

$$t_{\text{clk}} \geq 50\text{ns is the limiting factor}$$

Therefore, Clock Rate = 20 MHz

- (c) Q1 should remain unchanged for 2ns (t_h) after D2 is clocked


Q1 will be constant for at least 5ns (t_{pmin}) after the rising clock edge

$$t_{\text{constnat}} = t_h + \text{delay} = 2\text{ns} + \text{delay}$$

$$t_{\text{constnat}} = t_{\text{pmin}} = 5\text{ns}$$


$$\text{delay} = t_{\text{pmin}} - t_h = 3\text{ ns}$$

1.20 (a)

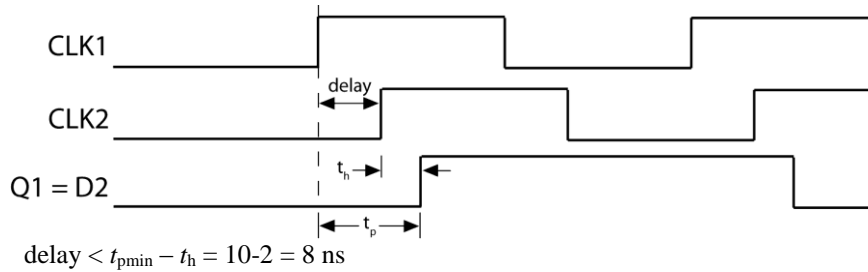

- (b) $t_{\text{clk}} \geq t_{\text{pmin}} + t_{\text{su}} = 15 + 4 = 19\text{ ns}$. (worst case occurs when delay = 0)

1.21 (a)

 


- (b) By definition of set up and hold time, D should be constant 10 ns (t_{su}) before, and 5 ns (t_h) after the clock edge.

- (c) External inputs should not change 18 ns before, and 1 ns after clock edge.

$$t_y = t_{\text{cmax}} + t_{\text{su}} = (4 + 4) + 10 = 18$$


$$t_x = t_h - t_{\text{cmin}} = 5 - (2 + 2) = 1$$

1.22 (a)

 

- (b) Setup time = 20 ns - 10 ns = 10 ns (due to change in X)
 Hold time = $t_{pmin} + t_{pla} = 5 \text{ ns} + 5 \text{ ns} = 10 \text{ ns}$ (due to change in Q)

1.23

 

- 1.24 (a) $t_{clk} \geq t_{su} + t_{pmax} + t_{cmax}$
 $t_{clk} \geq 5 + 12 + 4 = 21 \text{ ns}$
 $t_{clkmin} = 21 \text{ ns}$

- (b) $t_x = t_h - t_{cmin} = 3 - 1 = 2 \text{ ns}$. X can change as early as 2 ns after the clock edge.

- 1.25 (a) $16 \text{ ns} + 24 \text{ ns} + 8 \text{ ns} = \underline{48 \text{ ns}}$. (to satisfy setup time) (hold time is not a problem because it takes at least $12 + 2 = 14 \text{ ns}$ from rising clock edge until D changes)

- (b) earliest time: to satisfy hold time, $t_h - t_{cmin} = 4 \text{ ns} - 2 \text{ ns} = \underline{2 \text{ ns}}$
 latest time: to satisfy setup time, $8 \text{ ns} + 16 \text{ ns} = 24 \text{ ns}$ before rising clock edge. $48 \text{ ns clock} - 24 \text{ ns} = \underline{24 \text{ ns}}$ after rising clock edge

- 1.26 (a) The maximum delay path of this circuit starts at flip-flop 2 and ends at flip-flop 1:

$$f_{max} = 1/(t_{pmax} + t_{cmax} + t_{su}) = 1/(24\text{ns} + 16\text{ns} + 8\text{ns}) \approx 20.83 \text{ MHz}$$

- (b) $f_{max} = 1/(t_{pmax} + t_{cmax} - t_{skew} + t_{su}) = 1/(24\text{ns} + 16\text{ns} - 5\text{ns} + 8\text{ns}) \approx 23.26 \text{ MHz}$

- (c) $f_{max} = 1/(t_{pmax} + t_{cmax} + t_{skew} + t_{su}) = 1/(24\text{ns} + 16\text{ns} + 5\text{ns} + 8\text{ns}) \approx 18.87 \text{ MHz}$

(d) $t_y \geq t_h - t_{cxmin} = 4ns - 2ns = 2ns$
 $t_x \geq t_{cxmax} + t_{su} = 16ns + 8ns = 24ns$

X can change 2 ns after and 24 ns before the rising clock edge.

(e) From part (d), X can change 2 ns after and 24 ns before the rising clock edge of flip-flop 1. However, because the rising clock edge of flip-flop 2 is delayed 5 ns from the rising edge of flip-flop 1, then X can change -3 ns after and 29 ns before the rising clock edge of flip-flop 2. In other words, X cannot change between 29 and 3 ns before the rising clock edge of flip-flop 2.

(f) From part (d), X can change 2 ns after and 24 ns before the rising clock edge of flip-flop 1. However, because the rising clock edge of flip-flop 2 is advanced 5 ns from the rising edge of flip-flop 1, then X can change 7 ns after and 19 ns before the rising clock edge of flip-flop 2.

1.27 (a) Consider following delays:

input to first FF: $t_{su} = 20ns$
left FF to middle FF: $t_{pmax} + t_{c1max} + t_{skew1} + t_{su} = 10ns + 7ns + 0ns + 20ns = 37ns$
middle FF to right FF: $t_{pmax} + t_{c2max} - t_{skew2} + t_{su} = 10ns + 11ns - 0ns + 20ns = 41ns$
right FF to output: $t_{pmax} = 10ns$

The maximum of these is 41 ns. Therefore, the minimum clock period should be 41 ns.

(b) $t_{clk} \geq t_{pmax} + t_{c1max} + t_{su}$
 $41ns \geq 10ns + 4ns + 20 = 34ns$

There is no setup time violation for the middle flip-flop. The setup time margin is $41 - 34 = 7$ ns.

(c) $t_{pmin} + t_{c1min} \geq t_h$
 $5ns + 1ns < 10ns$

There is a hold time violation for the middle flip-flop.

(d) For negative clock skew:
 $t_{skewmin} = t_h - t_{pmin} - t_{cmin} = 10ns - 5ns - 1ns = 4ns$

To fix the hold time violation for the middle flip-flop, make $t_{skew1min} = 4$ ns and keep $t_{skew2min} = 0$ ns.

(e) The new worst-case delay of the path from the left flip-flop to the middle flip-flop is:
 $t_{pmax} + t_{c1max} + t_{skew1} + t_{su} = 10ns + 4ns + 4ns + 20ns = 38ns$

However, this delay is still less than the 41 ns delay of the path from the middle flip-flop to the right flip-flop. Therefore, t_{clkmin} is still 41 ns.

- 1.28 (a) Consider following delays:
input to first FF: $t_{su} = 10ns$
left FF to middle FF: $t_{pmax} + t_{c1max} + t_{skew1} + t_{su} = 20ns + 7ns + 0ns + 10ns = 37ns$
middle FF to right FF: $t_{pmax} + t_{c2max} - t_{skew2} + t_{su} = 20ns + 11ns - 3ns + 10ns = 38ns$
right FF to output: $t_{pmax} = 20ns$

The maximum of these is 38 ns. Therefore, the minimum clock period should be 38 ns.


- (b) $t_{clk} \geq t_{pmax} + t_{c1max} + t_{skew1} + t_{su}$
 $38 ns \geq 20ns + 4ns + 0ns + 10ns = 34 ns$
There is no setup time violation for the middle flip-flop. The setup time margin is $38 - 34 = 4 ns$.

- (c) $t_{pmin} + t_{c1min} \geq t_h - t_{skew1}$
 $12ns + 1ns \geq 2ns - 0ns$
There is no hold time violation for the middle flip-flop. The hold time margin is $13 - 2 = 11 ns$.

- (d) Because both setup and hold time requirements are met for the middle flip-flop, the clock skew delays in place are valid.


- (e) The worst-delay path is still from the middle flip-flop to the right flip-flop. Therefore, t_{clkmin} is still 38 ns.

1.29

 


- 1.30 (a) No


- (b)

 


(c)

 

1.31 (a)

 

(b)

 

The clock input to the NAND gate in (a) is inverted. After the rising edge of the clock, this input to the NAND gate is a '0', so CK1 will remain a constant '1', regardless of any changes that may occur in the EN input of the gate due to transients.

1.32 $Eni = 0$ $Ena = 0$ $Enb = 0$ $Enc = 1$ $Lda = 1$ $Ldb = 1$ $Ldc = 0$

