

**Gregory L. Moss**

**Lab Solutions Manual**

**for**

**Lab Manual: A Design Approach**

to accompany

**DIGITAL SYSTEMS:**

**PRINCIPLES AND APPLICATIONS**

Eleventh Edition

By Ronald J. Tocci, Neal S. Widmer, & Gregory L. Moss

**Prentice Hall**

Boston Columbus Indianapolis New York San Francisco Upper Saddle River  
Amsterdam Cape Town Dubai London Madrid Milan Munich Paris Montreal Toronto  
Delhi Mexico City Sao Paulo Sydney Hong Kong Seoul Singapore Taipei Tokyo



**This work is protected by United States copyright laws and is provided solely for the use of instructors in teaching their courses and assessing student learning. Dissemination or sale of any part of this work (including on the World Wide Web) will destroy the integrity of the work and is not permitted. The work and materials from it should never be made available to students except by instructors using the accompanying text in their classes. All recipients of this work are expected to abide by these restrictions and to honor the intended pedagogical purposes and the needs of other instructors who rely on these materials.**

---

**Copyright ©2011 Pearson Education, Inc., publishing as Prentice Hall, 1 Lake Street, Upper Saddle River, New Jersey 07458.** All rights reserved. Manufactured in the United States of America. This publication is protected by Copyright, and permission should be obtained from the publisher prior to any prohibited reproduction, storage in a retrieval system, or transmission in any form or by any means, electronic, mechanical, photocopying, recording, or likewise. To obtain permission(s) to use material from this work, please submit a written request to Pearson Education, Inc., Permissions Department, One Lake Street, Upper Saddle River, New Jersey.

Many of the designations by manufacturers and seller to distinguish their products are claimed as trademarks. Where those designations appear in this book, and the publisher was aware of a trademark claim, the designations have been printed in initial caps or all caps.

10 9 8 7 6 5 4 3 2 1

**PEARSON**


ISBN-13: 978-0-13-512382-9  
ISBN-10: 0-13-512382-8

# **CONTENTS**

Unit 1	Introduction to the DE0/DE1/DE2 Development & Education Boards	1
Unit 2	Testing Combinational Logic Circuits using DE0/DE1/DE2 Boards	3
Unit 3	Schematic Capture and Analysis of Combinational Logic Circuits	6
Unit 4	Design and Simulation of Combinational Circuits	8
Unit 5	Creating Hierarchical Logic Circuits	16
Unit 6A	Combinational Circuit Design with AHDL	22
Unit 6V	Combinational Circuit Design with VHDL	28
Unit 7	Testing Flip-Flops and Sequential Circuit Applications	36
Unit 8	Timing and Waveshaping Circuits	41
Unit 9	Arithmetic Circuit Applications	43
Unit 10	Analyzing and Testing Synchronous Counters	50
Unit 11	Creating and Testing Counter Functions	51
Unit 12	Applications Using Maxplus2 Counters	58
Unit 13	Applications Using LPM_Counter Megafunctions	63
Unit 14A	Counter Designs Using AHDL	71
Unit 14V	Counter Designs Using VHDL	84
Unit 15	Shift Register Applications	99
Unit 16	Synchronous Counter Design with Flip-flops	112
Unit 17	Decoder and Display Applications	119
Unit 18	Encoder Applications	133
Unit 19	Multiplexer Applications	141
Unit 20	Demultiplexer Applications	147
Unit 21	Magnitude Comparator Applications	153
Unit 22	Digital/Analog and Analog/Digital Conversion	157
Unit 23	Memory Systems	165
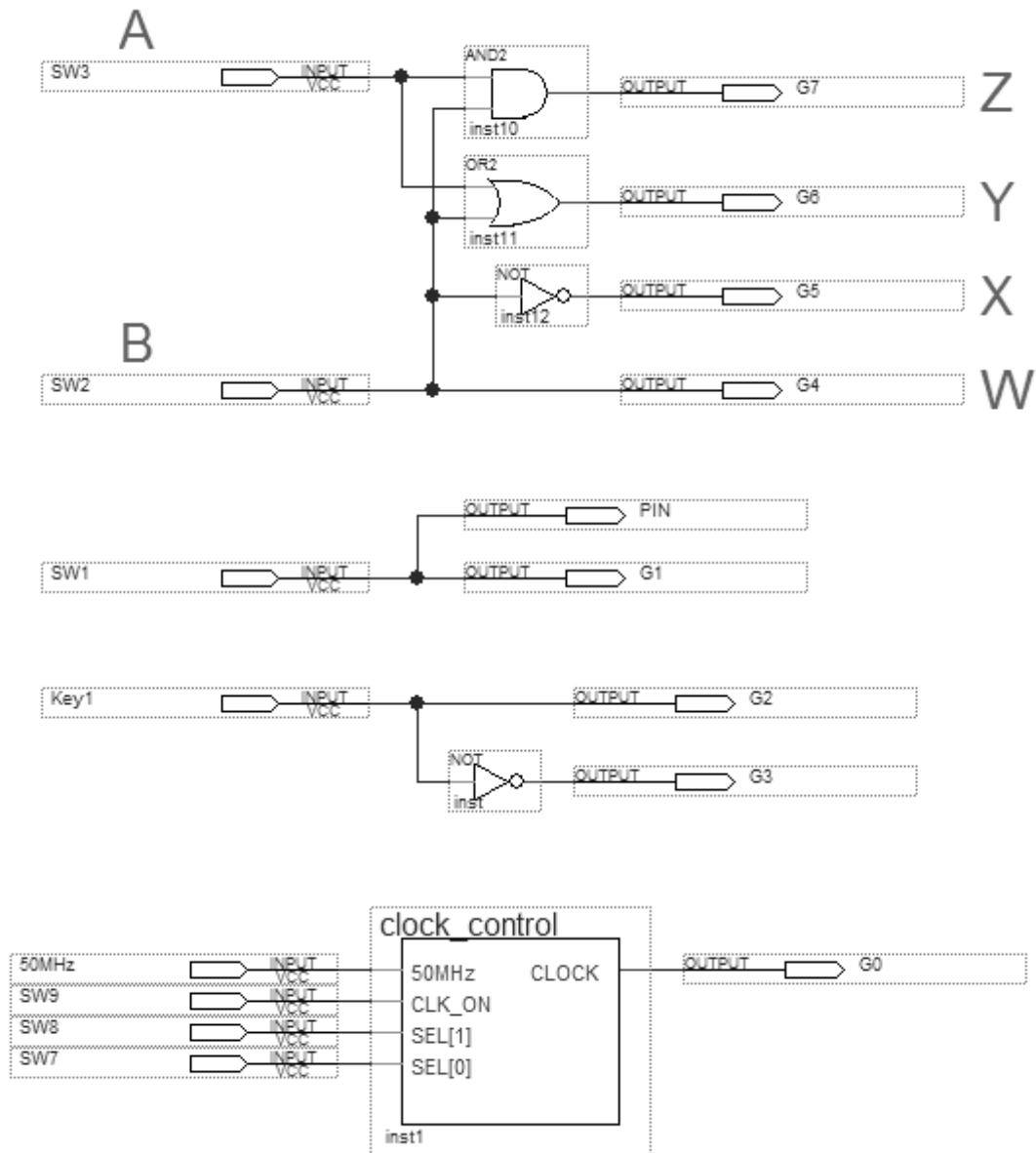
## Unit 1 Introduction to the DE0, DE1, or DE2 Development & Education Board

Project: Intro2DE0, Intro2DE1, or Intro2DE2



### 1.3 Logic Switches

Board	DE0	DE1	DE2
# switches	10	10	18

Logic Switch SW1	LEDG1 (on/off)	Logic level (high/low)	Voltage at connector pin
Down	Off	Low	~0 V
Up	On	High	~3.3 V

#### 1.4 LEDs

LED label	Color	DE0	DE1	DE2
LEDR	Red	0	10	18
LEDG	Green	10	8	9

#### 1.5 Pushbuttons → Normally High

Board	DE0	DE1	DE2
Pushbutton	3	4	4

Pushbutton #1	LEDG2 (on/off)	LEDG3 (on/off)
Normal	On	Off
Pressed	Off	On

#### 1.6 Clock

CLK_ON (SW9)	1	1	1	1	0
SEL[1..0] (SW8, SW7)	00	01	10	11	XX
freq <sub>G0</sub>	0.5 Hz	5 Hz	25 Hz	50 Hz	0 Hz

#### 1.7 Simple logic circuits

A (SW3)	B (SW2)	W (LEDG4)	X (LEDG5)	Y (LEDG6)	Z (LEDG7)
0	0	0	1	0	0
0	1	1	0	1	0
1	0	0	1	1	0
1	1	1	0	1	1

$$W = B$$



$$X = \overline{B}$$


$$Y = A + B$$

$$Z = A \cdot B$$

## Unit 2 Testing Combinational Logic Circuits Using DE0, DE1, or DE2 Boards

Project: Lab2DE0, Lab2DE1, or Lab2DE2

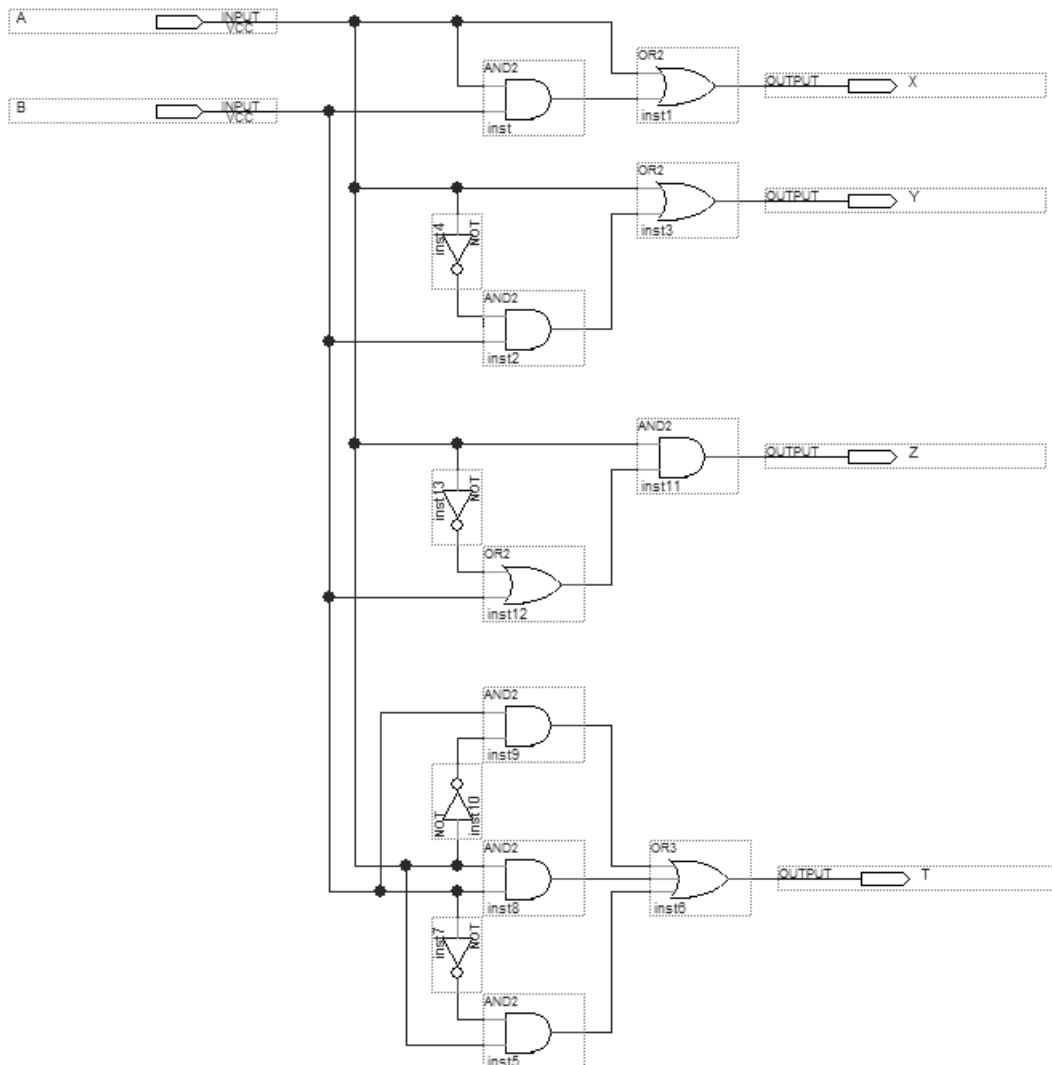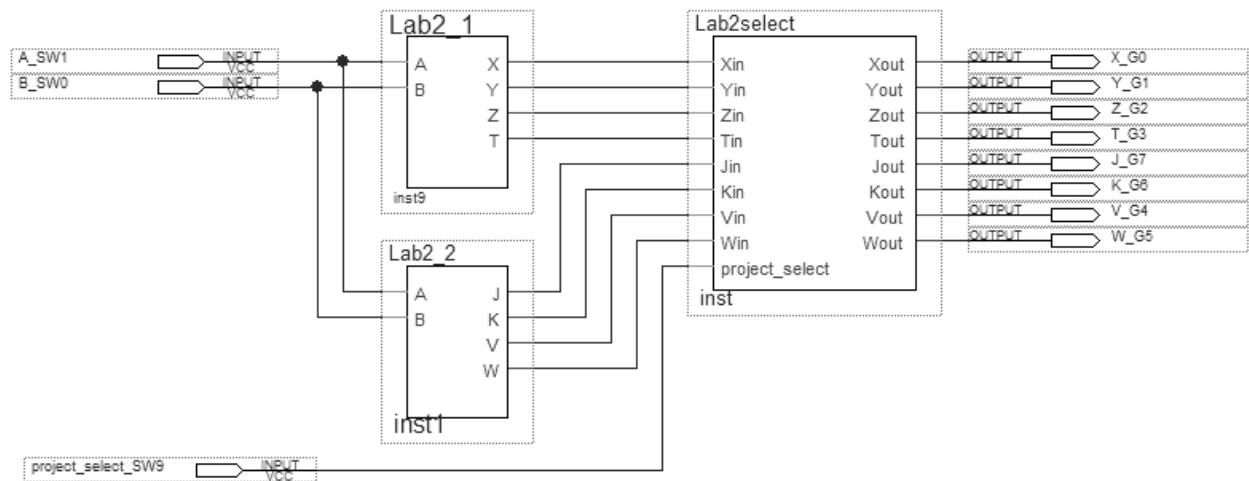

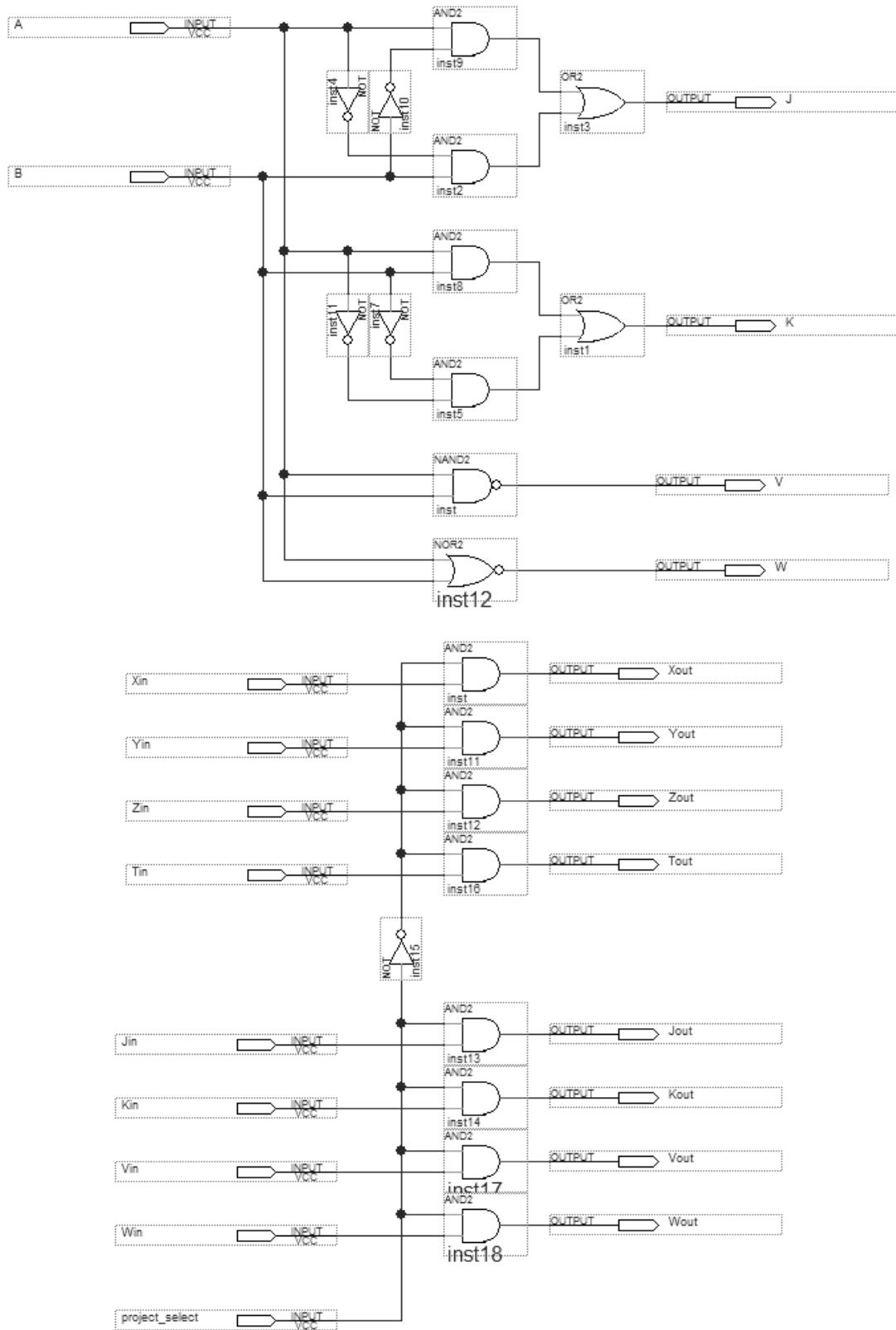

## 2.1 Simple circuits

$$X = A + A B = A$$

$$Y = A + \bar{A} B = A + B$$

$$Z = A (\bar{A} + B) = A B$$

$$T = \bar{A} B + A B + A \bar{B} = A + B$$

A	B	T	Z	Y	X	J	K	W	V
0	0	0	0	0	0	0	1	1	1
0	1	1	0	1	0	1	0	0	1
1	0	1	0	1	1	1	0	0	1
1	1	1	1	1	1	0	1	0	0

## 2.2 More circuit functions

$$V = \overline{A B}$$

$$W = \overline{A + B}$$

$$J = A \bar{B} + \bar{A} B = A \oplus B$$

$$K = A B + \bar{A} \bar{B} = \overline{A \oplus B}$$



### Unit 3 Schematic Capture & Analysis of Combinational Logic Circuits

3.1 Example 3-1 (see Lab Manual Example 3-1 & Quartus Tutorial 1 – Schematic)

3.2 Equivalent circuits

(a)  $V = W?$       true

$$V = A (B + C)$$

$$W = A C + A B$$

(b)  $X = Y?$       true

$$X = \bar{A} \bar{B} + A B + A C$$

$$Y = \bar{A} \bar{B} + A B + \bar{B} C$$

A	B	C	V	W	X	Y
0	0	0	0	0	1	1
0	0	1	0	0	1	1
0	1	0	0	0	0	0
0	1	1	0	0	0	0
1	0	0	0	0	0	0
1	0	1	1	1	1	1
1	1	0	1	1	1	1
1	1	1	1	1	1	1

3.3 DeMorgan's theorem

(a)  $p1 = p2 = p3?$       true


$$p1 = \bar{a} \bar{b} \quad p2 = \bar{a} \bar{b} \quad p3 = \overline{a + b}$$

(b)  $q1 = q2 = q3?$       true

$$q1 = \bar{a} + \bar{b} \quad q2 = \bar{a} + \bar{b} \quad q3 = \overline{a b}$$


a	b	p	q
0	0	1	1
0	1	0	1
1	0	0	1
1	1	0	0

3.4 2-bit adder

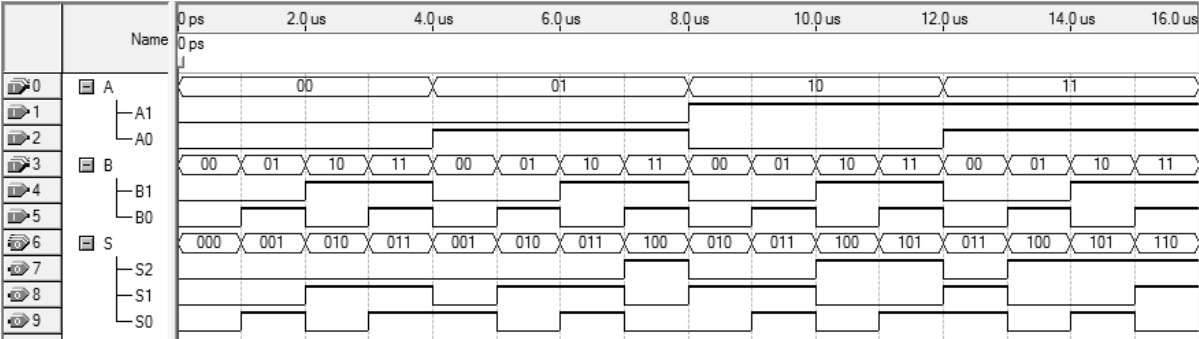

## Unit 4 Design and Simulation of Combinational Circuits

 
### 4.1 Majority vote (see Lab Manual Example 4-1 & Quartus Tutorial 2 – Simulation)



### 4.2 Two-input multiplexer

S	A	B	Y
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

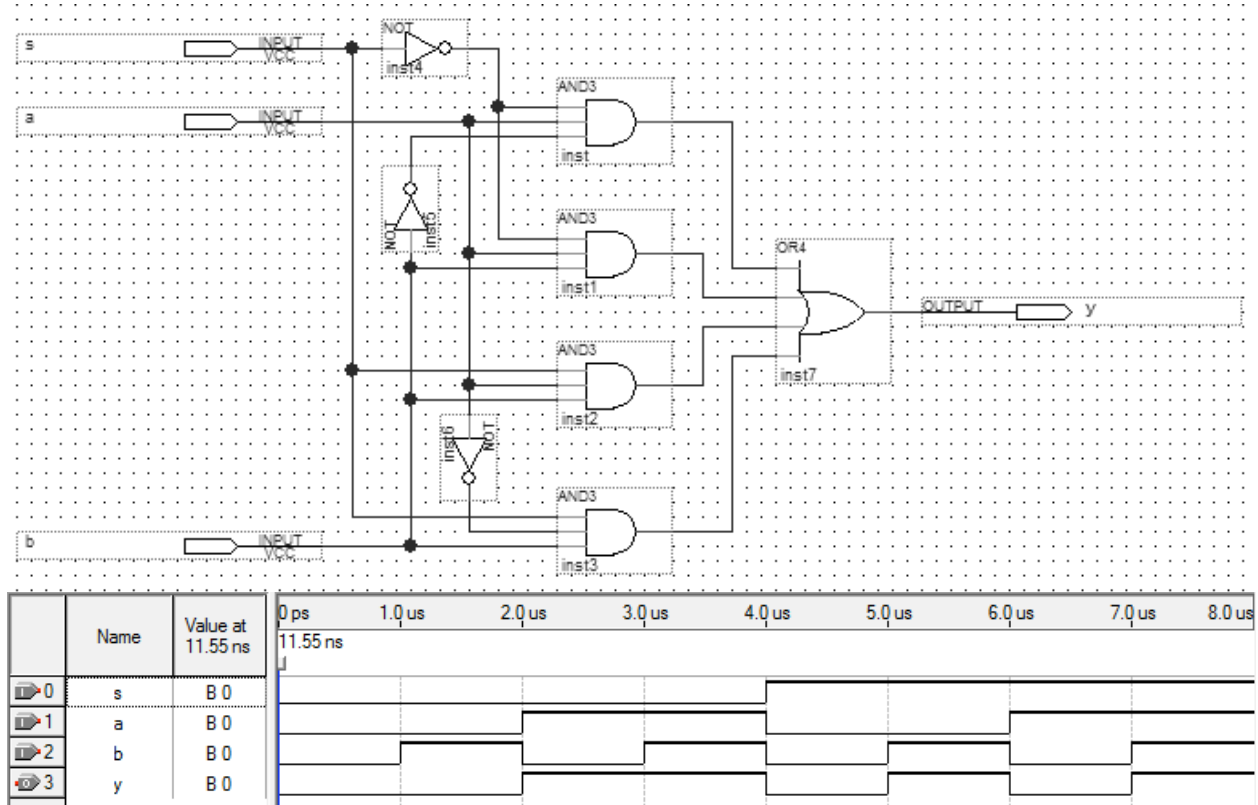
$$Y = \bar{S} A \bar{B} + \bar{S} A B + S \bar{A} B + S A B$$




### 4.3 Non-BCD input

A	B	C	D	GT9
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1
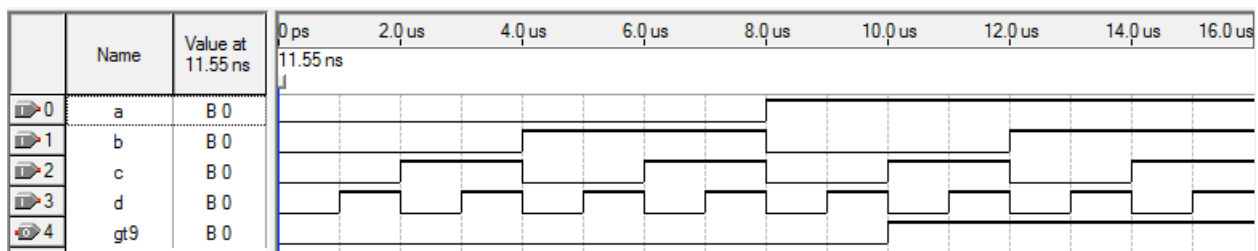
$$\begin{aligned}
 GT9 = & A \bar{B} C \bar{D} + A \bar{B} C D + A B \bar{C} \bar{D} + A B \bar{C} D \\
 & + A B C \bar{D} + A B C D
 \end{aligned}$$





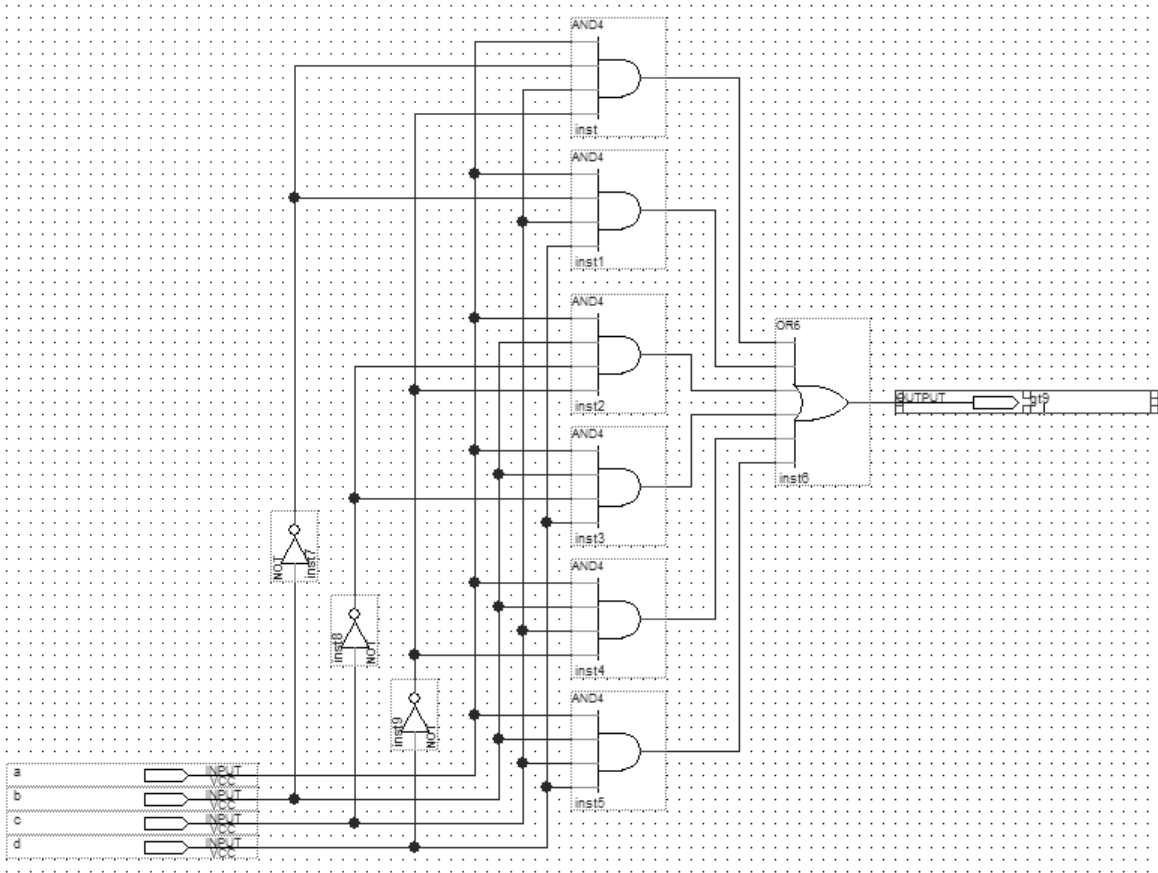

#### 4.4 Two-bit comparator

A1	A0	B1	B0	EQ
0	0	0	0	1
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	1
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1
 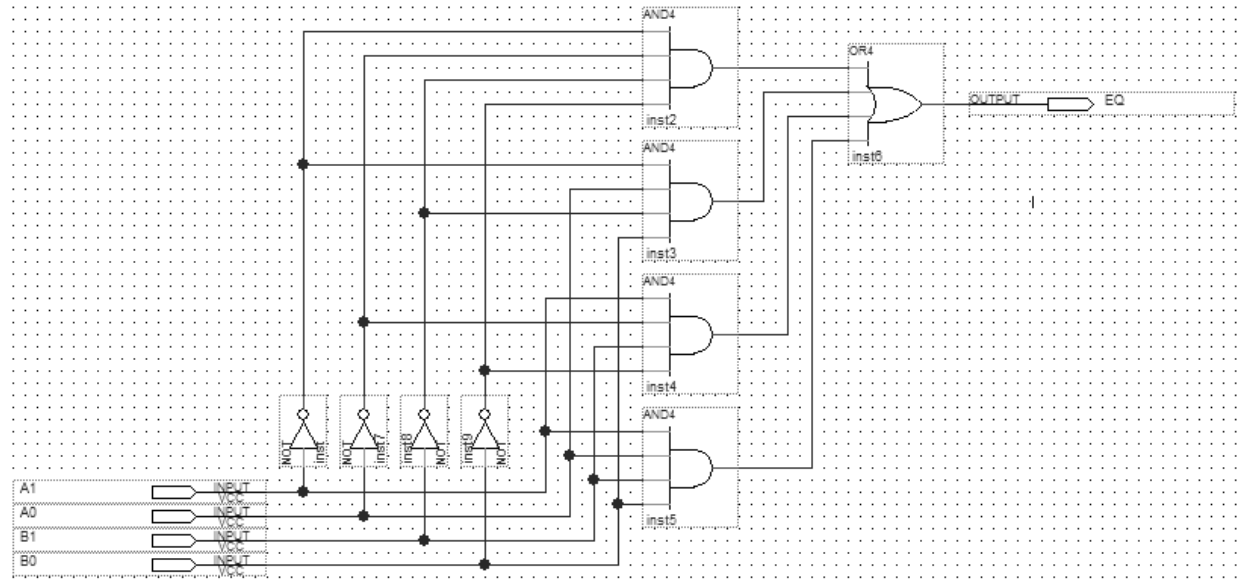
$$EQ = \overline{A1} \overline{A0} \overline{B1} \overline{B0} + \overline{A1} A0 \overline{B1} B0 + A1 \overline{A0} B1 \overline{B0} + A1 A0 B1 B0$$





#### 4.5 Binary number detector

$$Y0 = G \bar{B} \bar{A}$$

$$Y1 = G \bar{B} A$$

$$Y2 = G B \bar{A}$$


$$Y3 = G B A$$

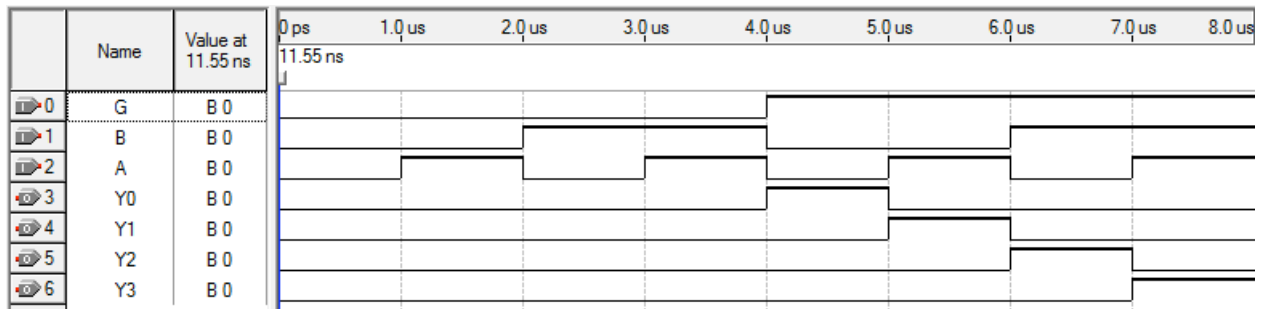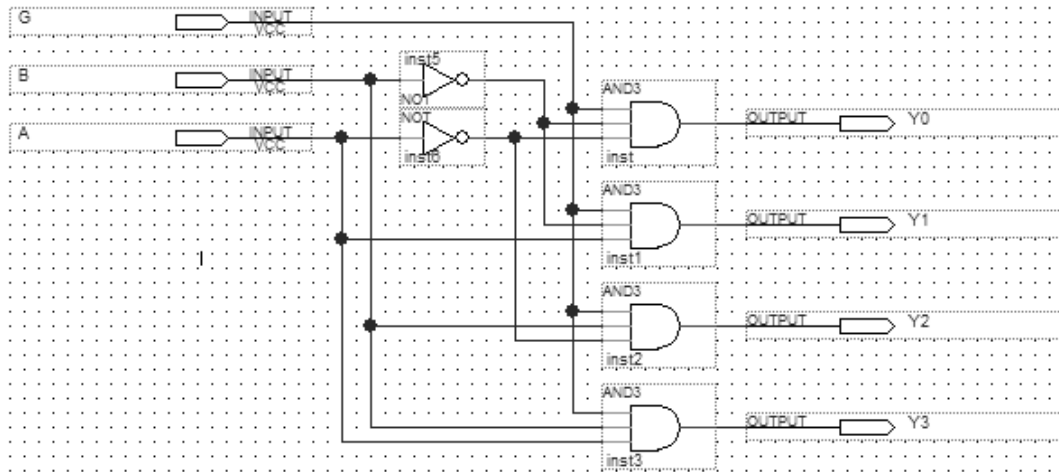


4.6 Alarm circuit

T	P	F	L	A
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	1
1	0	0	0	0
1	0	0	1	1
1	0	1	0	0
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1
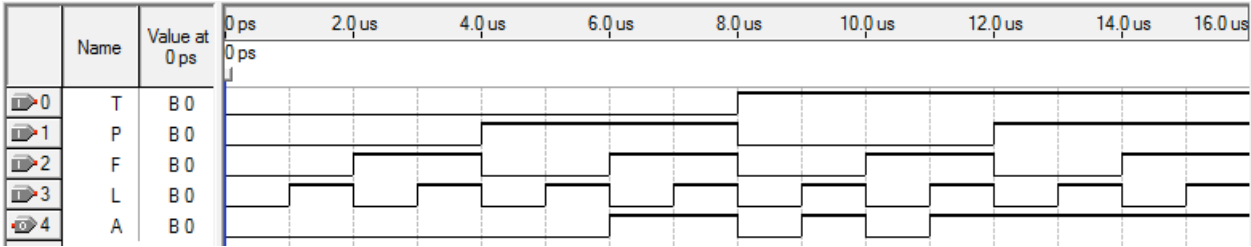
$$A = \overline{T} P F \overline{L} + \overline{T} P F L + T \overline{P} \overline{F} L + T \overline{P} F L$$
$$+ T P \overline{F} \overline{L} + T P \overline{F} L + T P F \overline{L} + T P F L$$







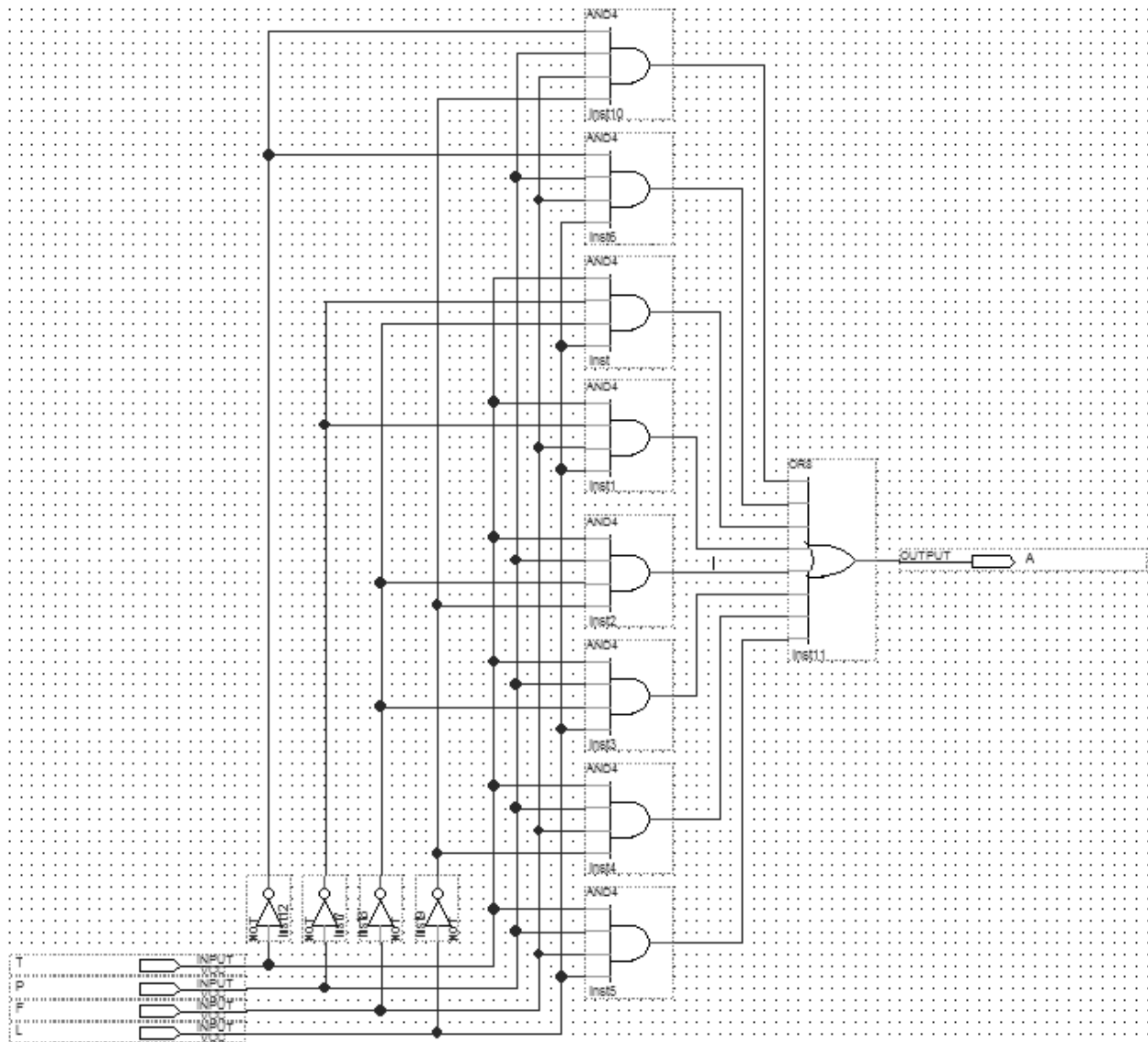

## 4.7 Elevator control



A	B	C	D	F
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1
 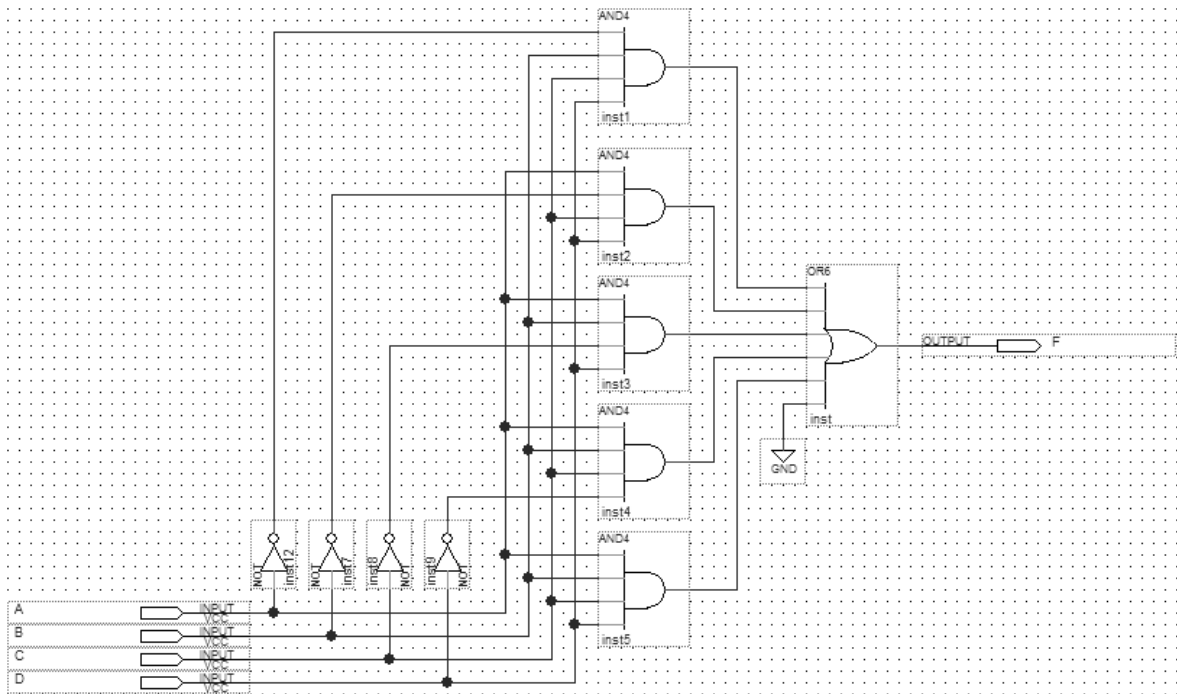
$$F = \bar{A} B C D + A \bar{B} C D + A B \bar{C} D + A B C \bar{D} + A B C D$$






## Unit 5 Creating Hierarchical Logic Circuits

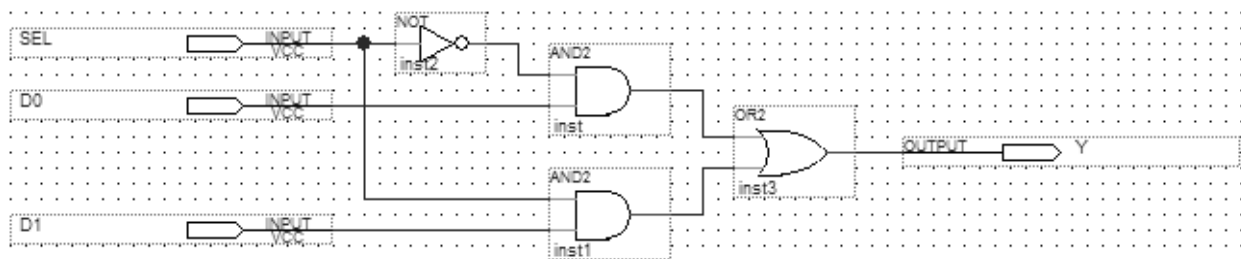
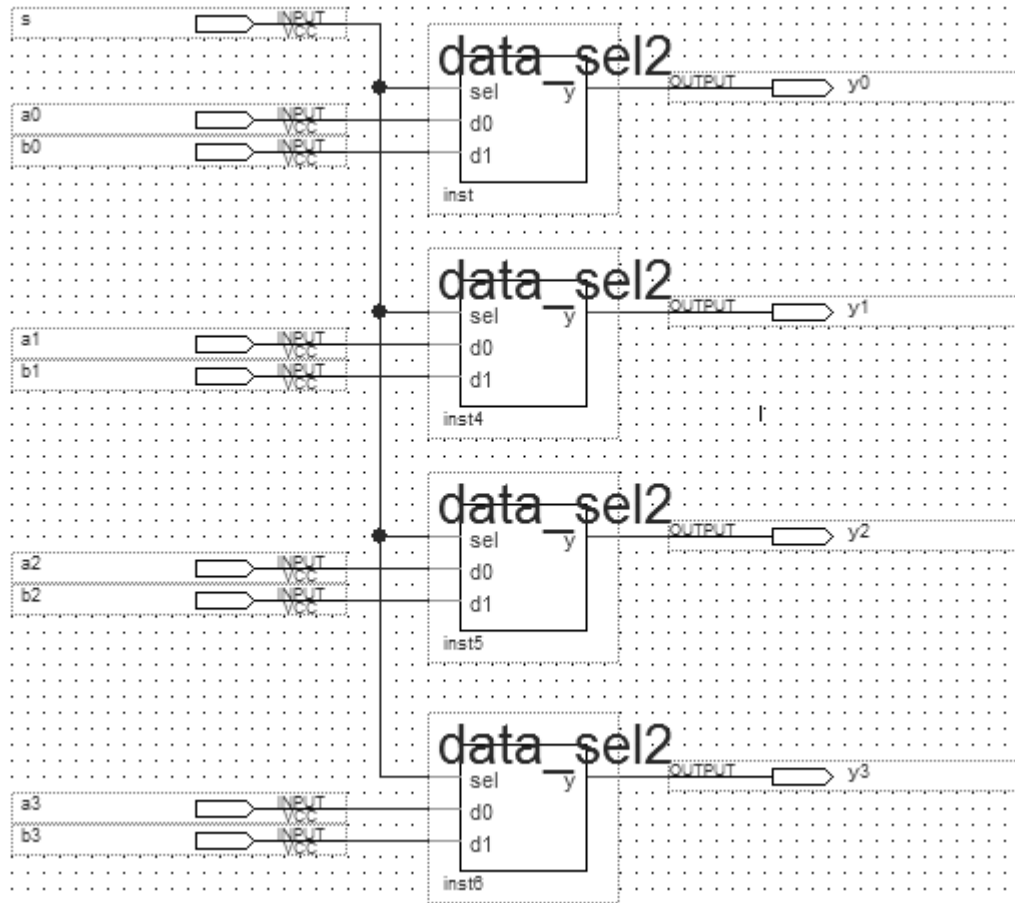
- 5.1 1-out-of-4 data selector (see Lab Manual Example 5-1 & Quartus Tutorial 3 – Hierarchical)
- 5.2 2-channel, 4-bit multiplexer





### 5.3 Multiplexer & decoder

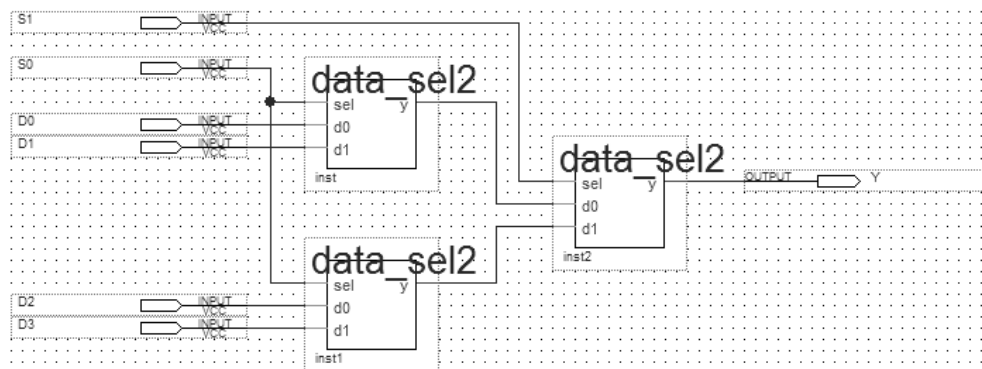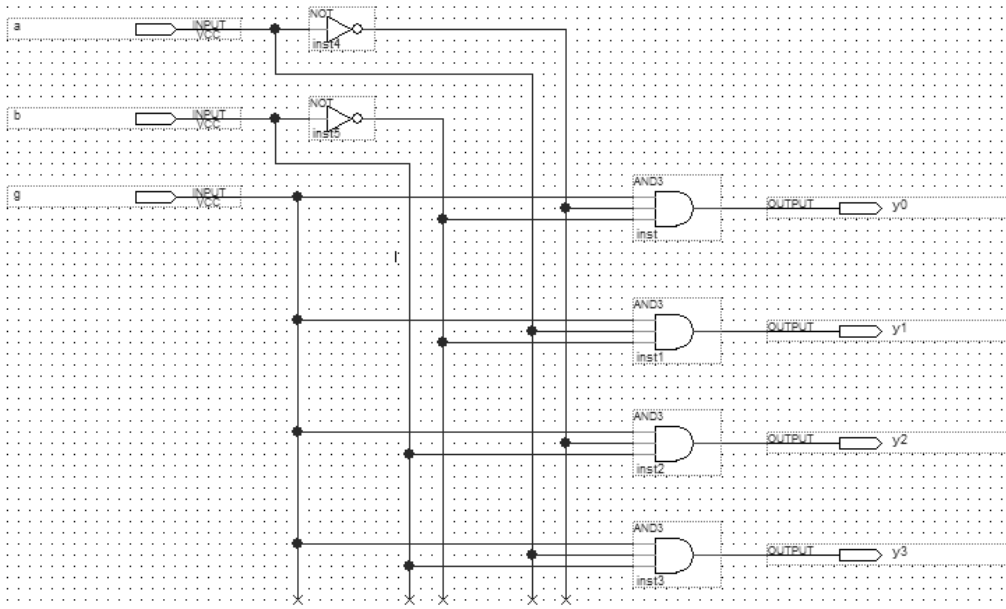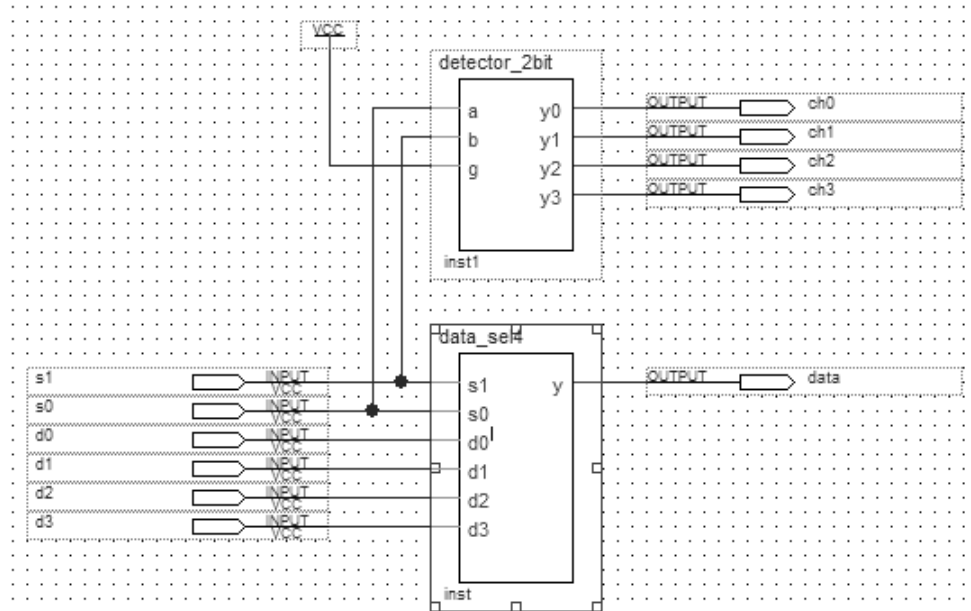





## 5.4 3-bit decoder

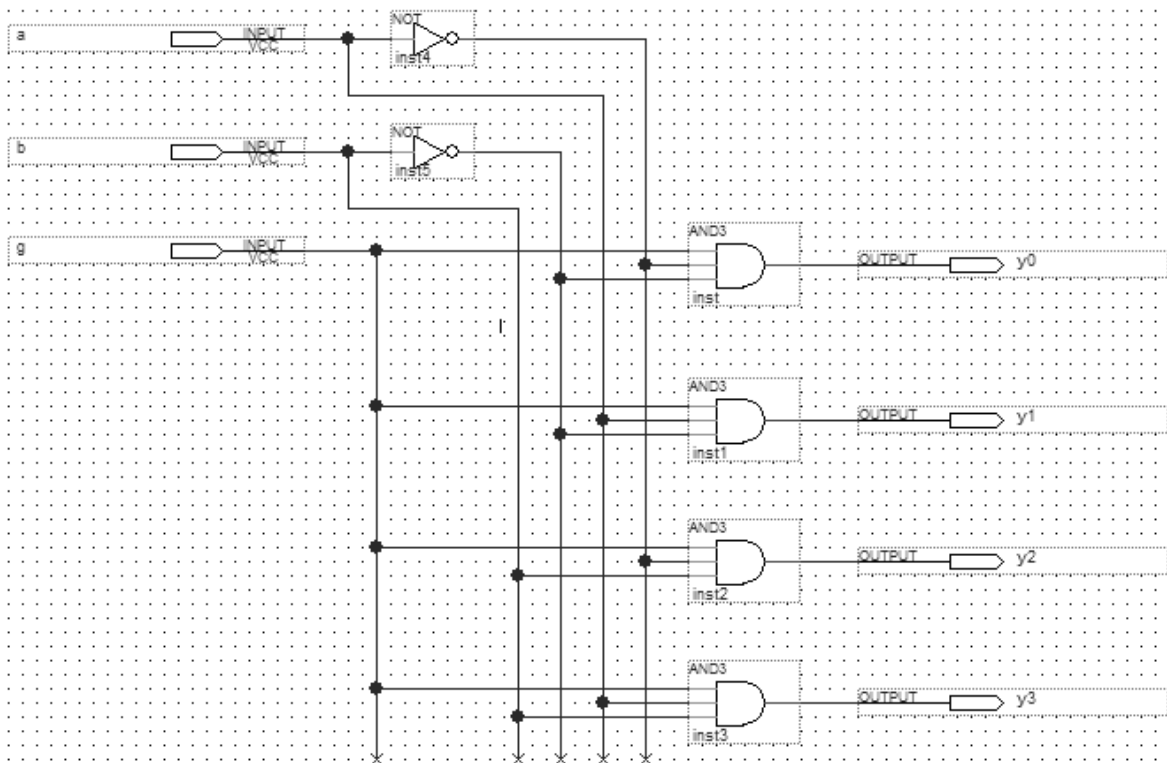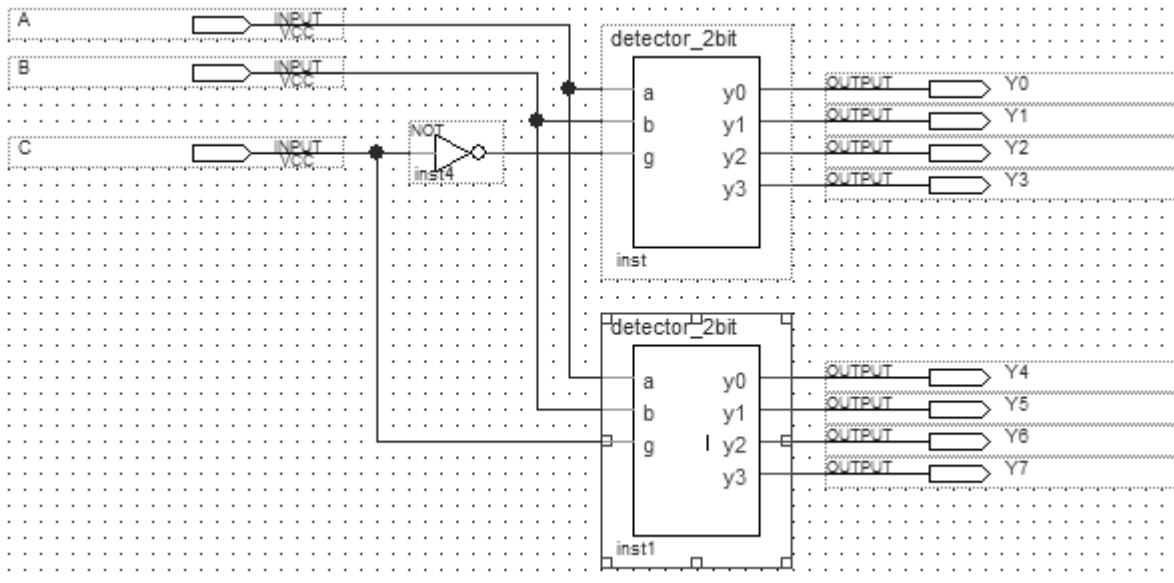



## 5.5 4-bit decoder

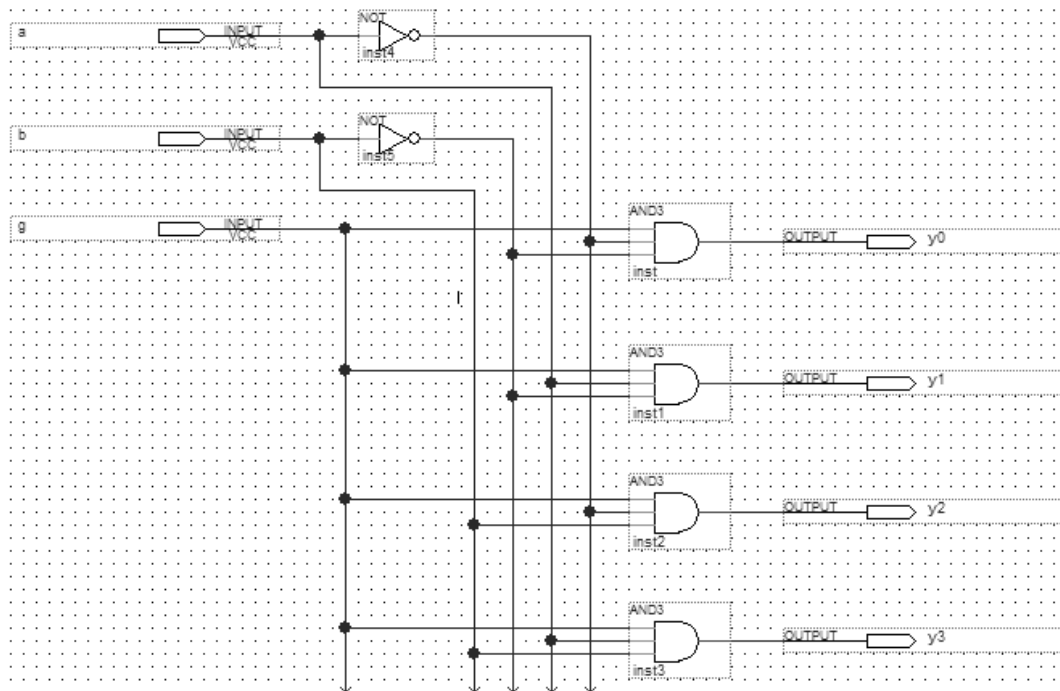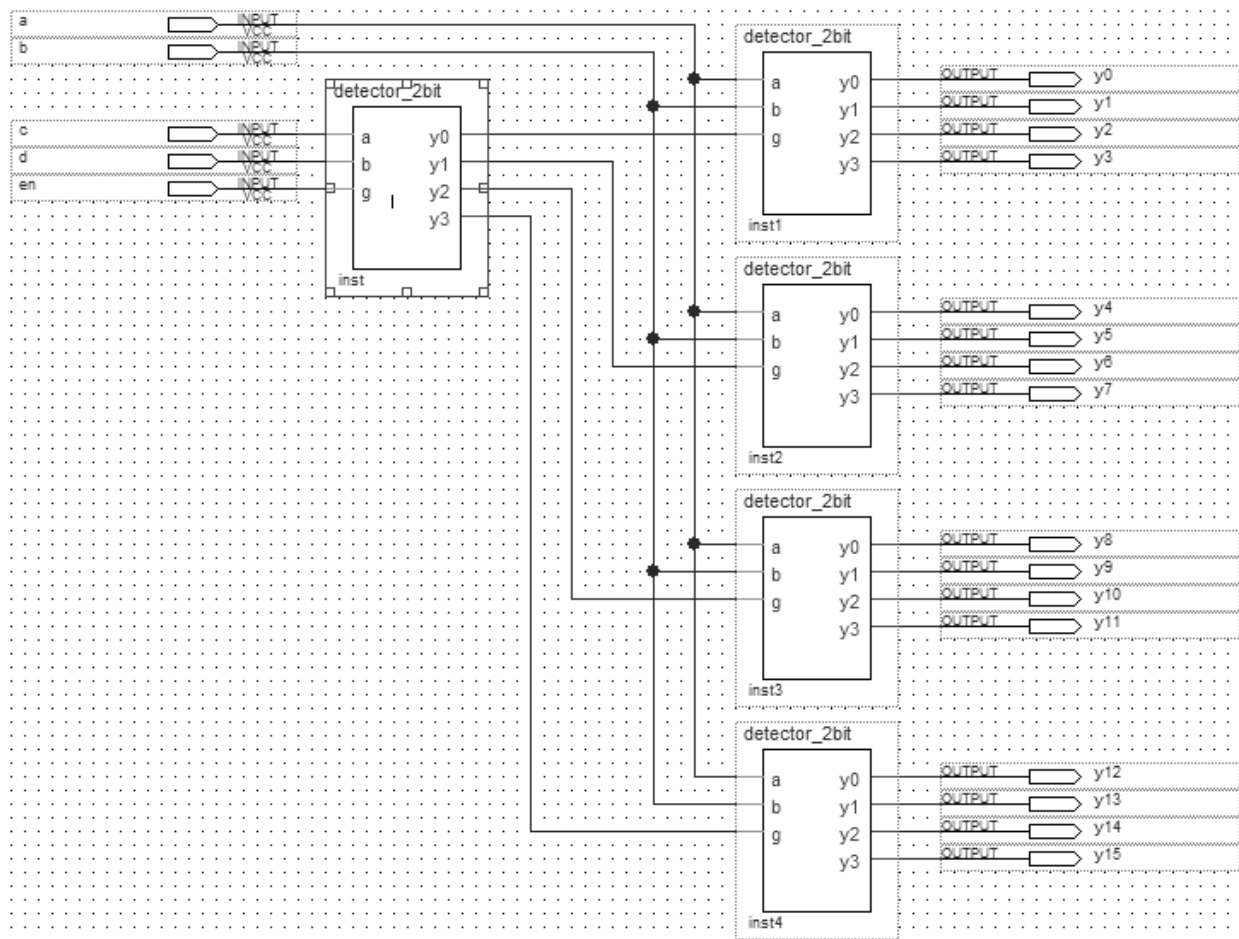

## 5.6 Data transmission

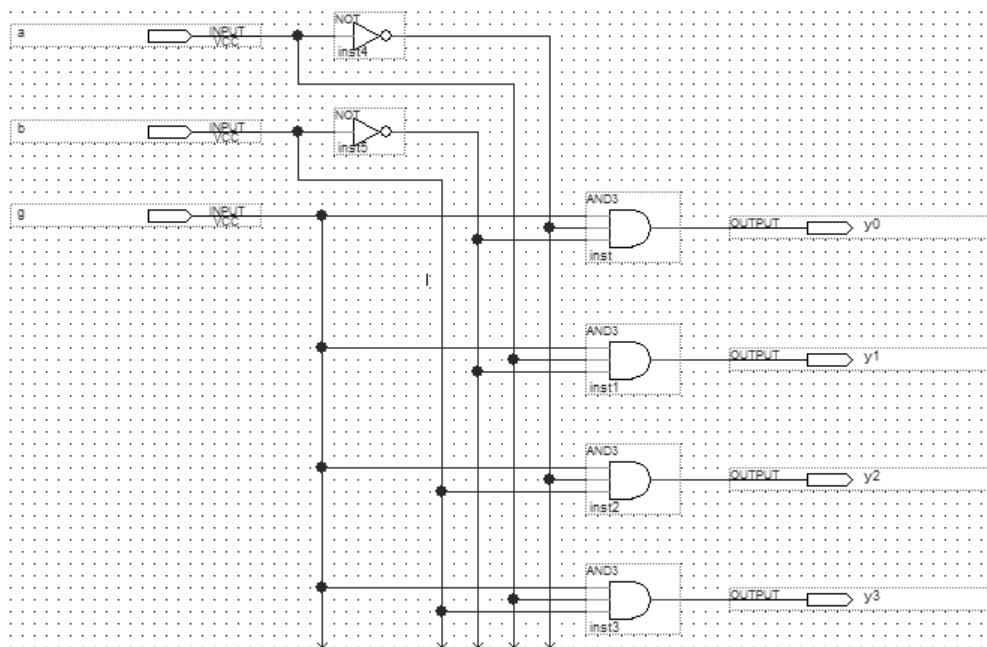 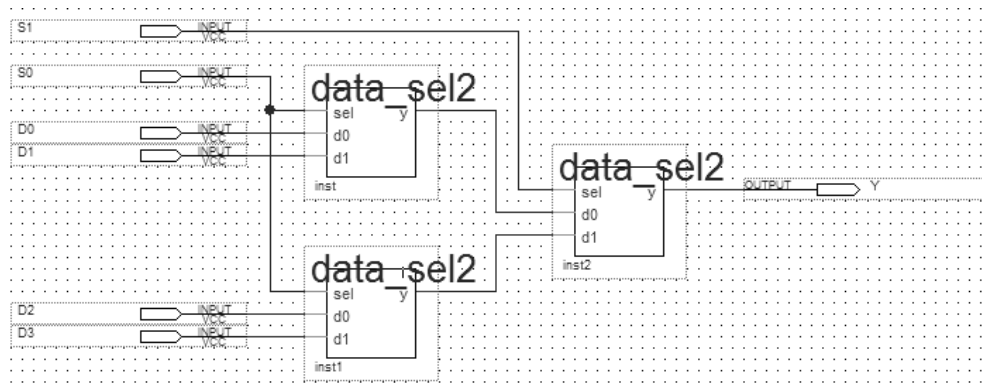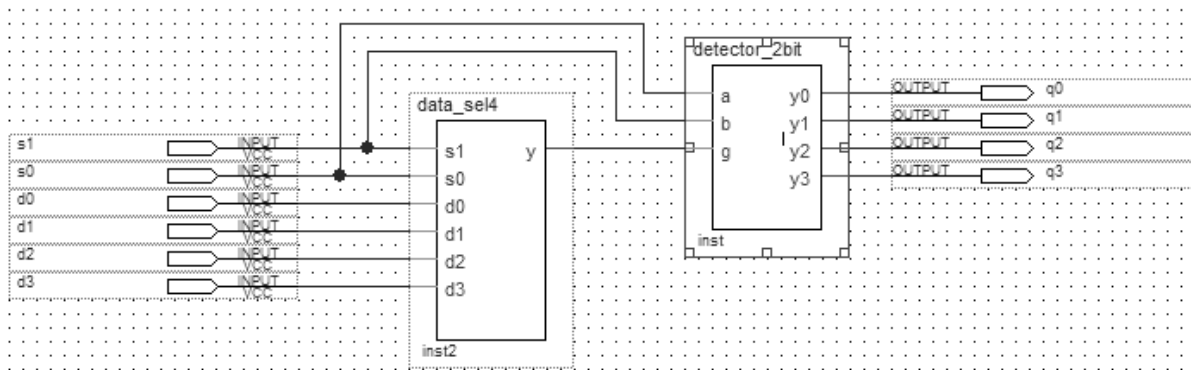

## 5.7 2-bit magnitude comparator

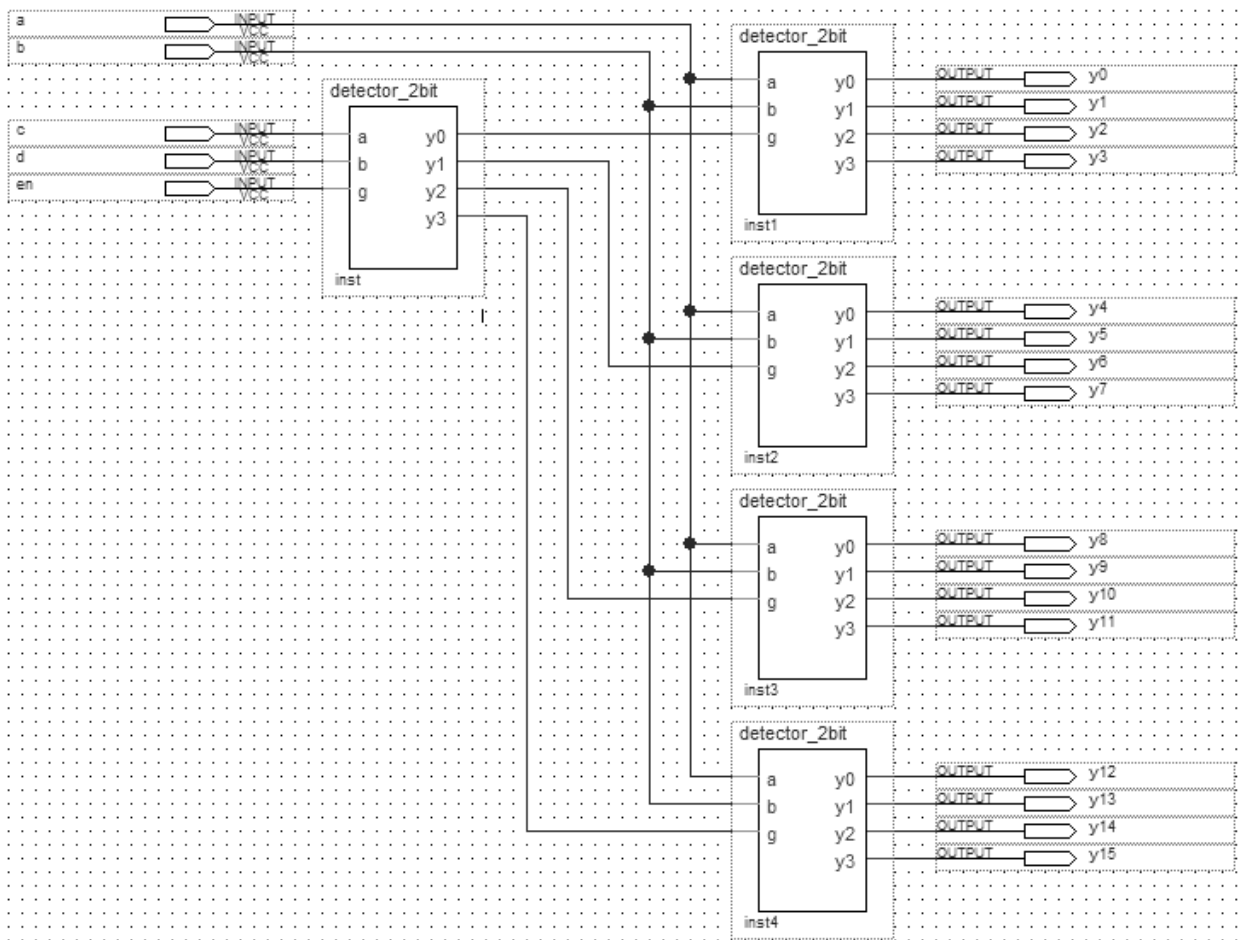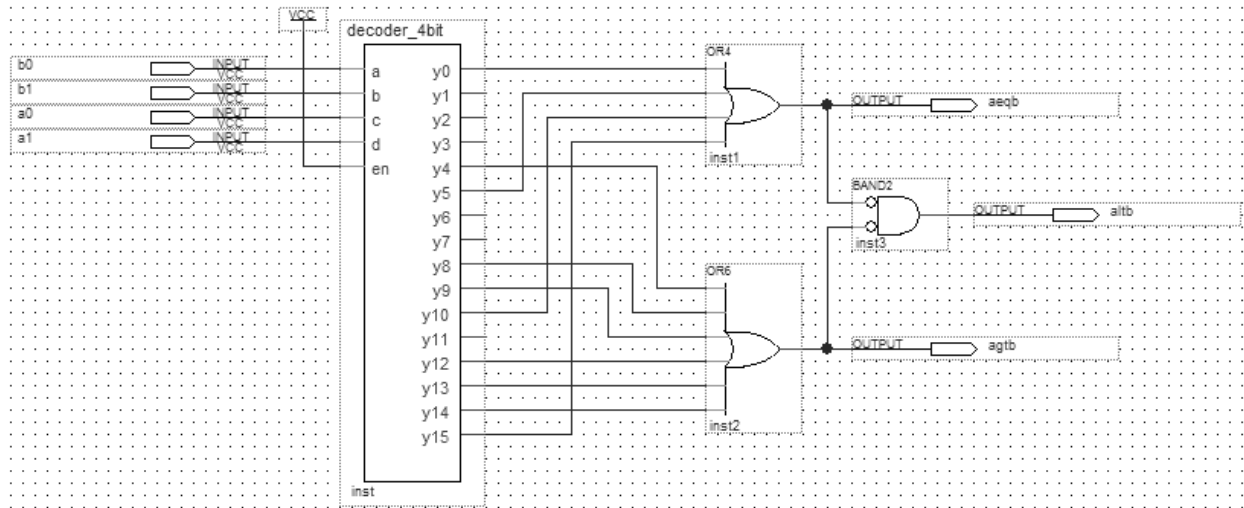



## Unit 6A Combinational Circuit Design with AHDL

6A.1 2-bit comparator (see Lab Manual Example 6-1 & Quartus Tutorial 4 – HDL)


6A.2 Code converter (see Lab Manual Example 6-2 & Quartus Tutorial 4 – HDL)

6A.3 Modified data selector

```

SUBDESIGN multiplexer      -- project 6A.3
(
    en, d[1..0], s        :INPUT;
    y                      :OUTPUT;
)
BEGIN
    -- CASE nested inside IF statement
    IF !en THEN           -- evaluate CASE when en is low
        CASE s IS
            WHEN 0        =>    y = d0;
            WHEN 1        =>    y = d1;
        END CASE;
    ELSE
        y = GND;          -- disabled
    END IF;
END;

```


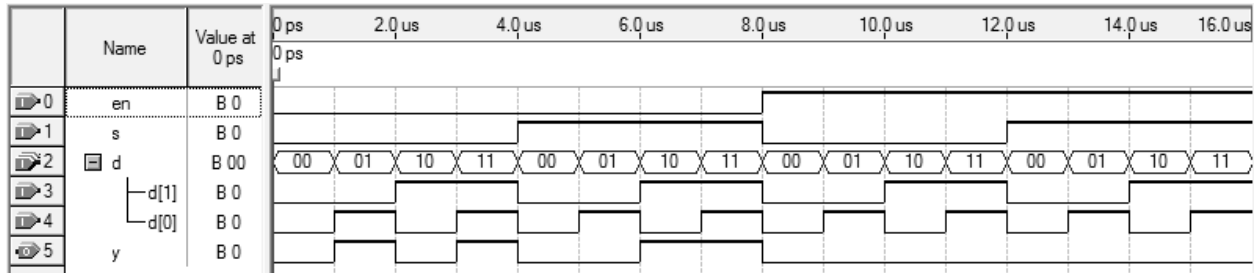


## 6A.4 Gray-code-to-binary conversion

```

SUBDESIGN gray
(
    gray[5..0]      :INPUT;
    bin[5..0]       :OUTPUT;
)
BEGIN
    bin5 = gray5;           -- MSBs are the same
    bin4 = bin5 $ gray4;    -- XOR prev out $ next in
    bin3 = bin4 $ gray3;
    bin2 = bin3 $ gray2;
    bin1 = bin2 $ gray1;
    bin0 = bin1 $ gray0;
END;

```

  


## 6A.5 BCD-to-binary converter

```

SUBDESIGN BCD2bin
(
    bcd[4..0]          :INPUT;
    bin[3..0], err     :OUTPUT;
)
BEGIN
    CASE bcd[] IS
        WHEN H"00"    => bin[] = H"0"; err = GND;
        WHEN H"01"    => bin[] = H"1"; err = GND;
        WHEN H"02"    => bin[] = H"2"; err = GND;
        WHEN H"03"    => bin[] = H"3"; err = GND;
        WHEN H"04"    => bin[] = H"4"; err = GND;
        WHEN H"05"    => bin[] = H"5"; err = GND;
        WHEN H"06"    => bin[] = H"6"; err = GND;
        WHEN H"07"    => bin[] = H"7"; err = GND;
        WHEN H"08"    => bin[] = H"8"; err = GND;
        WHEN H"09"    => bin[] = H"9"; err = GND;
        WHEN H"10"    => bin[] = H"A"; err = GND;
        WHEN H"11"    => bin[] = H"B"; err = GND;
        WHEN H"12"    => bin[] = H"C"; err = GND;
        WHEN H"13"    => bin[] = H"D"; err = GND;
        WHEN H"14"    => bin[] = H"E"; err = GND;
        WHEN H"15"    => bin[] = H"F"; err = GND;
        WHEN OTHERS   => bin[] = H"0"; err = VCC;
    END CASE;
END;

```

 

## 6A.6 Binary-to-BCD converter

```
SUBDESIGN bin2BCD
(
    bin[4..0]      :INPUT;
    bcd[5..0]      :OUTPUT;
)
BEGIN
    TABLE          -- use hex to define each BCD digit
        bin[]       =>    bcd[];
        B"00000"    =>    H"00";
        B"00001"    =>    H"01";
        B"00010"    =>    H"02";
        B"00011"    =>    H"03";
        B"00100"    =>    H"04";
        B"00101"    =>    H"05";
        B"00110"    =>    H"06";
        B"00111"    =>    H"07";
        B"01000"    =>    H"08";
        B"01001"    =>    H"09";
        B"01010"    =>    H"10";
        B"01011"    =>    H"11";
        B"01100"    =>    H"12";
        B"01101"    =>    H"13";
        B"01110"    =>    H"14";
        B"01111"    =>    H"15";
        B"10000"    =>    H"16";
        B"10001"    =>    H"17";
        B"10010"    =>    H"18";
        B"10011"    =>    H"19";
        B"10100"    =>    H"20";
        B"10101"    =>    H"21";
        B"10110"    =>    H"22";
        B"10111"    =>    H"23";
        B"11000"    =>    H"24";
        B"11001"    =>    H"25";
        B"11010"    =>    H"26";
        B"11011"    =>    H"27";
        B"11100"    =>    H"28";
        B"11101"    =>    H"29";
        B"11110"    =>    H"30";
        B"11111"    =>    H"31";
    END TABLE;
END;
```

### 6A.7 Tens digit detector

```
SUBDESIGN decade
(
    num[5..0]      :INPUT;
    tens[6..0]     :OUTPUT;
)
BEGIN
    -- 1st true condition determines output
    IF      num[] <= 9   THEN  tens[] = B"0000001";
    ELSIF   num[] <= 19  THEN  tens[] = B"0000010";
    ELSIF   num[] <= 29  THEN  tens[] = B"0000100";
    ELSIF   num[] <= 39  THEN  tens[] = B"0001000";
    ELSIF   num[] <= 49  THEN  tens[] = B"0010000";
    ELSIF   num[] <= 59  THEN  tens[] = B"0100000";
    ELSE
        tens[] = B"1000000";
    END IF;
END;
```

### 6A.8 Lamp display

```
SUBDESIGN lamps
(
    in[2..0]       :INPUT;
    out[7..1]      :OUTPUT;
)
BEGIN
    -- test every in[] condition
    CASE in[] IS
        WHEN 0      => out[] = B"0000000";
        WHEN 1      => out[] = B"0000001";
        WHEN 2      => out[] = B"0000011";
        WHEN 3      => out[] = B"0000111";
        WHEN 4      => out[] = B"0001111";
        WHEN 5      => out[] = B"0011111";
        WHEN 6      => out[] = B"0111111";
        WHEN 7      => out[] = B"1111111";
    END CASE;
END;
```

## 6A.9 Programmable logic unit

```
SUBDESIGN logic_unit
(
    a[3..0], b[3..0], s[1..0], en           :INPUT;
    f[3..0]                                 :OUTPUT;
)
BEGIN
    -- control input selects function
    IF      s[] == 0 & en THEN f[] = a[] # b[];
    ELSIF   s[] == 1 & en THEN f[] = a[] & b[];
    ELSIF   s[] == 2 & en THEN f[] = a[] $ b[];
    ELSIF   s[] == 3 & en THEN f[] = !a[];
    ELSE    f[] = B"0000";      -- output disabled
    END IF;
END;
```

## 6A.10 Number range detector

```
SUBDESIGN range
(
    num[4..0], en           :INPUT;
    range[4..1]             :OUTPUT;
)
BEGIN
    -- determine if num[] in ranges when enabled
    -- active-hi outs
    range1 = num[] >= 4 & num[] <= 12 & en;
    range2 = num[] >= 15 & num[] <= 20 & en;
    range3 = num[] >= 18 & num[] <= 24 & en;
    -- active-low out
    range4 = !(num[] >= 26 & num[] <= 30 & en);
END;
```

## 6A.11 Data switcher

```
SUBDESIGN switcher
(
    en, in[1..0], s[1..0]       :INPUT;
    out[1..0]                   :OUTPUT;
)
BEGIN
    IF !en THEN -- detect active-low enable
        CASE s[] IS -- determine control input
            WHEN 0 => out1 = in1; out0 = in0;
            WHEN 1 => out1 = in0; out0 = in0;
            WHEN 2 => out1 = in1; out0 = in1;
            WHEN 3 => out1 = in0; out0 = in1;
        END CASE;
    ELSE out[] = B"00"; -- disabled
    END IF;
END;
```

## Unit 6V Combinational Circuit Design with VHDL

6V.1 2-bit comparator (see Lab Manual Example 6-1 & Quartus Tutorial 4 – HDL)

6V.2 Code converter (see Lab Manual Example 6-2 & Quartus Tutorial 4 – HDL)


6V.3 Modified data selector

```

ENTITY multiplexer IS
PORT ( en      :IN BIT;
      d      :IN BIT_VECTOR (1 DOWNTO 0);
      s      :IN BIT;
      y      :OUT BIT );
END multiplexer;

ARCHITECTURE modify OF multiplexer IS
BEGIN
    PROCESS (en, d, s)    -- invoke on changes
    BEGIN
        IF (en = '0') THEN    -- en low?
            CASE s IS        -- nested CASE
                WHEN '0' =>    y <= d(0);
                WHEN '1' =>    y <= d(1);
            END CASE;
        ELSE -- otherwise disabled output
            y <= '0';
        END IF;
    END PROCESS;
END modify;

```


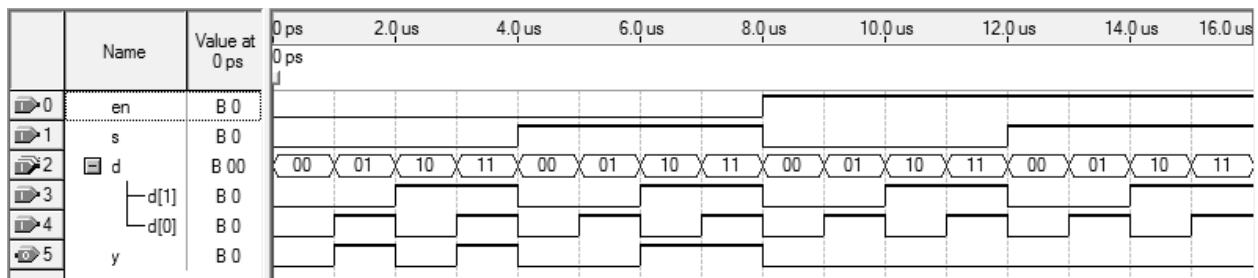


## 6V.4 Gray-code-to-binary conversion

```

ENTITY gray IS
PORT (      gray      :IN BIT_VECTOR (5 DOWNTO 0);
       bin           :OUT BIT_VECTOR (5 DOWNTO 0) );
END gray;
ARCHITECTURE converter OF gray IS
SIGNAL temp          :BIT_VECTOR (5 DOWNTO 0);
BEGIN
    temp(5) <= gray(5);           -- MSBs are the same
    temp(4) <= temp(5) XOR gray(4);
    temp(3) <= temp(4) XOR gray(3);
    temp(2) <= temp(3) XOR gray(2);
    temp(1) <= temp(2) XOR gray(1);
    temp(0) <= temp(1) XOR gray(0);
    bin <= temp;                  -- assign temp to output
END converter;

```

  




## 6V.5 BCD-to-binary converter

```

ENTITY bcd2bin IS
PORT (      bcd      :IN BIT_VECTOR (4 DOWNTO 0);
        bin         :OUT BIT_VECTOR (3 DOWNTO 0);
        err         :OUT BIT
        );
END bcd2bin;
ARCHITECTURE a OF bcd2bin IS
BEGIN
    PROCESS (bcd)          -- bcd change invokes process
    BEGIN
        CASE bcd IS        -- test all bcd conditions
            WHEN "00000" => bin <= "0000";    err <= '0';
            WHEN "00001" => bin <= "0001";    err <= '0';
            WHEN "00010" => bin <= "0010";    err <= '0';
            WHEN "00011" => bin <= "0011";    err <= '0';
            WHEN "00100" => bin <= "0100";    err <= '0';
            WHEN "00101" => bin <= "0101";    err <= '0';
            WHEN "00110" => bin <= "0110";    err <= '0';
            WHEN "00111" => bin <= "0111";    err <= '0';
            WHEN "01000" => bin <= "1000";    err <= '0';
            WHEN "01001" => bin <= "1001";    err <= '0';
            WHEN "10000" => bin <= "1010";    err <= '0';
            WHEN "10001" => bin <= "1011";    err <= '0';
            WHEN "10010" => bin <= "1100";    err <= '0';
            WHEN "10011" => bin <= "1101";    err <= '0';
            WHEN "10100" => bin <= "1110";    err <= '0';
            WHEN "10101" => bin <= "1111";    err <= '0';
            WHEN OTHERS => bin <= "0000";    err <= '1';
        END CASE;
    END PROCESS;
END a;

```

 

## 6V.6 Binary-to-BCD converter

```
ENTITY bin2bcd IS
PORT (      bin      :IN BIT_VECTOR (4 DOWNTO 0);
        bcd         :OUT BIT_VECTOR (5 DOWNTO 0) );
END bin2bcd;
ARCHITECTURE a OF bin2bcd IS
BEGIN
    PROCESS (bin)          -- bin change invokes process
    BEGIN
        CASE bin IS        -- check all input values
            WHEN "00000" => bcd <= "000000";
            WHEN "00001" => bcd <= "000001";
            WHEN "00010" => bcd <= "000010";
            WHEN "00011" => bcd <= "000011";
            WHEN "00100" => bcd <= "000100";
            WHEN "00101" => bcd <= "000101";
            WHEN "00110" => bcd <= "000110";
            WHEN "00111" => bcd <= "000111";
            WHEN "01000" => bcd <= "001000";
            WHEN "01001" => bcd <= "001001";
            WHEN "01010" => bcd <= "010000";
            WHEN "01011" => bcd <= "010001";
            WHEN "01100" => bcd <= "010010";
            WHEN "01101" => bcd <= "010011";
            WHEN "01110" => bcd <= "010100";
            WHEN "01111" => bcd <= "010101";
            WHEN "10000" => bcd <= "010110";
            WHEN "10001" => bcd <= "010111";
            WHEN "10010" => bcd <= "011000";
            WHEN "10011" => bcd <= "011001";
            WHEN "10100" => bcd <= "100000";
            WHEN "10101" => bcd <= "100001";
            WHEN "10110" => bcd <= "100010";
            WHEN "10111" => bcd <= "100011";
            WHEN "11000" => bcd <= "100100";
            WHEN "11001" => bcd <= "100101";
            WHEN "11010" => bcd <= "100110";
            WHEN "11011" => bcd <= "100111";
            WHEN "11100" => bcd <= "101000";
            WHEN "11101" => bcd <= "101001";
            WHEN "11110" => bcd <= "110000";
            WHEN "11111" => bcd <= "110001";

        END CASE;
    END PROCESS;
END a;
```

## 6V.7 Tens digit detector

```
ENTITY decade IS
PORT (      num      :IN INTEGER RANGE 0 TO 63;
      tens          :OUT BIT_VECTOR (6 DOWNT0 0) );
END decade;

ARCHITECTURE b OF decade IS
BEGIN
    PROCESS (num)          -- num invokes process
    BEGIN -- 1st true condition determines output
        IF      num <= 9  THEN  tens <= B"0000001";
        ELSIF   num <= 19 THEN  tens <= B"0000010";
        ELSIF   num <= 29 THEN  tens <= B"0000100";
        ELSIF   num <= 39 THEN  tens <= B"0001000";
        ELSIF   num <= 49 THEN  tens <= B"0010000";
        ELSIF   num <= 59 THEN  tens <= B"0100000";
        ELSE
            tens <= B"1000000";
        END IF;
    END PROCESS;
END b;
```

## 6V.8 Lamp display

```
ENTITY lamps IS
PORT (      num      :IN INTEGER RANGE 0 TO 7;
      lites          :OUT BIT_VECTOR (7 DOWNT0 1) );
END lamps;

ARCHITECTURE cases OF lamps IS
BEGIN
    PROCESS (num)          -- num invokes process
    BEGIN
        CASE num IS        -- test every num condition
            WHEN 0 => lites <= "0000000";
            WHEN 1 => lites <= "0000001";
            WHEN 2 => lites <= "0000011";
            WHEN 3 => lites <= "0000111";
            WHEN 4 => lites <= "0001111";
            WHEN 5 => lites <= "0011111";
            WHEN 6 => lites <= "0111111";
            WHEN 7 => lites <= "1111111";
        END CASE;
    END PROCESS;
END cases;
```

## 6V.9 Programmable logic unit

```
ENTITY logic_unit IS
PORT (      a, b      :IN BIT_VECTOR (3 DOWNTO 0);
        s            :IN BIT_VECTOR (1 DOWNTO 0);
        en           :IN BIT;
        f            :OUT BIT_VECTOR (3 DOWNTO 0)      );
END logic_unit;

ARCHITECTURE program OF logic_unit IS
BEGIN
    PROCESS (a, b, s, en)      -- any input change
    BEGIN                      -- control input selects function
        IF                    s = "00" AND en = '1'
        THEN                  f <= a OR b;
        ELSIF                 s = "01" AND en = '1'
        THEN                  f <= a AND b;
        ELSIF                 s = "10" AND en = '1'
        THEN                  f <= a XOR b;
        ELSIF                 s = "11" AND en = '1'
        THEN                  f <= NOT a;
        ELSE                  f <= "0000";      -- disabled
        END IF;
    END PROCESS;
END program;
```

## 6V.10 Number range detector

```
ENTITY val_range IS
PORT (      en      :IN BIT;
        num       :IN INTEGER RANGE 0 TO 31;
        values    :OUT BIT_VECTOR (4 DOWNT0 1)      );
END val_range;

ARCHITECTURE proj OF val_range IS
BEGIN
    PROCESS (en, num)
    BEGIN
        IF en = '1' THEN                                -- enabled
            IF      (num >= 4 AND num <= 12)
                THEN values <= "1001";
            ELSIF (num >= 15 AND num <= 20)
                THEN values <= "1010";
            ELSIF (num >= 21 AND num <= 24)
                THEN values <= "1100";
            ELSIF (num >= 26 AND num <= 30)
                THEN values <= "0000";
            ELSE
                values <= "1000";
            END IF;    -- determine num
        ELSE
            values <= "1000";    -- disabled
        END IF;
    END PROCESS;
END proj;
```

## 6V.11 Data switcher

```
ENTITY switcher IS
PORT (   en           :IN BIT;
        input, sel    :IN BIT_VECTOR (1 DOWNTO 0);
        output        :OUT BIT_VECTOR (1 DOWNTO 0) );
END switcher;

ARCHITECTURE switch OF switcher IS
BEGIN
    PROCESS (en, input, sel)          -- sensitivity list
    BEGIN
        IF en = '0' THEN              -- active-low enable
            CASE sel IS                -- control input
                WHEN "00" =>
                    output(1) <= input(1);
                    output(0) <= input(0);
                WHEN "01" =>
                    output(1) <= input(0);
                    output(0) <= input(0);
                WHEN "10" =>
                    output(1) <= input(1);
                    output(0) <= input(1);
                WHEN "11" =>
                    output(1) <= input(0);
                    output(0) <= input(1);
            END CASE;
        ELSE
            output <= "00";            -- disabled
        END IF;
    END PROCESS;
END switch;
```

## Unit 7 Testing Flip-Flops and Sequential Circuit Applications

### 7.1 NAND SR latch

Set	Reset	Q	Qbar	
0	0	1	1	invalid
0	1	1	0	set
1	0	0	1	reset
1	1	Q	Qbar	hold

active-low control inputs

### 7.2 D latch


D latch is transparent when  $EN = 1$ , stores data when  $EN = 0$

### 7.3 JK flip-flop

J & K inputs are synchronous, active-low PRE & CLR are asynchronous, synchronous controls require clock for triggering, asynchronous controls have priority, PGT clock is triggering control


J	K	CLOCK	PRESET	CLEAR	Qn+1	Function
0	0	↑	1	1	Qn	Hold
0	1	↑	1	1	0	Reset
1	0	↑	1	1	1	Set
1	1	↑	1	1	!Qn	Toggle
X	X	X	0	1	1	Asynch preset
X	X	X	1	0	0	Asynch clear

### 7.4 D latch vs. D flip-flop

 

D latch is level-enabled (active-high) & D flip-flop is edge-triggered (positive going).

### 7.5 Binary counters

 


count sequence: 000 thru 111 & recycle → mod-8 up counter

synchronous counter → FFs are clocked simultaneously

active-high enable

## 7.6 Counter timing diagram

 


## 7.7 Frequency division

(assuming 10 kHz clock input frequency)

Signal	Frequency	Frequency Relationship
Clock	10 kHz	Input (assumed frequency)
QA	5 kHz	$\text{Freq}_{QA} = \text{Freq}_{\text{Clock}} \div 2$
QB	2.5 kHz	$\text{Freq}_{QB} = \text{Freq}_{\text{Clock}} \div 4$
QC	1.25 kHz	$\text{Freq}_{QC} = \text{Freq}_{\text{Clock}} \div 8$

## 7.8 4-bit binary counter

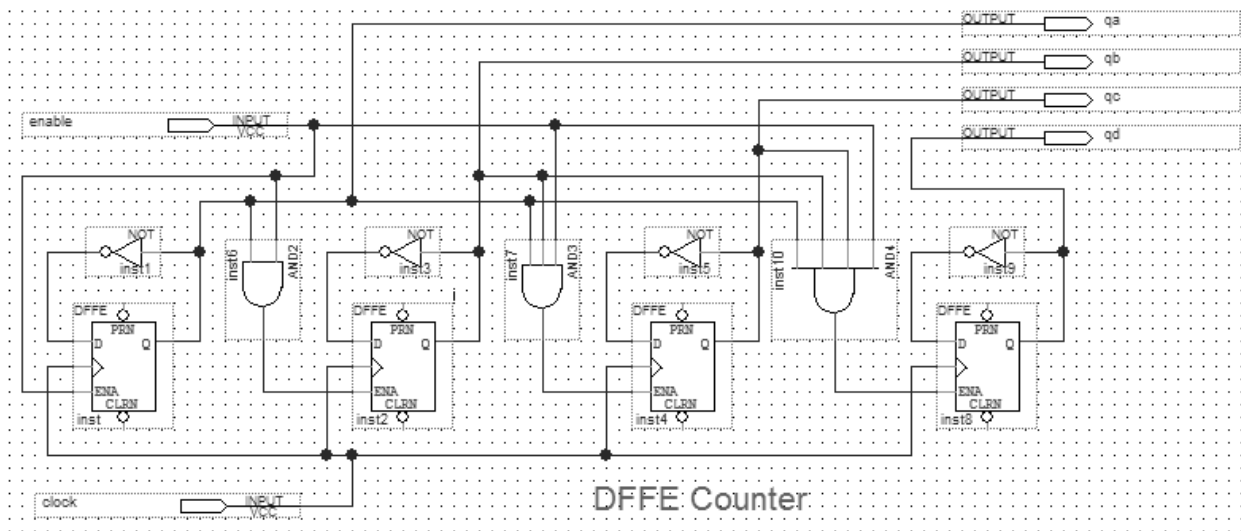

count sequence: 0000 thru 1111 & recycle → mod-16 up counter




## 7.9 4-bit register

q0 is the LSB because the D input for that FF is connected to qa, which is the LSB for the counter. q3 is the MSB because D input is connected to qd, the counter MSB.



Register is  $\uparrow$ -edge triggered.

Register holds data between clocks.

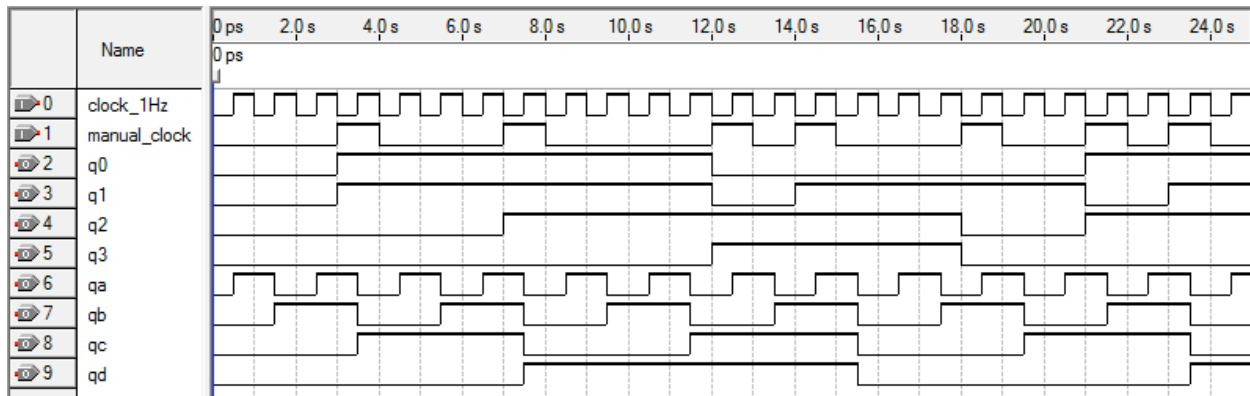If level-enabled, register would track the data input for the entire time that it is enabled.



## 7.10 LPM\_FF megafunction

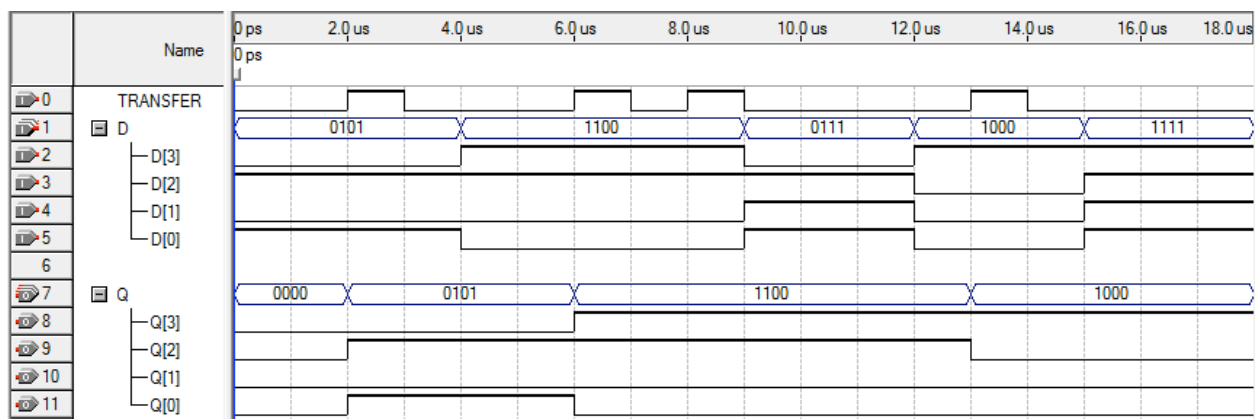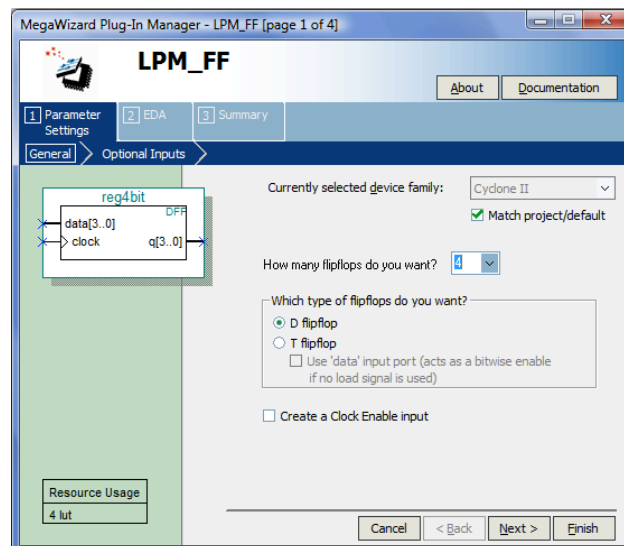

## 7.11 Binary counter

```
SUBDESIGN look_up_table
( q[3..0]      :INPUT;
  d[3..0]      :OUTPUT;)
BEGIN
CASE q[] IS
  WHEN H"0" =>    d[] = H"1";
  WHEN H"1" =>    d[] = H"2";
  WHEN H"2" =>    d[] = H"3";
  WHEN H"3" =>    d[] = H"4";
  WHEN H"4" =>    d[] = H"5";
  WHEN H"5" =>    d[] = H"6";
  WHEN H"6" =>    d[] = H"7";
  WHEN H"7" =>    d[] = H"8";
  WHEN H"8" =>    d[] = H"9";
  WHEN H"9" =>    d[] = H"A";
  WHEN H"A" =>    d[] = H"B";
  WHEN H"B" =>    d[] = H"C";
  WHEN H"C" =>    d[] = H"D";
  WHEN H"D" =>    d[] = H"E";
  WHEN H"E" =>    d[] = H"F";
  WHEN H"F" =>    d[] = H"0";
END CASE;
END;
```


```
ENTITY look_up_table IS
PORT ( q      :IN BIT_VECTOR (3 DOWNTO 0);
      d      :OUT BIT_VECTOR (3 DOWNTO 0));
END look_up_table;
ARCHITECTURE vhd1 OF look_up_table IS
BEGIN
PROCESS (q)
BEGIN
CASE q IS
  WHEN X"0" =>    d <= X"1";
  WHEN X"1" =>    d <= X"2";
  WHEN X"2" =>    d <= X"3";
  WHEN X"3" =>    d <= X"4";
  WHEN X"4" =>    d <= X"5";
  WHEN X"5" =>    d <= X"6";
  WHEN X"6" =>    d <= X"7";
  WHEN X"7" =>    d <= X"8";
  WHEN X"8" =>    d <= X"9";
  WHEN X"9" =>    d <= X"A";
  WHEN X"A" =>    d <= X"B";
  WHEN X"B" =>    d <= X"C";
```

```

        WHEN X"C" =>    d <= X"D";
        WHEN X"D" =>    d <= X"E";
        WHEN X"E" =>    d <= X"F";
        WHEN X"F" =>    d <= X"0";
    END CASE;
END PROCESS;
END vhdl;

```

## 7.12 Cascading counters

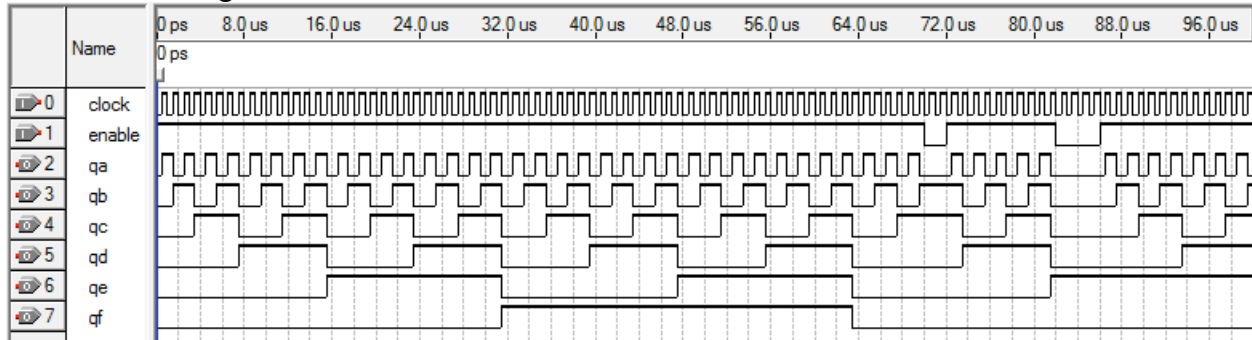

MSB: QF

AND gate detects 111 (terminal counter state) for QC QB QA

Enable controls QF QE QD counter through AND gate

## 7.13 Debouncing a logic switch

- counter appears to count erratically due to receiving multiple pulses on clock input from bouncing switch
- counter should count correctly (0000 through 1111) with latch  
latch see a "hold" command when switch bounces open  
pull-up resistors ensure that open latch inputs are held high

## Unit 8 Timing and Waveshaping Circuits

### 8.1 Schmitt trigger waveshaper

Rounded output waveform for 7404

Square output waveform for 74LS14; triggers at approximately 1.6 V and 0.8 V on input waveform.

### 8.2 Pulse stretcher

$t_p = 0.693 RC$  example solution:

$t_p = 0.47 \text{ s.}$  using  $C = 10 \mu\text{f}$  &  $R = 68 \text{ k}\Omega$

### 8.3 Variable frequency clock

duty cycle =  $(R_A + R_B)/(R_A + 2R_B) \approx 50\%$  if  $R_A \ll R_B$  with  $R_A \geq 1 \text{ k}\Omega$

frequency =  $1.44/(R_A + 2R_B)C$

example solution:

duty cycle = 50.4% with  $R_A = 1 \text{ k}\Omega$  &  $R_B = 68 \text{ k}\Omega$

capacitor	frequency
10 $\mu\text{f}$	1.05 Hz
0.01 $\mu\text{f}$	1.05 kHz
0.001 $\mu\text{f}$	10.53 kHz

### 8.4 Waveform generator

SIGNAL1:  $T = 1 \text{ ms.}$  & duty cycle = 80%  $\rightarrow$  freq. = 1 kHz

on 555:  $t_L = 200 \mu\text{s} = 0.693 R_B C = 0.693 R_B (0.01 \mu\text{f}) \rightarrow R_B = 28.8 \text{ k}\Omega$

$t_H = 800 \mu\text{s} = 0.693 (R_A + R_B) (0.01 \mu\text{f}) \rightarrow R_A = 86.6 \text{ k}\Omega$

using  $R_A = 82 \text{ k}\Omega$ ,  $R_B = 27 \text{ k}\Omega$ ,  $C = 0.01 \mu\text{f}$ :

$T = 0.94 \text{ ms}$  & duty cycle = 80.1%

on 74221:  $1B = 2A = \text{SIGNAL1}$

$1A = 0$  &  $2B = 1$  &  $1CLR = 2CLR = 1$

$t_p = 0.693 RC$

SIGNAL2:  $t_p = 300 \mu\text{s} \rightarrow$  use 1Q output

using  $C = 0.01 \mu\text{f} \rightarrow R = 43.3 \text{ k}\Omega \rightarrow$  try 47  $\text{k}\Omega$

SIGNAL3:  $t_p = 100 \mu\text{s} \rightarrow$  use  $\overline{2Q}$  output

using  $C = 0.0047 \mu\text{f} \rightarrow R = 30.7 \text{ k}\Omega \rightarrow$  try 33  $\text{k}\Omega$

### 8.5 Variable duty-cycle square wave generator

Assuming  $V_F = 0.7\text{V}$ :

$$T = t_L + t_H = 1.00(R_A + R_B)C$$

$$\therefore f = 1/[(R_A + R_B)C]$$

for  $f = 10\text{ kHz}$ , try  $0.0047\text{ }\mu\text{f}$

$$\rightarrow (R_A + R_B) = 21.3\text{ k}\Omega$$

for D.C. = 15% =  $R_A/(R_A + R_B) = 0.15$

$$\rightarrow R_A = 0.15 (21.3\text{ k}\Omega) = 3.2\text{ k}\Omega$$

for D.C. = 85% =  $R_A/(R_A + R_B) = 0.85$

$$\rightarrow R_A = 0.85 (21.3\text{ k}\Omega) = 18.1\text{ k}\Omega$$

$\therefore$  use  $3.3\text{ k}\Omega + 10\text{ k}\Omega$  pot +  $8.2\text{ k}\Omega$  resistors =  $21.5\text{ k}\Omega = R_A + R_B$

### 8.6 Delayed pulse

use both one-shots in 74221:

1A = trigger, 2A = 1Q

$$t_w = 0.22\text{ ms} = 0.693R_2C_2$$

$$\rightarrow \text{if } C_2 = 0.0047\text{ }\mu\text{f}, R_2 = 68\text{ k}\Omega$$

$$t_d = 0.33\text{ ms} = 0.693R_1C_1$$

$$\rightarrow \text{if } C_1 = 0.01\text{ }\mu\text{f}, R_1 = 47\text{ k}\Omega$$

### 8.7 Clock generator using one-shots

on 74221: 1A = 2Q, 2A = 1Q

$$t_1 = 0.693R_1C = 0.693R_1(0.1\text{ }\mu\text{f})$$

$$\rightarrow \text{for } 5\text{ ms}, R_1 = 72\text{ k}\Omega$$

try  $R_1 = 72\text{ k}\Omega$

$$\rightarrow t_1 = 5.68\text{ ms}$$


$$t_2 = 0.693R_2(0.1\text{ }\mu\text{f})$$

$$\rightarrow \text{for } 10\text{ ms} - 5.68\text{ ms} = 4.32\text{ ms}$$


$$R_2 = 62\text{ k}\Omega$$

## Unit 9 Arithmetic Circuit Applications


### 9.1 Four-bit adder

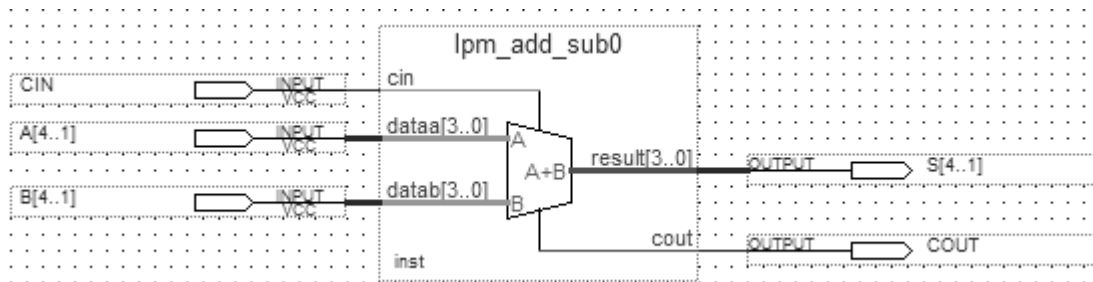

### 9.2 Four-bit binary adder/subtractor

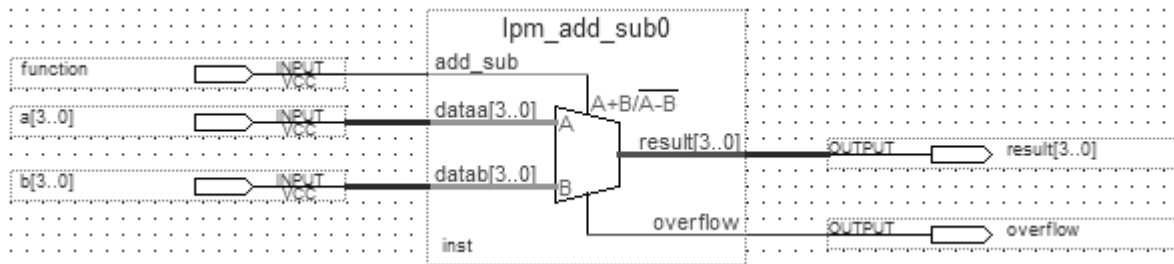


### 9.3 BCD adder (one digit)

 

```
SUBDESIGN gt9detect
(
    cin, z[3..0]           :INPUT;
    cout, correct[3..0]    :OUTPUT;
)
BEGIN
    IF cin == VCC # z[] > 9      THEN
        cout = VCC;
        correct[] = 6;
    ELSE
        cout = GND;
        correct[] = 0;
    END IF;
END;
```

```
ENTITY gt9detect IS
PORT (
    cin       :IN BIT;
    z         :IN INTEGER RANGE 0 TO 15;
    cout      :OUT BIT;
    correct   :OUT INTEGER RANGE 0 TO 15
);
END gt9detect;
ARCHITECTURE vhd1 OF gt9detect IS
BEGIN
    PROCESS (c4, z)
    BEGIN
        -- detect if binary sum >9
        IF c4 = '1' OR z > 9 THEN
            cout <= '1';
            correct <= 6;
        ELSE
            cout <= '0';
            correct <= 0;
        END IF;
    END PROCESS;
END vhd1;
```

## 9.4 BCD to binary converter

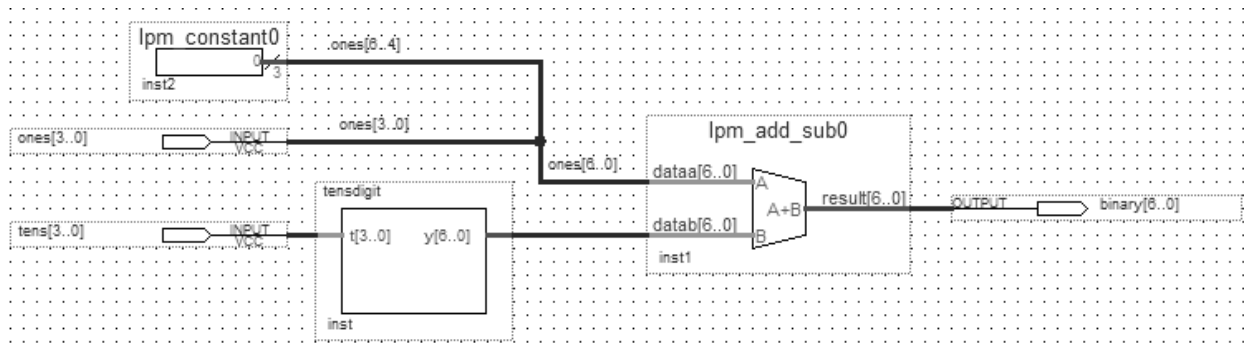


```
SUBDESIGN tensdigit
(
    t[3..0]      :INPUT;
    y[6..0]      :OUTPUT;
)
BEGIN
CASE t[] IS
    WHEN 0 => y[] = 0;
    WHEN 1 => y[] = 10;
    WHEN 2 => y[] = 20;
    WHEN 3 => y[] = 30;
    WHEN 4 => y[] = 40;
    WHEN 5 => y[] = 50;
    WHEN 6 => y[] = 60;
    WHEN 7 => y[] = 70;
    WHEN 8 => y[] = 80;
    WHEN 9 => y[] = 90;
    WHEN OTHERS => y[] = B"1111111";
END CASE;
END;
```

```
ENTITY tensdigit IS
PORT ( t :IN INTEGER RANGE 0 TO 15;
       y :OUT INTEGER RANGE 0 TO 90 );
END tensdigit;
ARCHITECTURE vhdl OF tensdigit IS
BEGIN
    y <= t * 10;
END;
```

	Name	Value at 0 ps	0 ps	10.0 us	20.0 us	30.0 us	40.0 us	50.0 us	60.0 us	70.0 us	80.0 us	90.0 us	100.0 us
0	tens	H 2	2	5	2	7	8	0	1	4	3	9	
5	ones	H 0	0	1	2	3	4	5	6	7	8	9	
10	binary	H 14	14	33	16	49	54	05	10	2F	26	63	



## 9.5 Binary to BCD converter

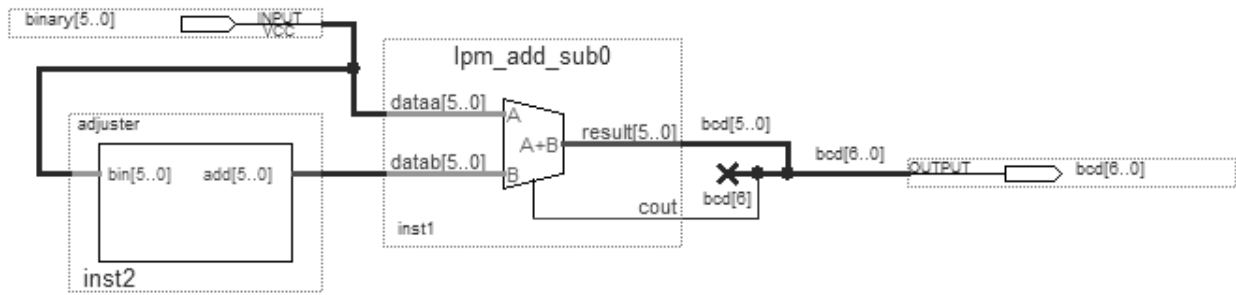

```

SUBDESIGN  adjuster
(
    bin[5..0]      :INPUT;
    add[5..0]      :OUTPUT;
)
BEGIN
    IF    bin[] < 10      THEN add[] = 0;
    ELSIF bin[] < 20      THEN add[] = 6;
    ELSIF bin[] < 30      THEN add[] = 12;
    ELSIF bin[] < 40      THEN add[] = 18;
    ELSIF bin[] < 50      THEN add[] = 24;
    ELSIF bin[] < 60      THEN add[] = 30;
    ELSE
        add[] = 36;
    END IF;
END;

```



```

ENTITY adjuster IS
PORT (
    bin      :IN INTEGER RANGE 0 TO 63;
    add      :OUT INTEGER RANGE 0 TO 63
);
END adjuster;


ARCHITECTURE vhd1 OF adjuster IS
BEGIN
    PROCESS (bin)
    BEGIN
        IF    bin < 10      THEN      add <= 0;
        ELSIF bin < 20      THEN      add <= 6;
        ELSIF bin < 30      THEN      add <= 12;
        ELSIF bin < 40      THEN      add <= 18;
        ELSIF bin < 50      THEN      add <= 24;
        ELSIF bin < 60      THEN      add <= 30;
        ELSE
            add <= 36;
        END IF;
    END PROCESS;
END vhd1;

```

## 9.6 Up/down counter

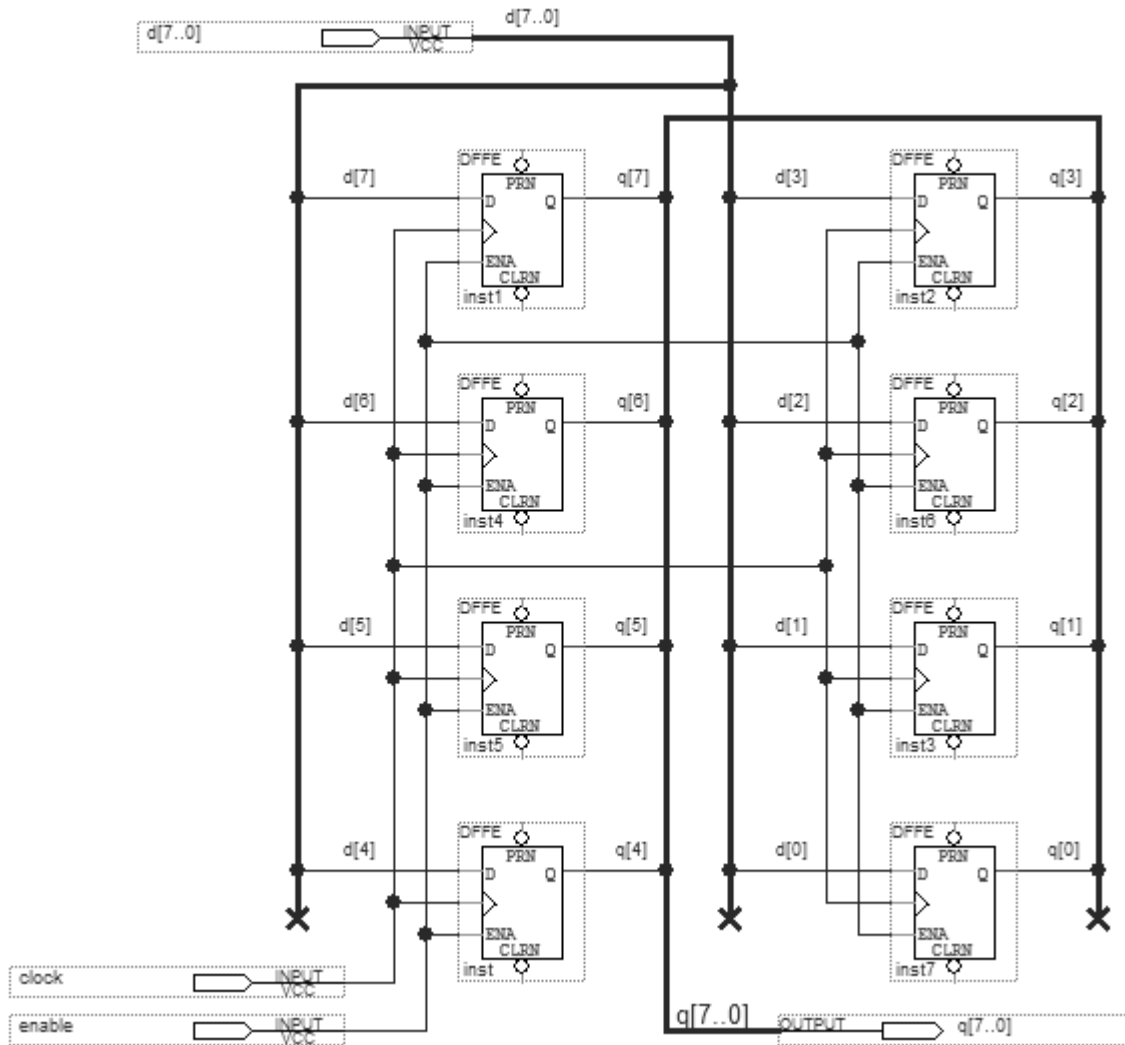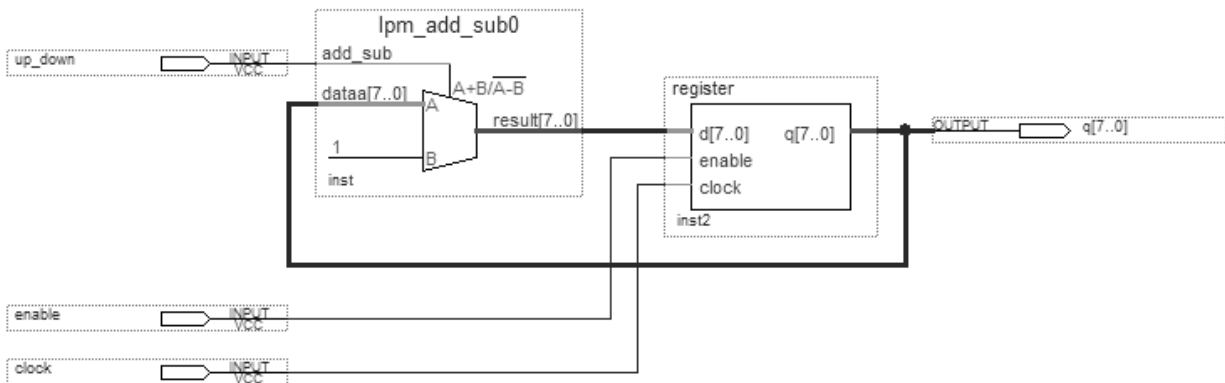

## 9.7 Binary multiplier

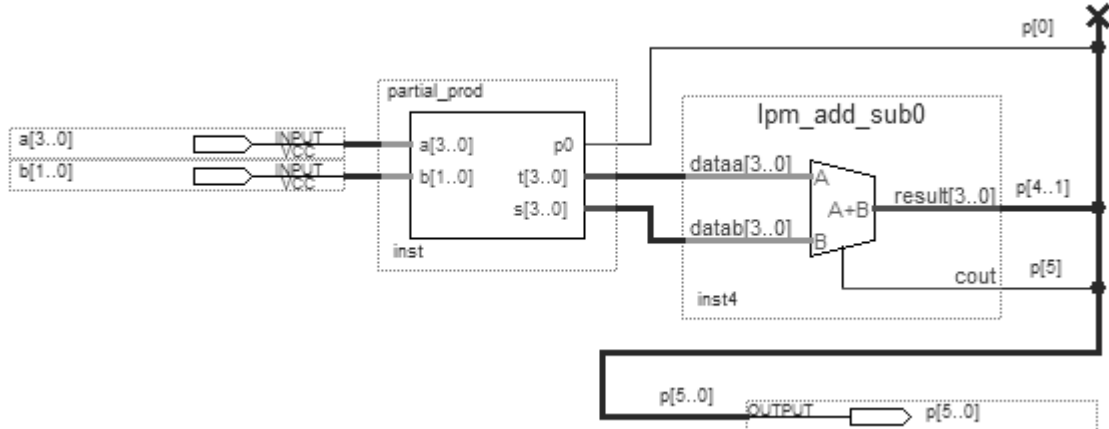


```
SUBDESIGN partial_prod
(
    a[3..0], b[1..0]      :INPUT;
    p0, t[3..0], s[3..0] :OUTPUT;
)
VARIABLE
    r[3..0] :NODE;
BEGIN
    r[3..0] = a[3..0] & b0;
    s[3..0] = a[3..0] & b1;
    t[3..0] = (GND, r[3..1]);
    p0 = r0;
END;
```







```
ENTITY partial_prod IS
PORT (
    a      :IN BIT_VECTOR (3 DOWNT0 0);
    b      :IN BIT_VECTOR (1 DOWNT0 0);
    p0     :OUT BIT;
    s, t   :OUT BIT_VECTOR (3 DOWNT0 0)
);
END partial_prod;

ARCHITECTURE vhd1 OF partial_prod IS
SIGNAL    r      :BIT_VECTOR (3 DOWNT0 0);
BEGIN
    r(3 DOWNT0 0) <= a(3 DOWNT0 0) AND (b(0)&b(0)&b(0)&b(0));
    s(3 DOWNT0 0) <= a(3 DOWNT0 0) AND (b(1)&b(1)&b(1)&b(1));
    t(3 DOWNT0 0) <= '0' & r(3 DOWNT0 1);
    p0 <= r(0);
END vhd1;
```

	Name	Value at 0 ps	30.0 us	34.0 us	38.0 us	42.0 us	46.0 us	50.0 us	54.0 us	58.0 us	62.0 us																							
0	a	H 0	E	F	0	1	2	3	4	5	6	7	8	9	A	B	C	D	E	F	0	1	2	3	4	5	6	7	8	9	A	B	C	D
5	b	H 0	1																															
8	p	H 00	0E	0F	00	02	04	06	08	0A	0C	0E	10	12	14	16	18	1A	1C	1E	00	03	06	09	0C	0F	12	15	18	1B	1E	21	24	27

## 9.8 Multiplier megafunction

 


      	Name	Value at 0 ps	Timeline (0 ps to 32.0 us)																															
			0 ps																															
 0	 a	U 0	<div><div>0</div><div>1</div><div>2</div><div>3</div><div>4</div><div>5</div><div>6</div><div>7</div><div>8</div><div>9</div><div>10</div><div>11</div><div>12</div><div>13</div><div>14</div><div>15</div><div>0</div><div>1</div><div>2</div><div>3</div><div>4</div><div>5</div><div>6</div><div>7</div><div>8</div><div>9</div><div>10</div><div>11</div><div>12</div><div>13</div><div>14</div><div>15</div></div>																															
 5	 b	U 0	<div><div>0</div><div>10</div><div>4</div><div>15</div><div>1</div><div>9</div><div>2</div></div>																															
 10	 prod	U 0	<div><div>0</div><div>40</div><div>50</div><div>60</div><div>70</div><div>80</div><div>36</div><div>40</div><div>44</div><div>48</div><div>52</div><div>56</div><div>60</div><div>0</div><div>15</div><div>30</div><div>45</div><div>60</div><div>5</div><div>6</div><div>7</div><div>8</div><div>9</div><div>90</div><div>99</div><div>108</div><div>26</div><div>28</div><div>30</div></div>																															

## Unit 10 Analyzing and Testing Synchronous Counters

 
### 10.1 Counter 1 (a & b)

Recycling Mod-10 up counter (counts 0 to 9)



 
### 10.2 Counter 2 (a & b)

Recycling Mod-10 down counter (counts 9 down to 0)


 
### 10.3 Counter 3 (a & b)



Recycling Mod-13 up counter (counts 0 to 12)


  
### 10.4 Counter 4 (a & b)

Recycling Mod-9 down counter (counts 9 to 1 after start-up sequence)


Top simulation: JK counter      Bottom simulation: D counter



## Unit 11 Creating and Testing Counter Functions
 
### 11.1 Mod-16 binary counter


LOAD = 0, CLR = 0, EN = 0 → counter stopped



LOAD = 0, CLR = 0, EN = 1

→ counter counts up 0000 to 1111 & recycles, clocked on positive-edge

 
→ EN is active-high count enable, Q3 = MSB, Q0 = LSB



LOAD = 0, CLR = 1, EN = 1

→ counter clears immediately when CLR goes high, CLR is asynchronous & not dependent upon EN

 
→ CLR is active-high, CLR has higher priority than EN (counting)



LOAD = 1, CLR = 0, EN = 0

→ counter loads D[3..0] when LOAD goes high, LOAD is synchronous & overrides counting

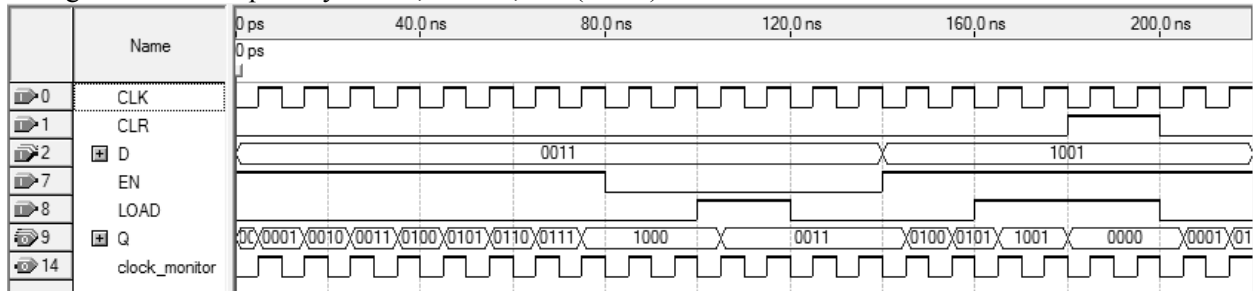→ highest to lowest priority: CLR, LOAD, EN (count)




## 11.2 Binary counter signal frequencies

signal	Clock	Q0	Q1	Q2	Q3
frequency	16kHz	8kHz	4kHz	2kHz	1kHz


$$\text{freq}_{Q3} = \frac{1}{2} \text{freq}_{Q2} = \frac{1}{2} \text{freq}_{Q1} = \frac{1}{2} \text{freq}_{Q0} = \frac{1}{2} \text{freq}_{\text{Clock}}$$
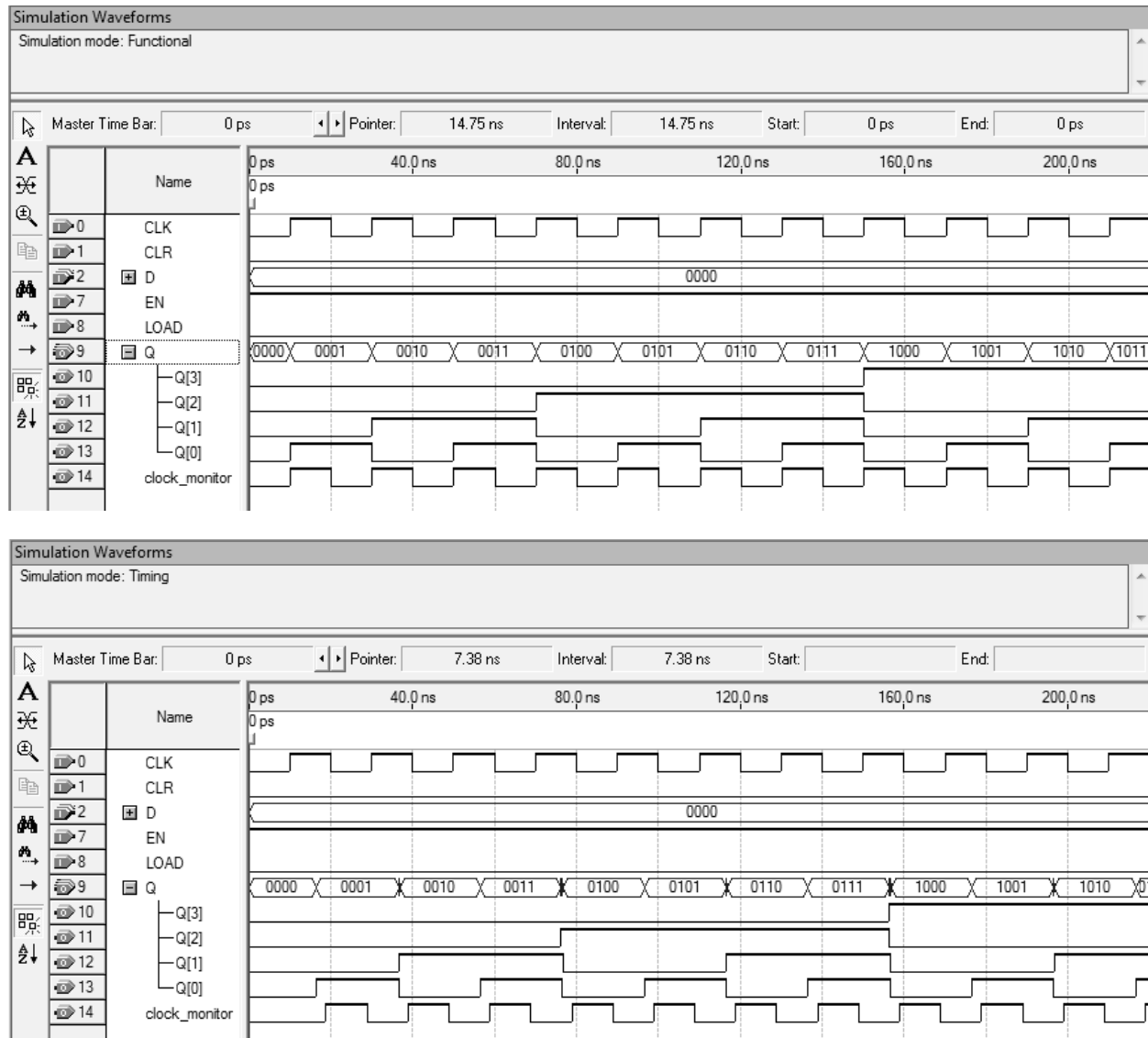
### 11.3 Functional vs. timing simulation








## 11.4 Mod-12 counters

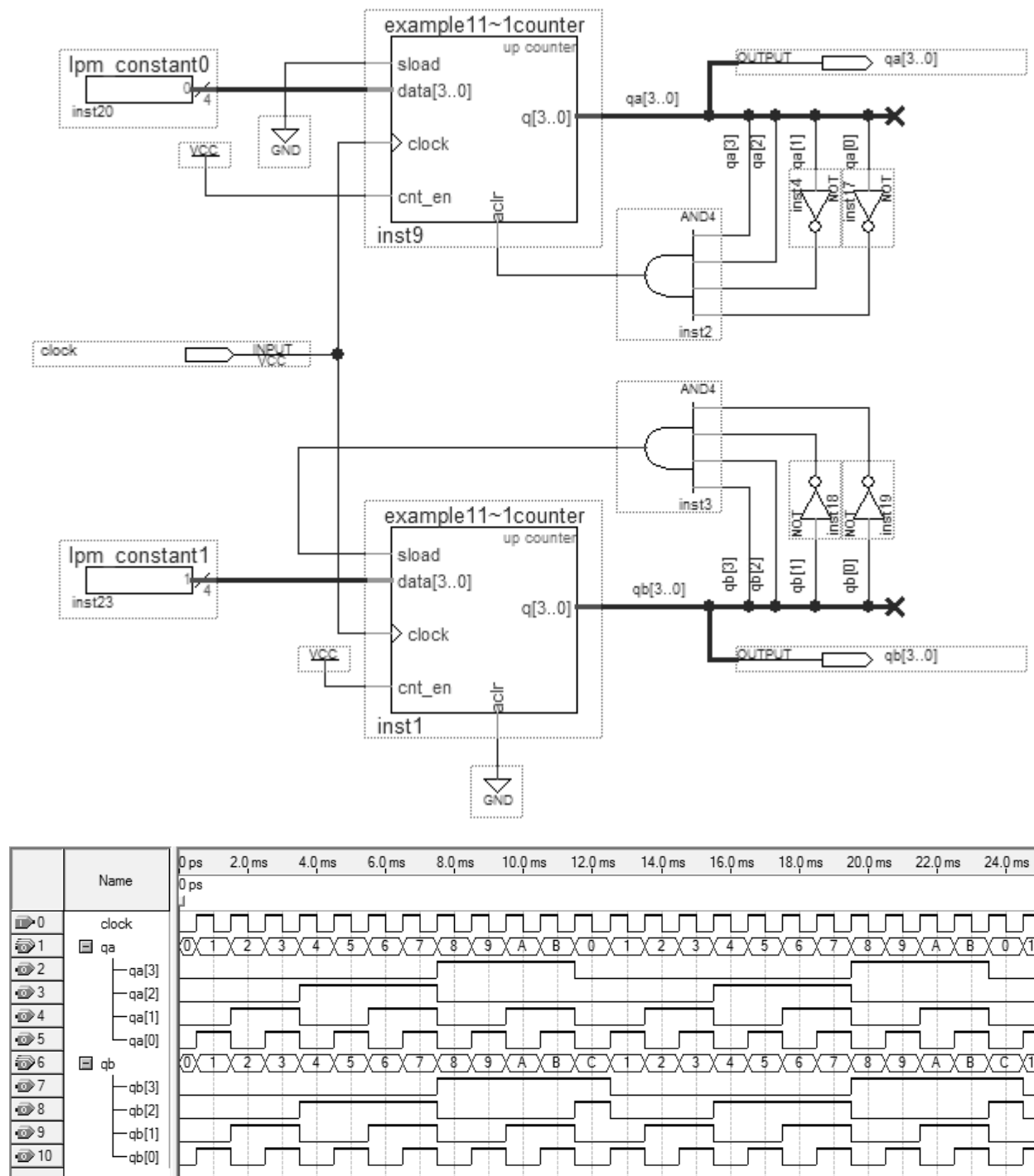


Decode 1100 ( $12_{10}$ ) on each counter. Data input for counter B is 0001.  
 Counter A counts sequence 0000 to 1011 due to asynchronous CLR.  
 Counter B counts sequence 0001 to 1100 due to synchronous LOAD.  
 To produce same count sequence for counter B, need to decode 1011 ( $11_{10}$ ) & LOAD 0000.

## 11.5 Self-stopping counter

  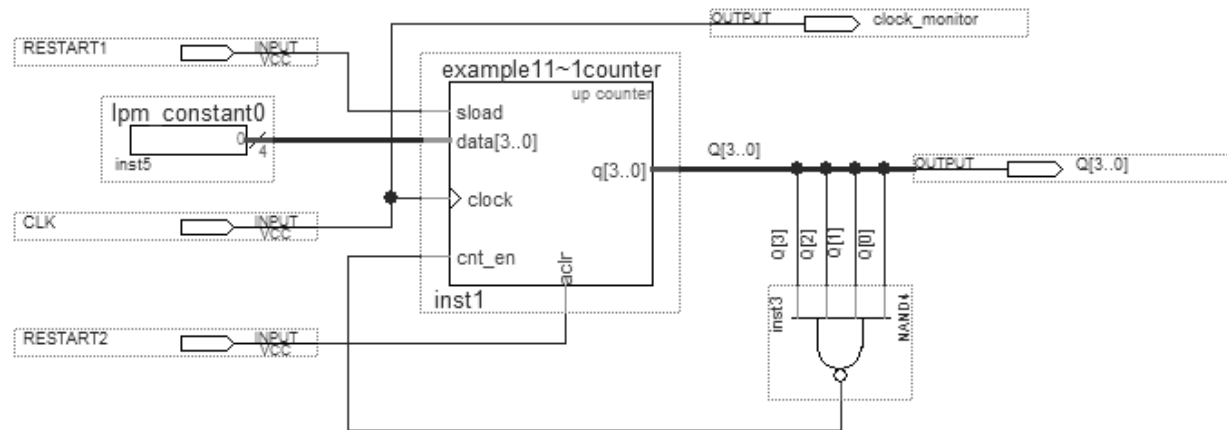


## 11.6 Mod-10 up/down counter

 


Active-high count enable. UP\_DN = 0 counts down, UP\_DN = 1 counts up. TS = 1 when counter reaches terminal state (9 when counting up & 0 when counting down). ENABLE also controls TS output.

## 11.7 Mod-10 timing diagram

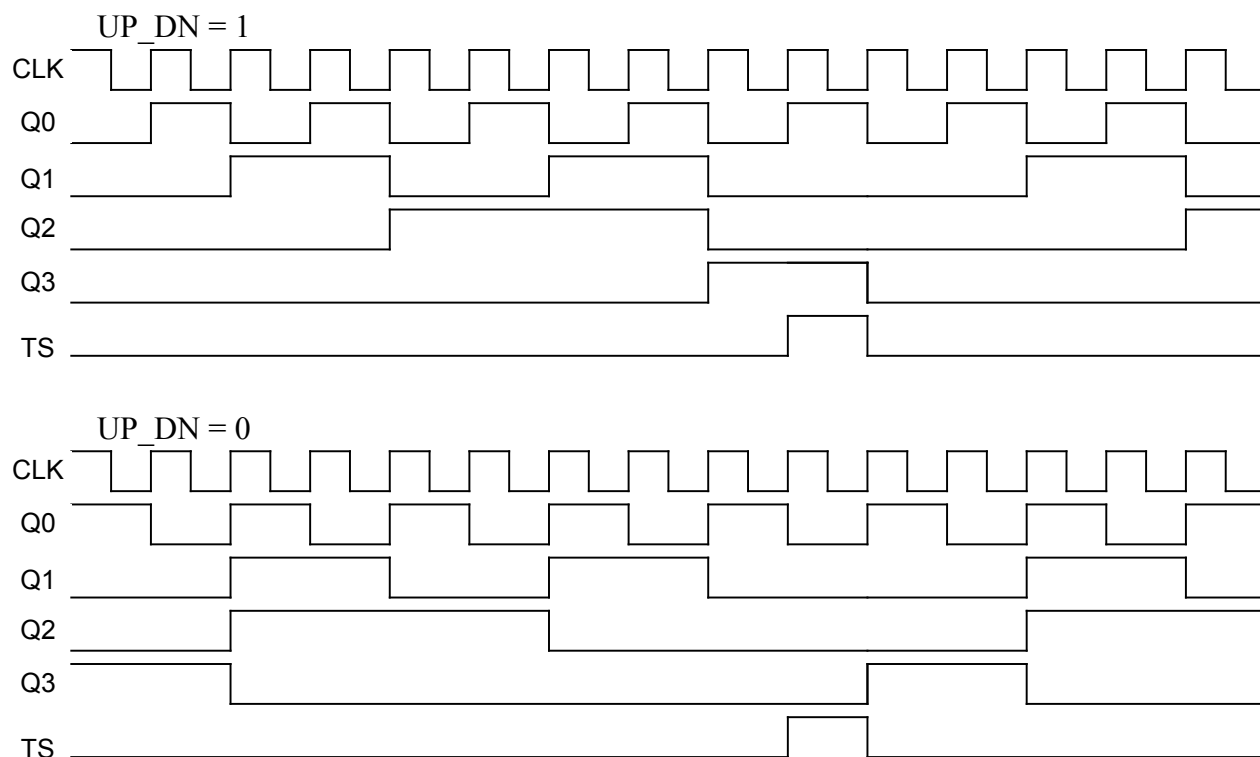

## 11.8 Comparing counters

 

Cntr\_a: count sequence is 0001 to 1100 (mod-12), terminal state is 1100 ( $12_{10}$ )




Cntr\_b: count sequence is 0000 to 1011 (mod-12), terminal state is 1011 ( $11_{10}$ )

Same modulus for each counter, no transient states present

Cout detects the terminal state for cntr\_a

Sset is a synchronous set control that will load the specified value ( $1_{10}$ ) when enabled

## 11.9 Counter waveforms

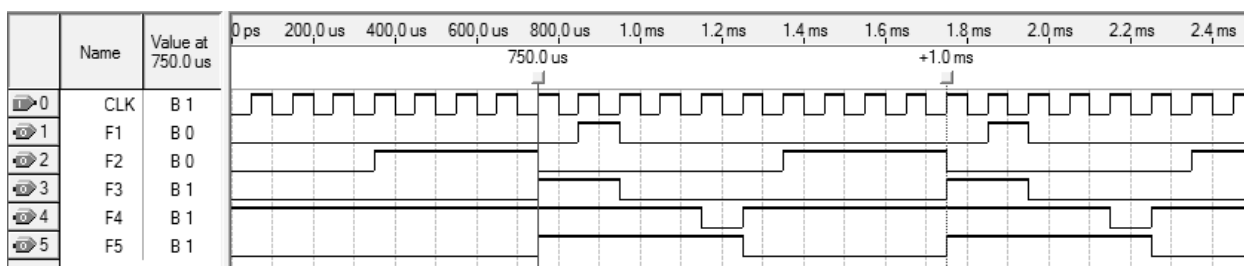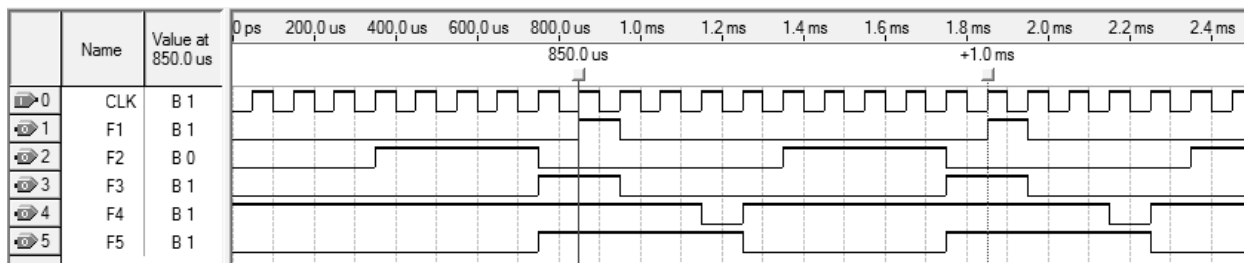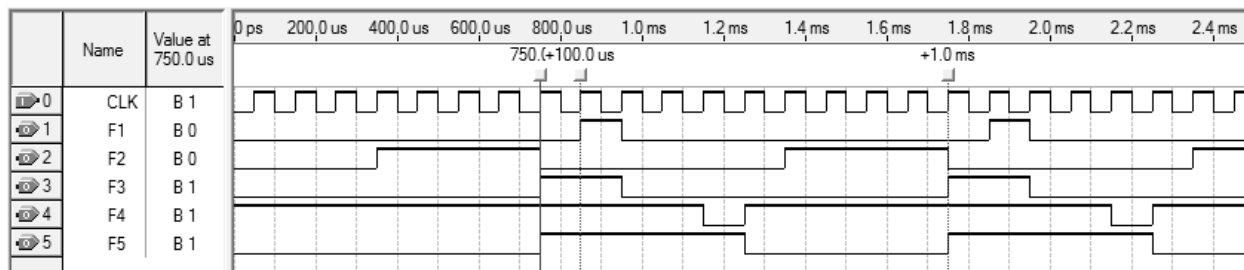

Each output has the same frequency (1kHz).

Both counters are mod-10 counters.


Duty cycles for each output is different due to signal used.

Output signals also have different phases (i.e., pulse occurs at different times).



Signal	F1	F2	F3	F4	F5
Duty Cycle	10%	40%	20%	90%	50%

## Unit 12 Applications Using Maxplus2 Counters


### 12.1 Mod-13 count sequence

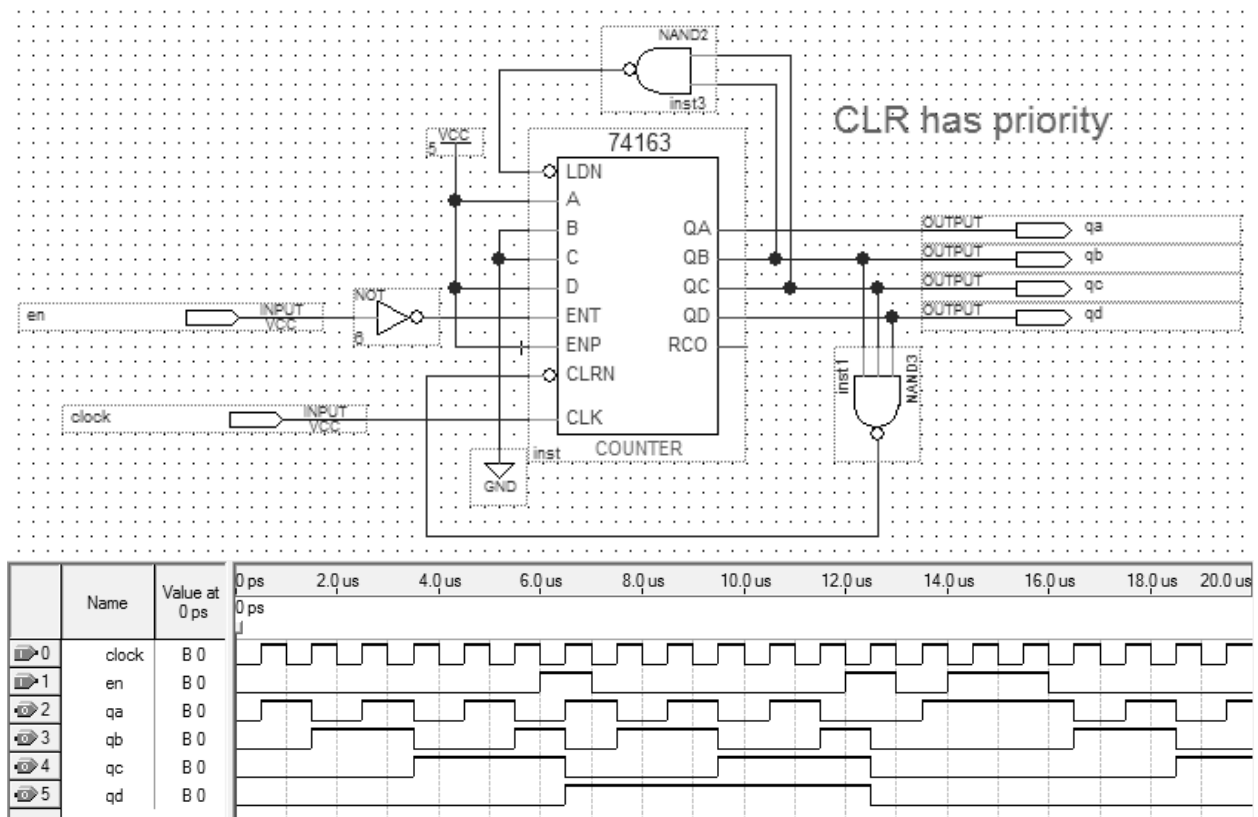


## 12.2 Frequency divider circuit

 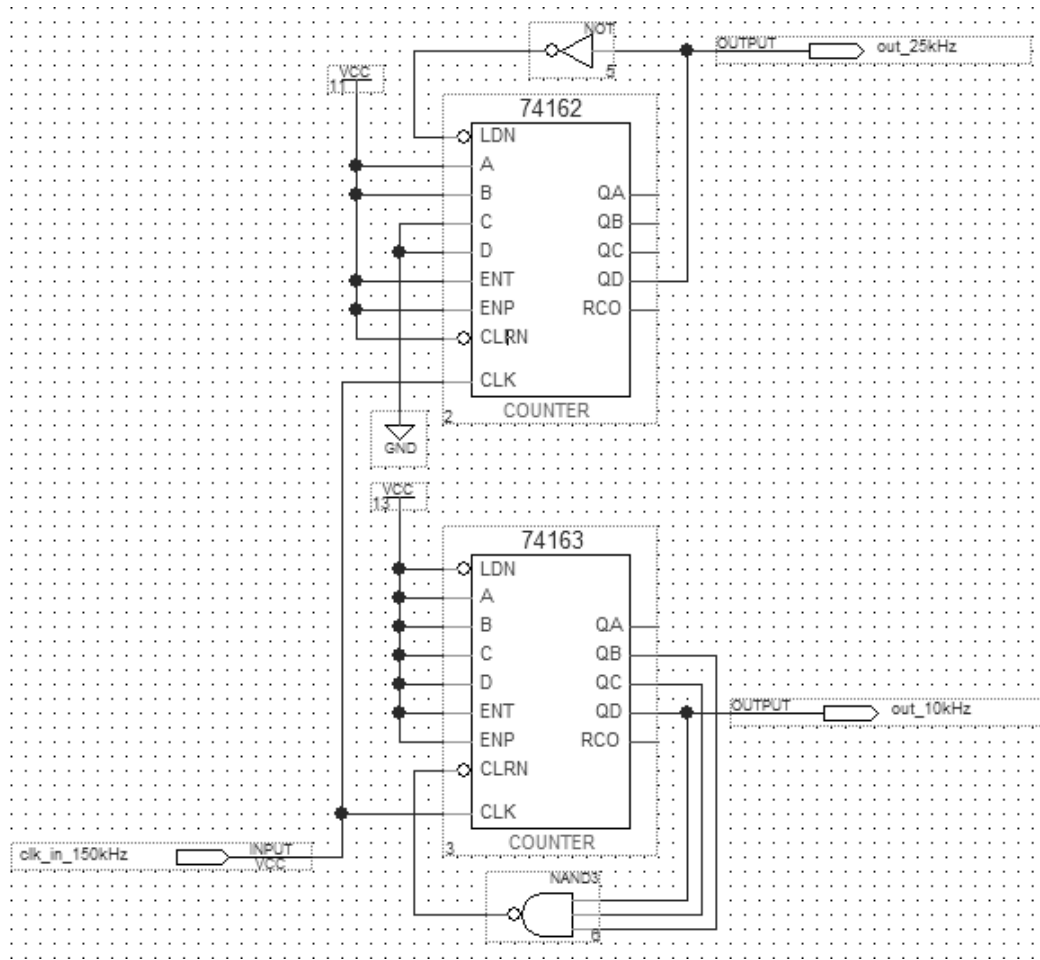


### 12.3 Mod-200 binary counter


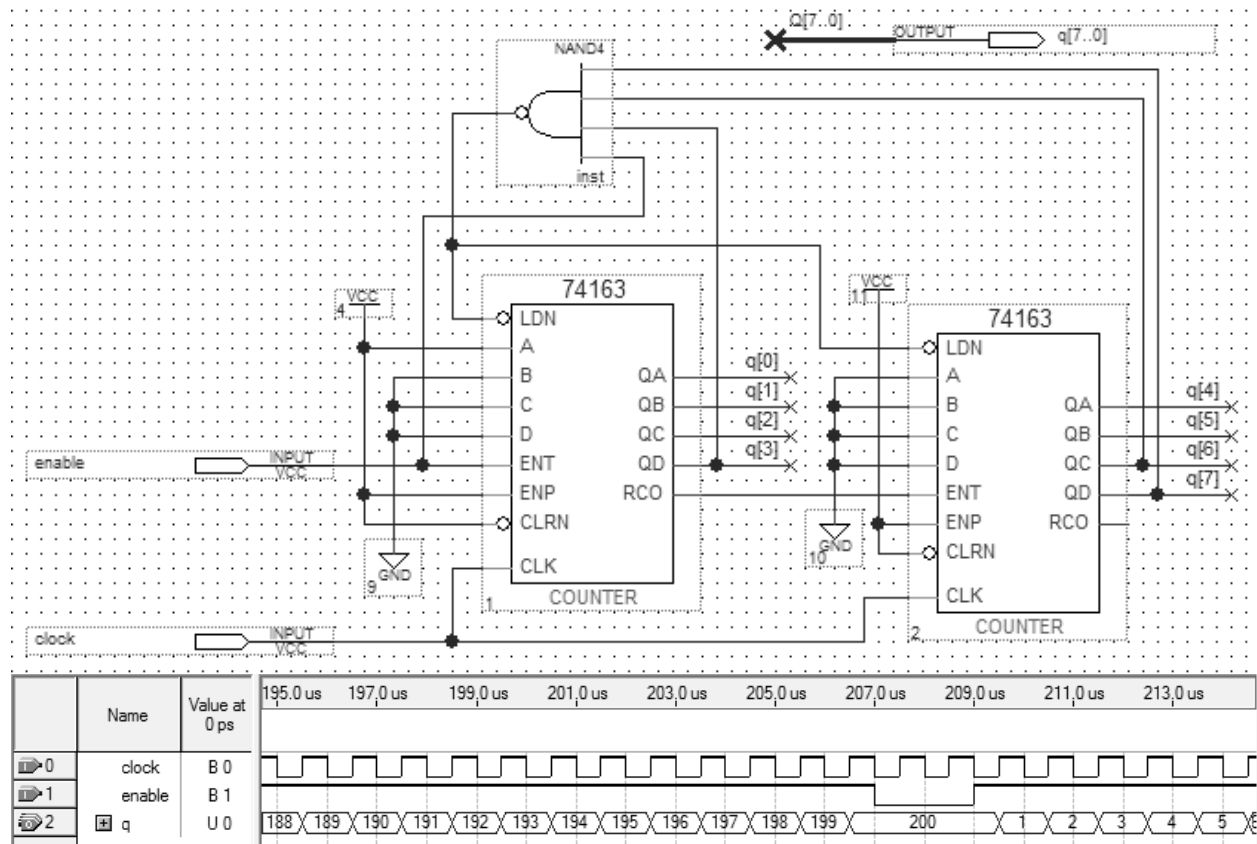

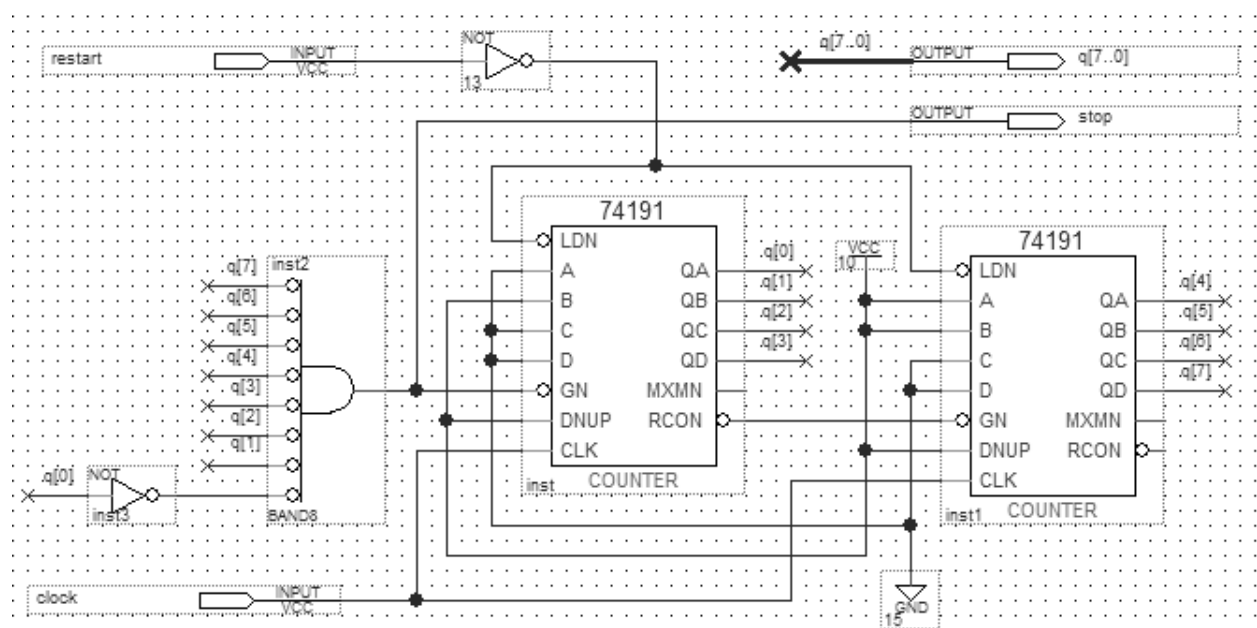
### 12.4 Mod-50, self-stopping, down-counter





 


## 12.5 Waveform generator circuits

 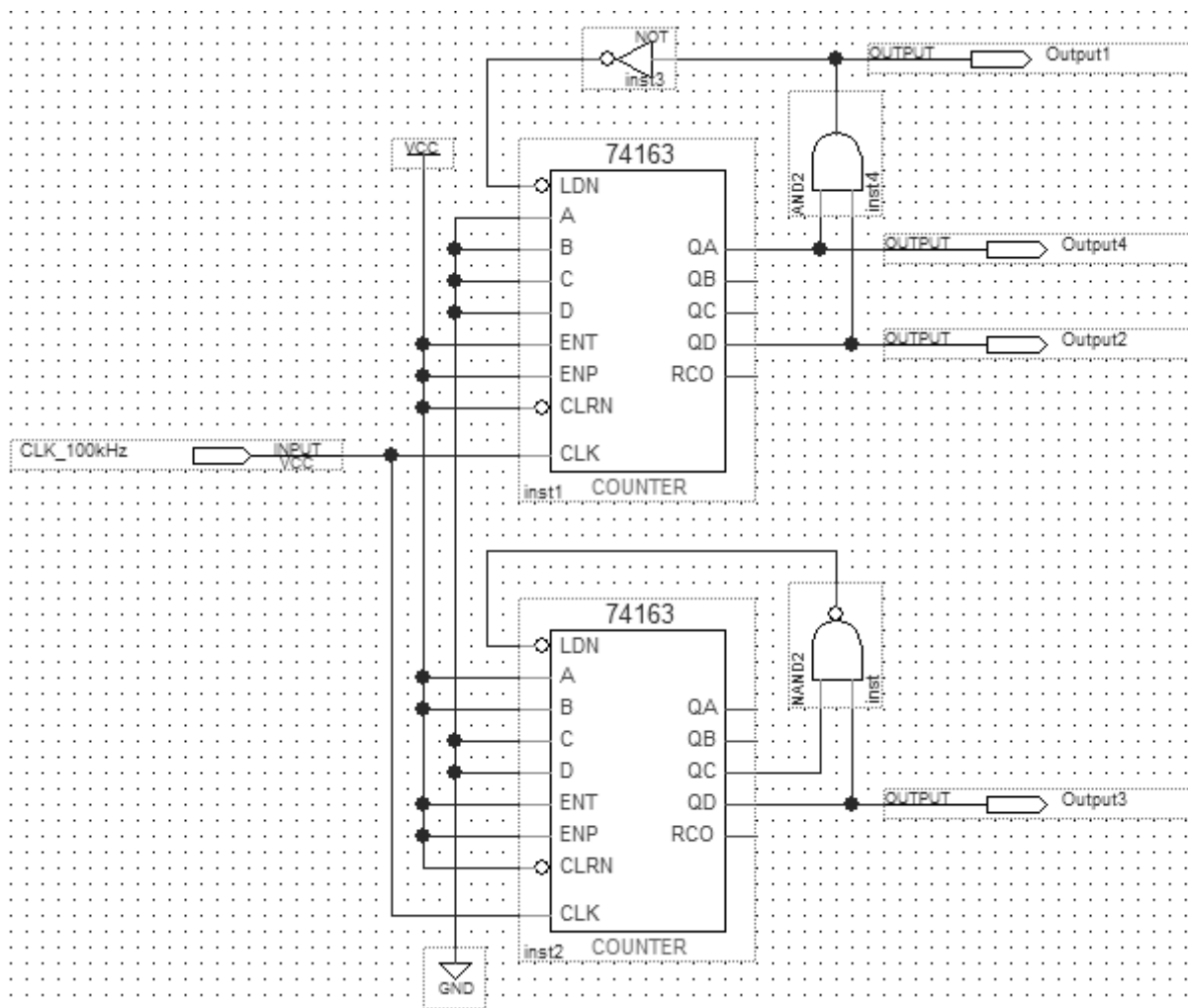





## 12.6 Mod-100 BCD counter

  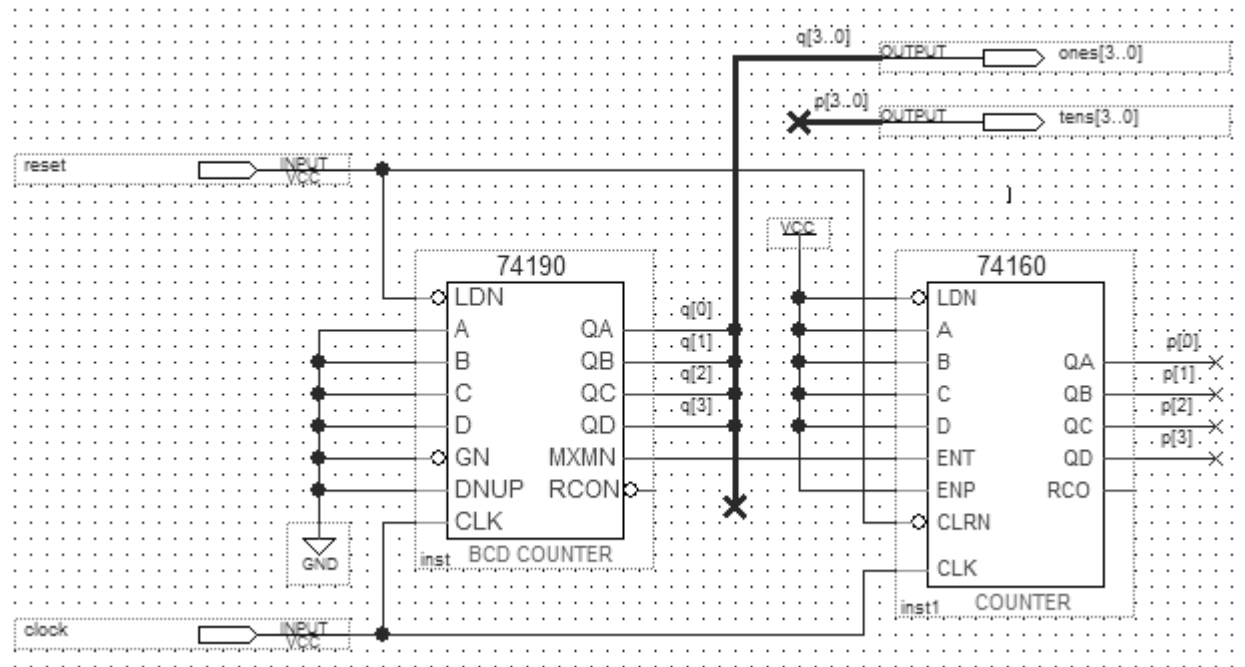



74162 has a synchronous clear, but design requires an asynchronous “reset”

## Unit 13 Applications using LPM Counter Megafunctions


### 13.1 Mod-256 binary down-counter

  


### 13.2 Mod-200 binary counter

 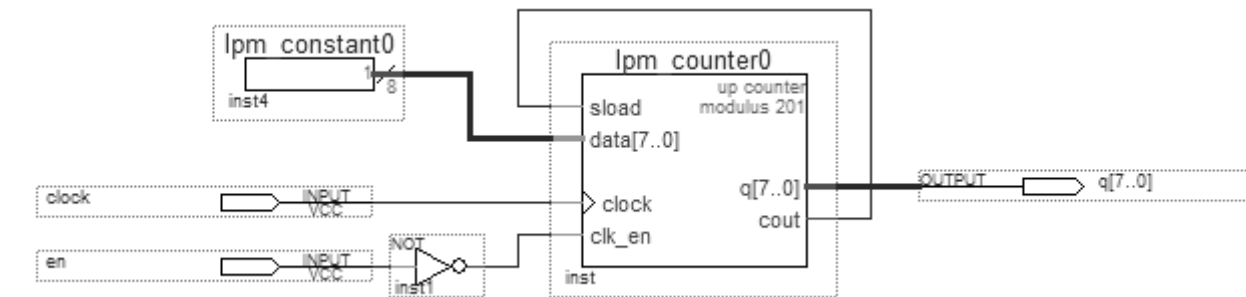


### 13.3 Self-stopping binary counter



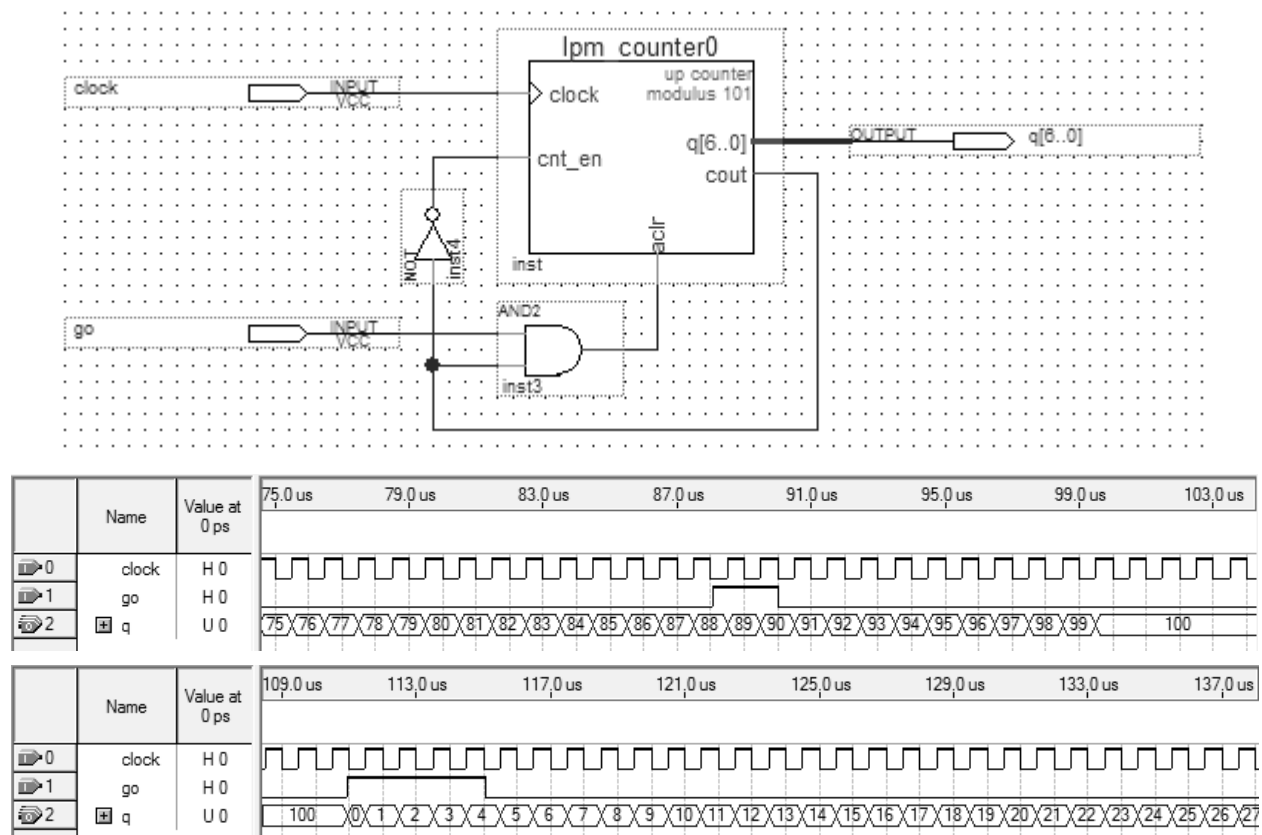


### 13.4 Automatic up/down counter


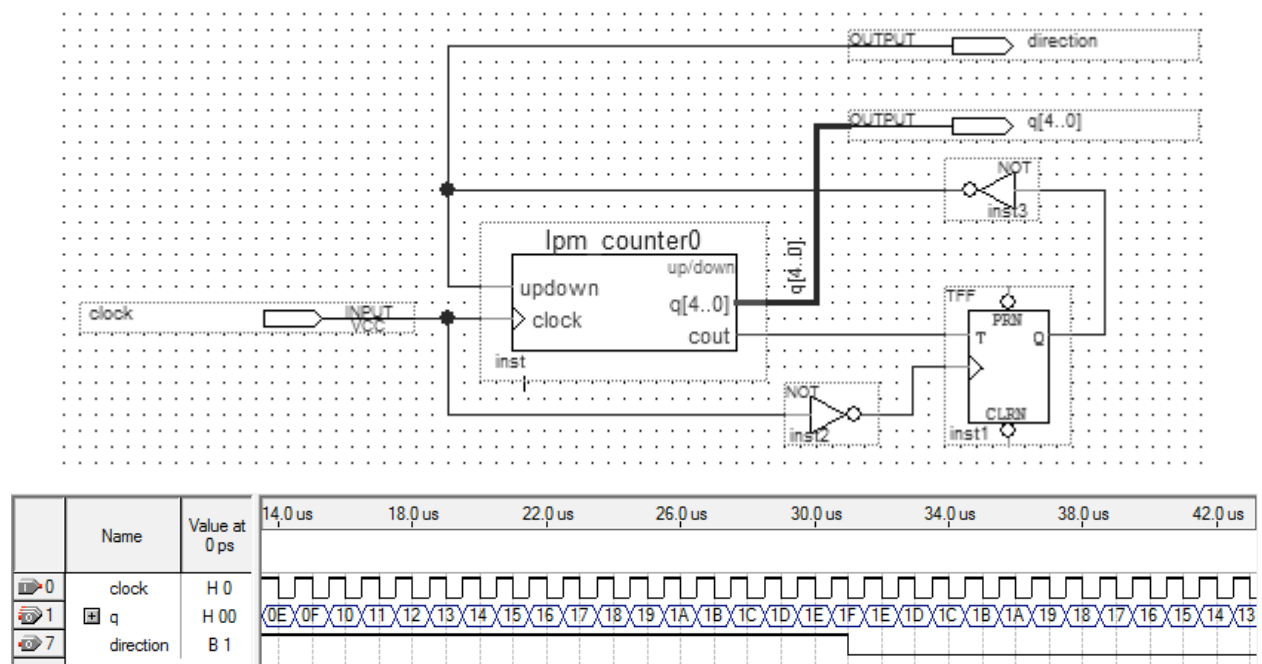


 



### 13.5 Mod-100, up/down, BCD counter

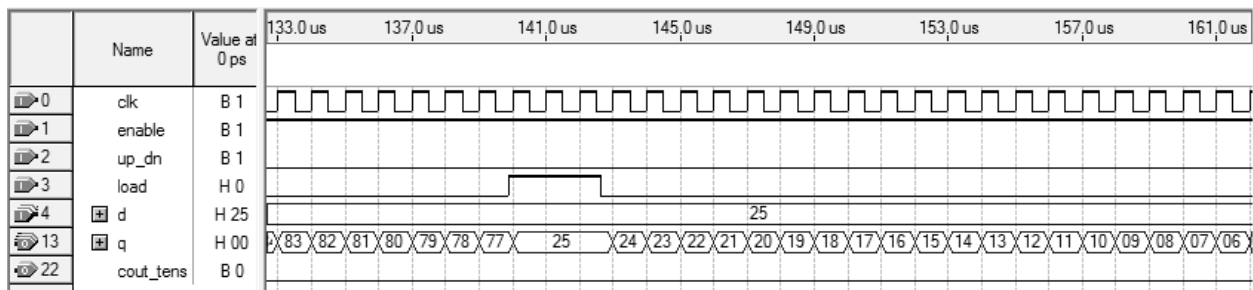 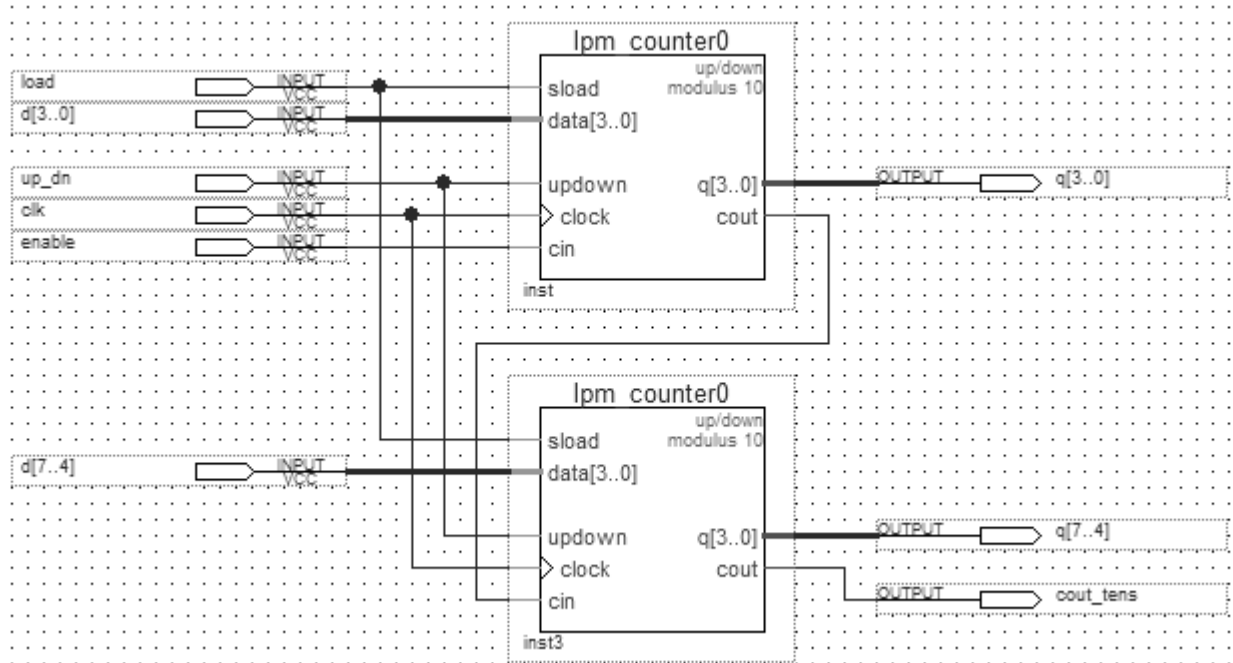


### 13.6 Mod-50 BCD counter

 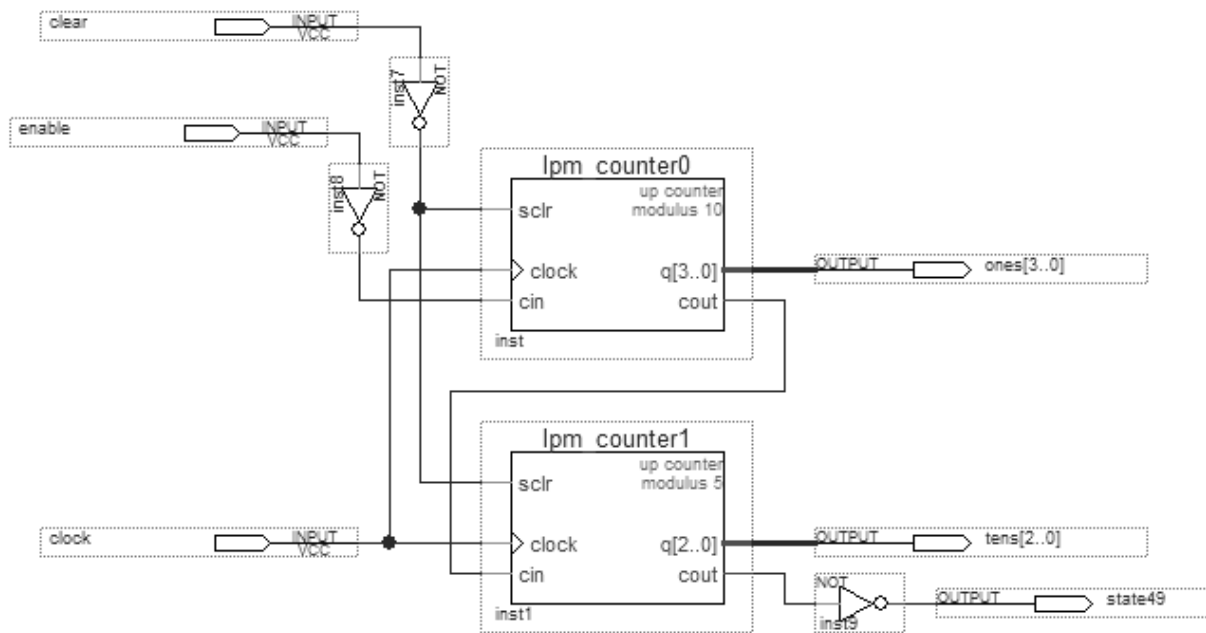

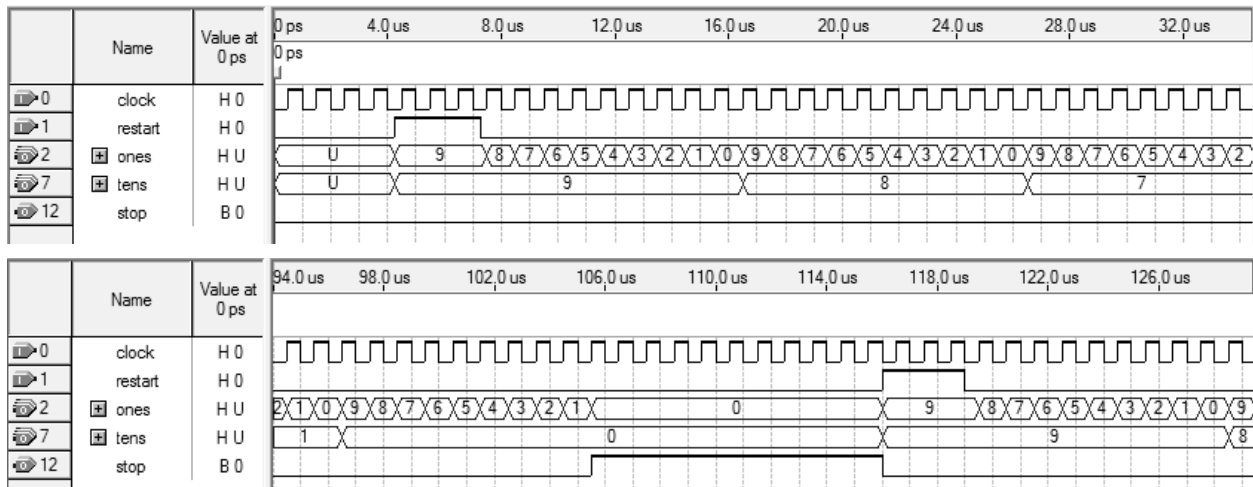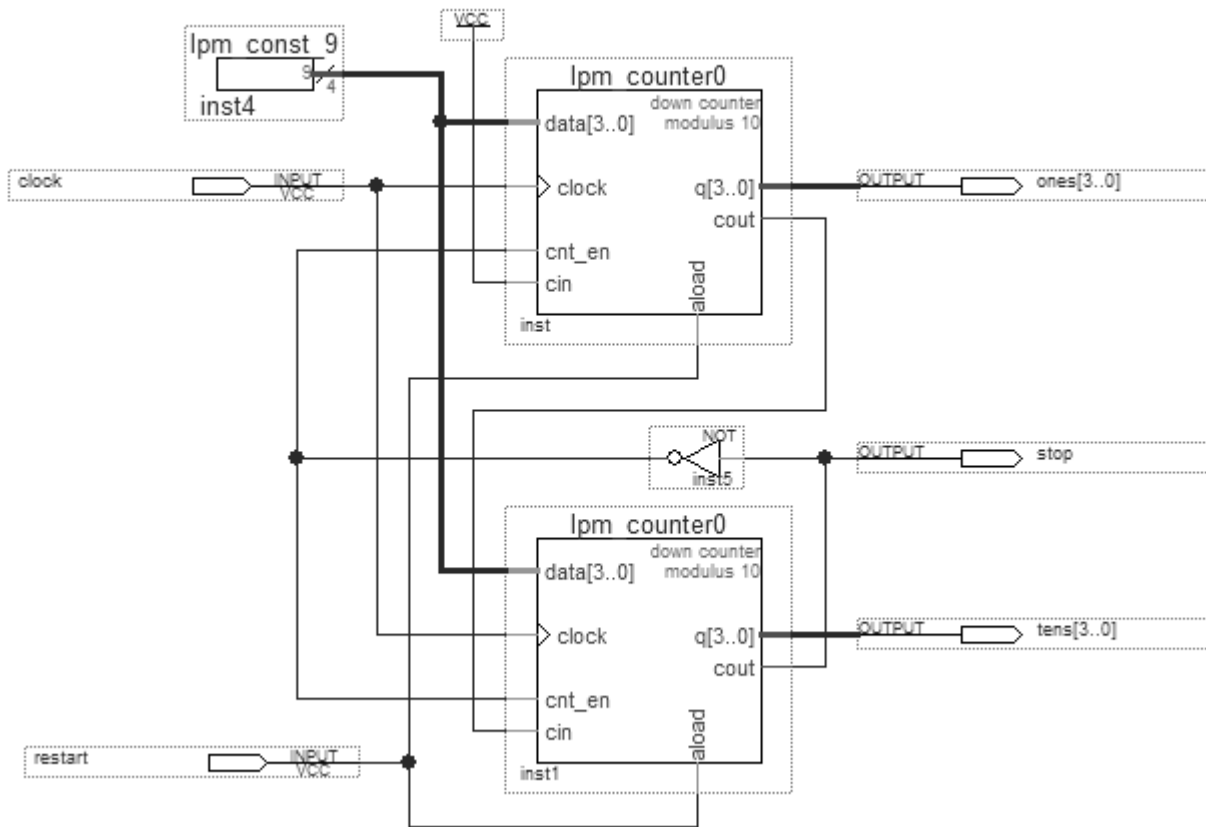
### 13.7 Mod-100, self-stopping, BCD down-counter






### 13.8 Clock frequency divider

 


### 13.9 Frequency divider

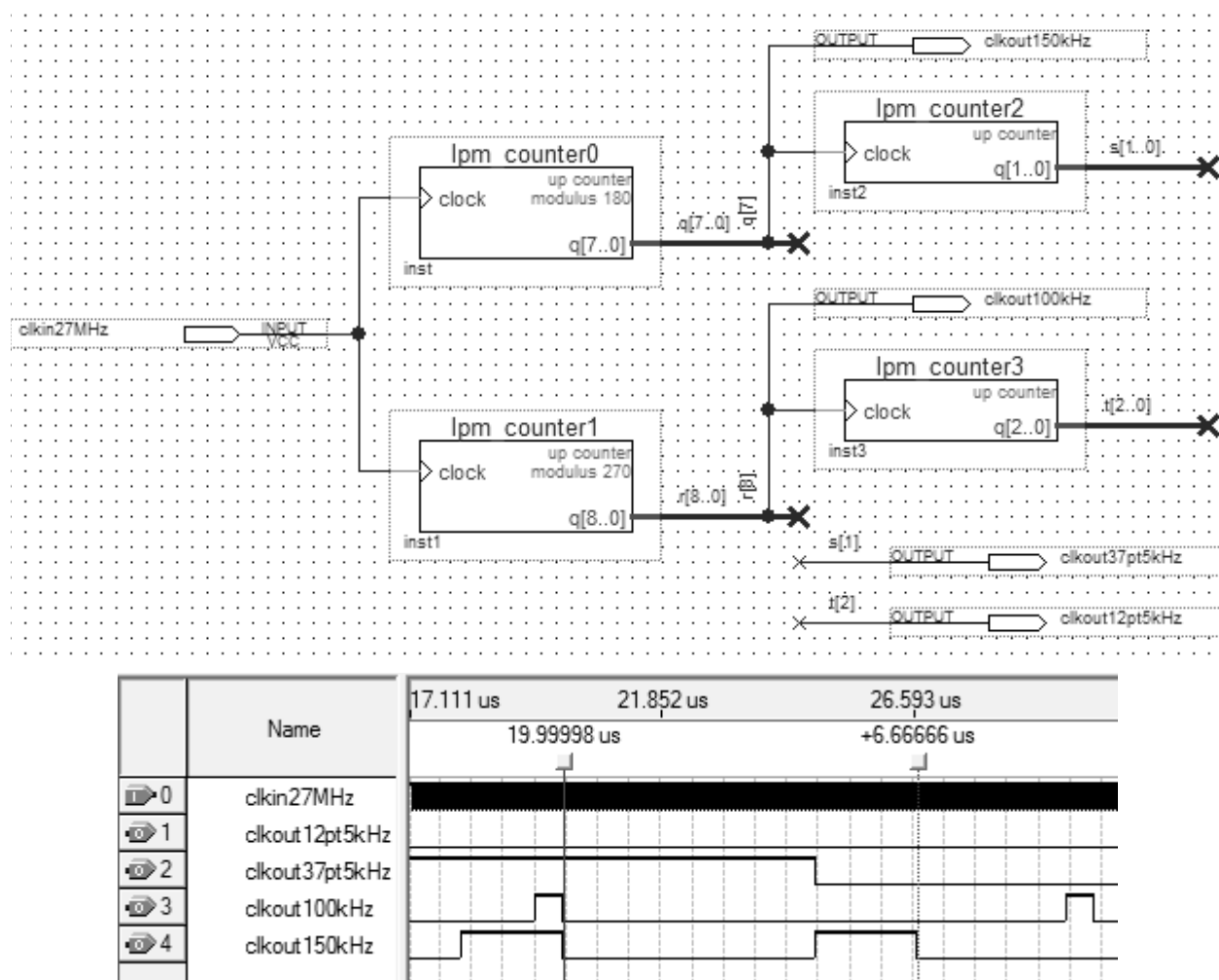

   



### 13.10 One-shot counter

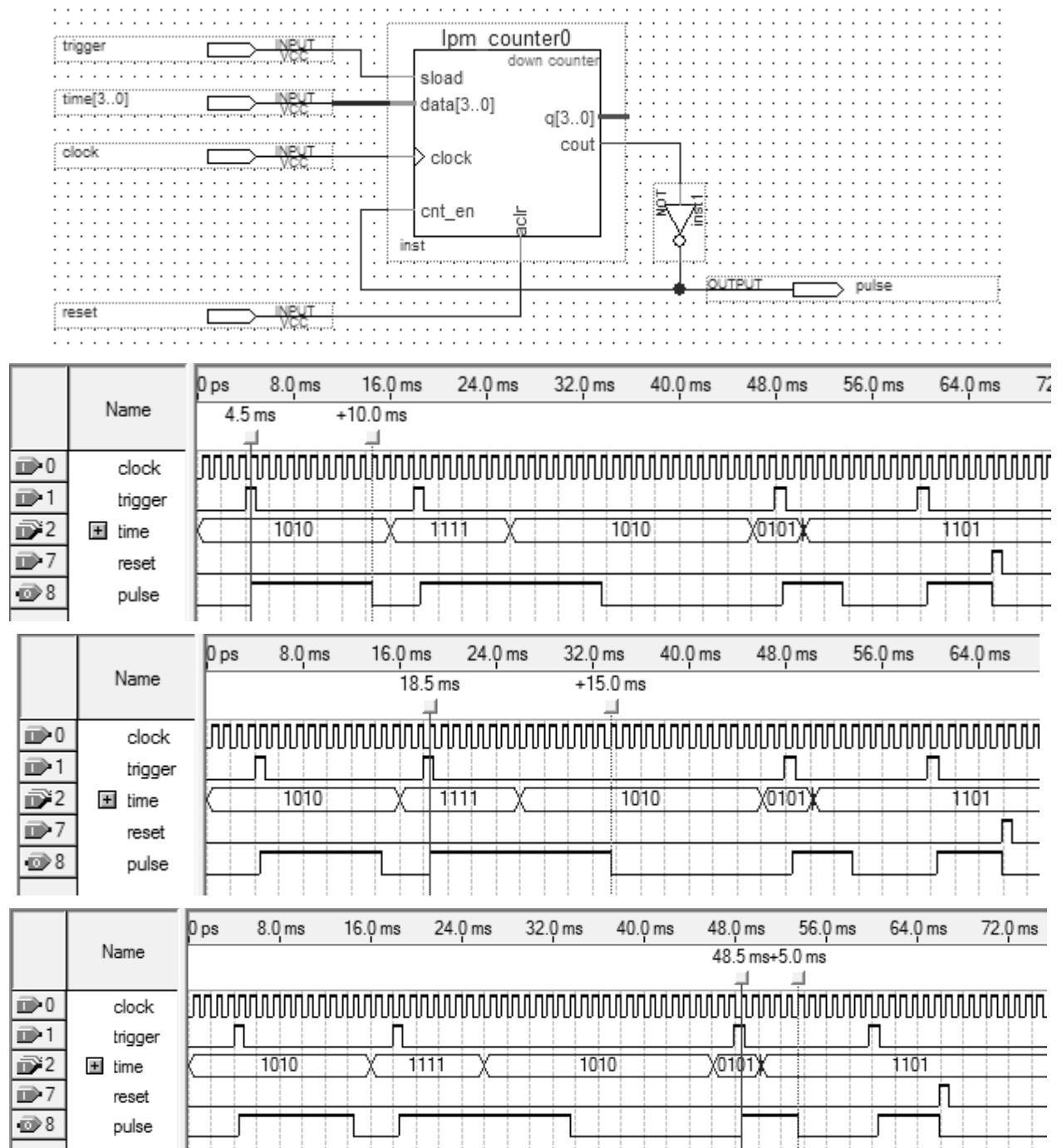

Using a 1-kHz clock, this circuit will produce output pulses from 1 ms to 15 ms wide.

## Unit 14A Counter Designs using AHDL




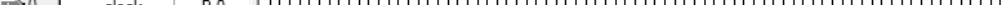

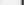
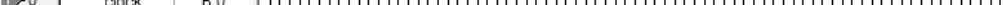

 
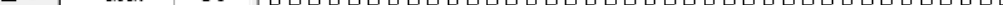
### 14A.1 Binary down counter

```
SUBDESIGN mod16dwn
(
    clock, ld, en, data[3..0]      :INPUT;
    q[3..0], last                  :OUTPUT;
)
VARIABLE
    q[3..0]                        :DFF;
BEGIN
    q[].clk = clock;                -- connect clock

    IF ld == VCC THEN               -- load is highest priority
        q[].d = data[];            -- synchronous load
    ELSIF en == GND THEN            -- active-low count enable
        q[].d = q[].q - 1;         -- count down
    ELSE
        q[].d = q[].q;             -- hold count
    END IF;

    IF q[].q == 0 THEN              -- detect terminal state
        last = VCC;                -- active-high output
    ELSE
        last = GND;               -- if not the last state
    END IF;
END;
```

### 14A.3 Mod-60 BCD counter

	Name	Value at 0 ps	33.0 us	37.0 us	41.0 us	45.0 us	49.0 us	53.0 us	57.0 us	61.0 us	65.0 us	69.0 us	73.0 us	77.0 us	81.0 us	
	clock	B 0														
	resn	B 1														
	 ones	U 0														
	 tens	U 0														

```

SUBDESIGN  mod10
(
    clock, resn          :INPUT;
    q[3..0], rco         :OUTPUT;
)
VARIABLE
    q[3..0]              :DFF;      -- 4 FFs
BEGIN
    DEFAULTS
        rco = GND;          -- inactive output
    END DEFAULTS;

    q[].clk = clock;

    IF !resn THEN           -- active-low reset
        q[].d = 0;
    ELSIF q[].q == 9 THEN    -- at terminal state?
        q[].d = B"0000";    -- recycle
        rco = VCC;          -- assert rco
    ELSE
        q[].d = q[].q + 1;   -- increment count
    END IF;
END;

```

```

SUBDESIGN  mod6
(
    clock, resn, en      :INPUT;
    q[2..0]              :OUTPUT;
)
VARIABLE
    q[2..0]              :DFF;      -- 3 FFs
BEGIN
    q[].clk = clock;

    IF !resn THEN          -- active-low reset
        q[].d = 0;
    ELSIF en THEN          -- increment tens digit
        IF q[].q == 5 THEN  -- at terminal state?
            q[].d = B"000"; -- recycle
        ELSE
            q[].d = q[].q + 1; -- increment count
        END IF;
    ELSE
        q[].d = q[].q;      -- hold current state
    END IF;
END;

```

#### 14A.4 Mod-100 binary counter

```
SUBDESIGN  mod100
(
    clock, enable, w      :INPUT;
    q[7..0], pulse        :OUTPUT;
)
VARIABLE
    q[7..0]                :DFF;        -- 8 FFs
BEGIN
    q[].clk = !clock;        -- clock on NGT

    IF  enable  THEN        -- count enabled?
        IF  q[].q == 99  THEN -- at terminal state?
            q[].d = 0;       -- recycle
        ELSE
            q[].d = q[].q + 1; -- increment count
        END IF;
    ELSE
        q[].d = q[].q;       -- hold count
    END IF;

    -- control pulse width of output
    IF  !w & q[].q >= 95  THEN pulse = VCC;
    ELSIF  w & q[].q >= 90  THEN pulse = VCC;
    ELSE  pulse = GND;
    END IF;
END;
```

## 14A.5 Stepper motor sequence controller

```

SUBDESIGN 'half-step'
(
    step, cw, go          :INPUT;
    q[3..0]               :OUTPUT;
)

VARIABLE
    stepper: MACHINE OF BITS (q[3..0])  -- state machine
        WITH STATES (  -- define stepper states
            initial = B"0000",
            s1 = B"0101",
            s2 = B"0001",
            s3 = B"1001",
            s4 = B"1000",
            s5 = B"1010",
            s6 = B"0010",
            s7 = B"0110",
            s8 = B"0100");

BEGIN

    stepper.clk = step;          -- clock port
    stepper.ena = go;            -- active-high enable port

    TABLE  -- present state/next state table
        stepper,      cw      =>      stepper;
        initial,      X      =>      s1;
        s1,           1      =>      s2;
        s1,           0      =>      s8;
        s2,           1      =>      s3;
        s2,           0      =>      s1;
        s3,           1      =>      s4;
        s3,           0      =>      s2;
        s4,           1      =>      s5;
        s4,           0      =>      s3;
        s5,           1      =>      s6;
        s5,           0      =>      s4;
        s6,           1      =>      s7;
        s6,           0      =>      s5;
        s7,           1      =>      s8;
        s7,           0      =>      s6;
        s8,           1      =>      s1;
        s8,           0      =>      s7;
    END TABLE;
END;

```

## 14A.6 Variable frequency divider

```
SUBDESIGN divider
(
    freq_in, m[1..0]                                :INPUT;
    freq_out                                           :OUTPUT;
)
VARIABLE
    count[4..0]                                       :DFF;
BEGIN
    count[].clk = freq_in;


    CASE m[] IS
        WHEN 0 =>
            freq_out = count[2];
            IF count[] == 4 THEN -- terminal state?
                count[].d = 0; -- recycle
            ELSE
                count[].d = count[].q + 1; -- count up
            END IF;
        WHEN 1 =>
            freq_out = count[3];
            IF count[] == 9 THEN -- terminal state?
                count[].d = 0; -- recycle
            ELSE
                count[].d = count[].q + 1; -- count up
            END IF;
        WHEN 2 =>
            freq_out = count[4];
            IF count[] == 19 THEN -- terminal state?
                count[].d = 0; -- recycle
            ELSE
                count[].d = count[].q + 1; -- count up
            END IF;
        WHEN 3 =>
            freq_out = count[4];
            IF count[] == 24 THEN -- terminal state?
                count[].d = 0; -- recycle
            ELSE
                count[].d = count[].q + 1; -- count up
            END IF;
    END CASE;
END;
```

## 14A.7 Digital lock

```

CONSTANT comb1 = H"7";
CONSTANT comb2 = H"F";
CONSTANT comb3 = H"A";
CONSTANT comb4 = H"2";
        -- define desired lock combination
SUBDESIGN lock
(enter          :INPUT;
 data[3..0]     :INPUT;
 unlock, ready  :OUTPUT;)
VARIABLE
    sm          :MACHINE
        WITH STATES (start, state1, state2, state3, done);
BEGIN
    DEFAULTS
        unlock = GND;
        ready  = GND;
    END DEFAULTS;
    sm.clk = enter;
    CASE sm IS
        WHEN start =>          -- beginning state
            ready = VCC;        -- ready to enter code
            IF data[] == comb1 THEN sm = state1;
            ELSE sm = start;
            END IF;
        WHEN state1 =>          -- 1st number ok
            IF data[] == comb2 THEN sm = state2;
            ELSE sm = start;    -- wrong number
            END IF;
        WHEN state2 =>          -- 2nd number ok
            IF data[] == comb3 THEN sm = state3;
            ELSE sm = start;
            END IF;
        WHEN state3 =>          -- 3rd number ok
            IF data[] == comb4 THEN sm = done;
            ELSE sm = start;
            END IF;
        WHEN done=>             -- 4th number ok
            sm = start;         -- relock when press enter
            unlock = VCC;       -- unlock
    END CASE;
END;

```

 



#### 14A.8 Programmable frequency divider

```
SUBDESIGN divide_by
(
    freq_in, b[7..0]      :INPUT;
    freq_out              :OUTPUT;
)

VARIABLE
    divide_by[7..0]      :DFF;      -- 8 FFs

BEGIN
    divide_by[].clk = freq_in;

    IF divide_by[] <= 1 THEN          -- detect last state
        divide_by[].d = b[];         -- reload number
        freq_out = VCC;              -- make pulse
    ELSE divide_by[].d = divide_by[].q - 1; -- decr.
    END IF;

END;
```

## 14A.9 State machine

```

SUBDESIGN state
(
    clock, r, s, t      :INPUT;
    q[2..0]             :OUTPUT;
)

VARIABLE
    sm      :MACHINE OF BITS (q[2..0])
            WITH STATES (s0 = B"000",
                        s1 = B"001",
                        s2 = B"010",
                        s3 = B"011",
                        s4 = B"100",
                        s5 = B"101",
                        s6 = B"110",
                        s7 = B"111");

BEGIN
    sm.clk = clock;

    TABLE      -- present state/next state table
        sm, r, s, t      =>      sm;
        s0, X, X, X      =>      s1;
        s1, X, X, X      =>      s7;
        s2, X, X, X      =>      s1;
        s3, 1, X, X      =>      s3;
        s3, 0, 1, X      =>      s4;
        s3, 0, 0, X      =>      s7;
        s5, X, X, X      =>      s1;
        s4, X, X, X      =>      s3;
        s6, X, X, X      =>      s4;
        s7, X, X, 0      =>      s1;
        s7, X, X, 1      =>      s6;
    END TABLE;

END;

```


## 14A.10 Variable pulse delay

```


SUBDESIGN  varypulsedelay
(
    clock          :INPUT;
    start          :INPUT;
    delay          :INPUT;
    pulse          :OUTPUT;
)
VARIABLE
    mach           :MACHINE      -- "buried" machine
    WITH STATES (
        idle, one, two, three, four, five,
        six, seven, eight, nine, ten);
BEGIN
    DEFAULTS
    pulse = GND;
    END DEFAULTS;
    mach.clk = clock;

    CASE mach IS
        WHEN idle =>      -- mach waits here
            IF start THEN mach = one;
            ELSE          mach = idle;
            END IF;
        WHEN one =>       mach = two;
        WHEN two =>       mach = three;
        WHEN three =>     mach = four;
        WHEN four =>     mach = five;
        WHEN five =>
            IF delay == GND THEN
                mach = idle;
                pulse = VCC;
            ELSE
                mach = six;
            END IF;
        WHEN six =>       mach = seven;
        WHEN seven =>     mach = eight;
        WHEN eight =>     mach = nine;
        WHEN nine =>     mach = ten;
        WHEN ten =>
            IF delay == VCC THEN
                pulse = VCC;
            END IF;
    END CASE;
END;

```

 

## 14A.11 Frequency divider

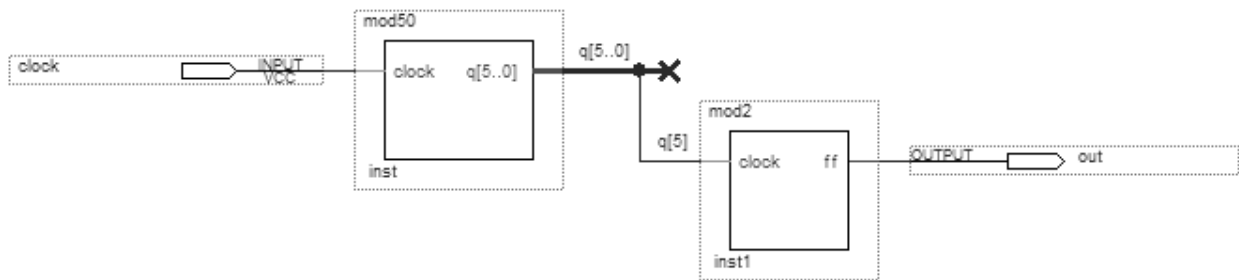

```
SUBDESIGN mod50
(
    clock          :INPUT;
    q[5..0]        :OUTPUT;
)
VARIABLE
    q[5..0]        :DFF;
BEGIN
    q[].clk = clock;

    IF q[] == 49    THEN
        q[].d = 0;
    ELSE
        q[].d = q[].q + 1;
    END IF;
END;
```

```
SUBDESIGN mod2
(
    clock          :INPUT;
    ff             :OUTPUT;
)
VARIABLE
    ff             :DFF;
BEGIN
    ff.clk = clock;

    ff.d = !ff.q;
END;
```

### 14A.12 Clock frequency divider

```
SUBDESIGN  clock_divider
(
    clock_50MHz           :INPUT;
    out_25kHz, out_10kHz  :OUTPUT;
)
VARIABLE
    q_25kHz[10..0], q_10kHz[12..0]  :DFF;
BEGIN
    q_25kHz[].clk = clock_50MHz;
    q_10kHz[].clk = clock_50MHz;

    out_25kHz = q_25kHz[10].q; -- only need MSB
    out_10kHz = q_10kHz[12].q; -- from 2 counters

    IF    q_25kHz[].q == 1999    THEN -- mod 2000
        q_25kHz[].d = 0;
    ELSE
        q_25kHz[].d = q_25kHz[].q + 1;
    END IF;

    IF    q_10kHz[].q == 4999 THEN -- mod 5000
        q_10kHz[].d = 0;
    ELSE
        q_10kHz[].d = q_10kHz[].q + 1;
    END IF;

END;
```

### 14A.13 Gray code counter

```
SUBDESIGN  gray
(
    clock, dir           :INPUT;
    q[3..0], index       :OUTPUT;
)
VARIABLE
    gray:  MACHINE OF BITS (q[3..0])  -- state machine
           WITH STATES (              -- gray code bit patterns
               s0 = B"0000",
               s1 = B"0001",
               s2 = B"0011",
               s3 = B"0010",
               s4 = B"0110",
               s5 = B"0111",
               s6 = B"0101",
               s7 = B"0100",
               s8 = B"1100",
```

```

        s9  = B"1101",
        s10 = B"1111",
        s11 = B"1110",
        s12 = B"1010",
        s13 = B"1011",
        s14 = B"1001",
        s15 = B"1000");

BEGIN
    gray.clk = clock;                -- state machine clock

    TABLE                          -- present state/next state table
        gray,                      dir      =>      gray,      index;
        s0,                        0        =>      s1,        0;
        s0,                        1        =>      s15,       0;
        s1,                        0        =>      s2,        1;
        s1,                        1        =>      s0,        1;
        s2,                        0        =>      s3,        1;
        s2,                        1        =>      s1,        1;
        s3,                        0        =>      s4,        1;
        s3,                        1        =>      s2,        1;
        s4,                        0        =>      s5,        1;
        s4,                        1        =>      s3,        1;
        s5,                        0        =>      s6,        1;
        s5,                        1        =>      s4,        1;
        s6,                        0        =>      s7,        1;
        s6,                        1        =>      s5,        1;
        s7,                        0        =>      s8,        1;
        s7,                        1        =>      s6,        1;
        s8,                        0        =>      s9,        1;
        s8,                        1        =>      s7,        1;
        s9,                        0        =>      s10,       1;
        s9,                        1        =>      s8,        1;
        s10,                       0        =>      s11,       1;
        s10,                       1        =>      s9,        1;
        s11,                       0        =>      s12,       1;
        s11,                       1        =>      s10,       1;
        s12,                       0        =>      s13,       1;
        s12,                       1        =>      s11,       1;
        s13,                       0        =>      s14,       1;
        s13,                       1        =>      s12,       1;
        s14,                       0        =>      s15,       1;
        s14,                       1        =>      s13,       1;
        s15,                       0        =>      s0,        1;
        s15,                       1        =>      s14,       1;
    END TABLE;
END;
```

## Unit 14V Counter Designs using VHDL

### 14V.1 Binary down counter

```
ENTITY mod16dwn IS
PORT( clock, load, en      :IN BIT;
      data                 :IN INTEGER RANGE 0 TO 15;
      q                   :OUT INTEGER RANGE 0 TO 15;
      last                :OUT BIT  );
END mod16dwn;

ARCHITECTURE down_count  OF mod16dwn IS
BEGIN
PROCESS (clock)           -- wait for clock
VARIABLE  counter         :INTEGER RANGE 0 TO 15;
BEGIN
    IF (clock'EVENT AND clock = '1') THEN
        IF load = '1' THEN -- load is highest priority
            counter := data; -- synchronous load
        ELSIF en = '0' THEN -- active-low count enable
            counter := counter - 1; -- count down
        END IF; -- hold is implied
    END IF;
    q <= counter; -- connect to output port
    IF counter = 0 THEN -- detect terminal state
        last <= '1'; -- active-high
    ELSE
        last <= '0';
    END IF;
END PROCESS;
END;
```

## 14V.2 Up/down BCD counter


```
ENTITY updn_mod10 IS
PORT (
    clock          :IN BIT;
    c              :IN BIT_VECTOR (1 DOWNTO 0);
    count          :OUT INTEGER RANGE 0 TO 15;
    carryn         :OUT BIT
);
END updn_mod10;

ARCHITECTURE vhdl OF updn_mod10 IS
BEGIN
    PROCESS (clock, c)          -- clock or control invokes process
    VARIABLE bcd               :INTEGER RANGE 0 TO 9;  -- counter variable
    BEGIN
        IF (clock'EVENT AND clock = '1') THEN        -- on PGT
            CASE c IS      -- determine control input
                WHEN "00" =>      -- reset
                    bcd := 0;
                WHEN "01" =>      -- count down
                    IF (bcd = 0) THEN      bcd := 9;
                    ELSE                  bcd := bcd - 1;
                    END IF;
                WHEN "10" =>      -- count up
                    IF (bcd = 9) THEN      bcd := 0;
                    ELSE                  bcd := bcd + 1;
                    END IF;
                WHEN "11" =>      -- hold count
                    bcd := bcd;
            END CASE;
        END IF;
        count <= bcd;          -- output counter

        -- assert active-low ripple carry output
        IF      (c = "01" AND bcd = 0)      THEN      carryn <= '0';
        ELSIF   (c = "10" AND bcd = 9)      THEN      carryn <= '0';
        ELSE                                         carryn <= '1';
        END IF;
    END PROCESS;
END vhdl;
```



### 14V.3 Mod-60 BCD counter

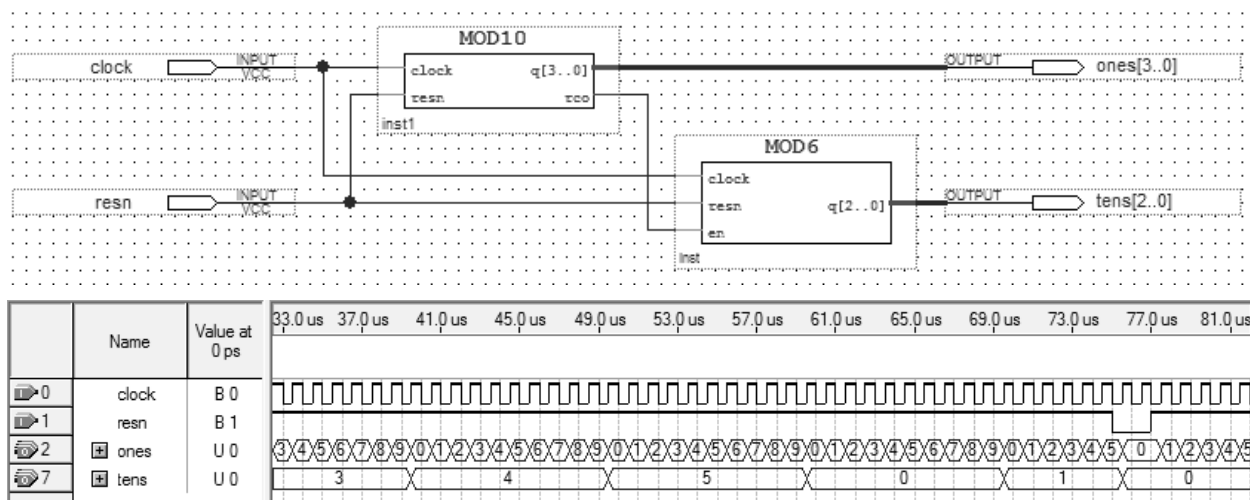

```

ENTITY mod10 IS
PORT (
    clock, resn      :IN BIT;
    q                :OUT INTEGER RANGE 0 TO 9;
    rco              :OUT BIT );
END mod10;

ARCHITECTURE vhd1 OF mod10 IS
BEGIN
    PROCESS (clock)
        VARIABLE count :INTEGER RANGE 0 TO 9;
    BEGIN

        IF (clock'EVENT AND clock = '1') THEN
            IF (resn = '0' OR count = 9) THEN
                count := 0;      -- reset/recycle
            ELSE
                count := count + 1;  -- increment
            END IF;
        END IF;

        IF (count = 9) THEN rco <= '1';      -- RCO
        ELSE rco <= '0';
        END IF;

        q <= count;      -- output count

    END PROCESS;
END vhd1;

```

```

ENTITY mod6 IS
PORT (
    clock, resn, en      :IN BIT;
    q                    :OUT INTEGER RANGE 0 TO 5   );
END mod6;

ARCHITECTURE vhd1 OF mod6 IS
BEGIN
    PROCESS (clock)
        VARIABLE count      :INTEGER RANGE 0 TO 5;      -- mod-6
    BEGIN

        IF (clock'EVENT AND clock = '1') THEN
            IF (resn = '0') THEN count := 0;              -- reset
            ELSIF (en = '1') THEN                          -- enabled
                IF (count = 5) THEN
                    count := 0;                            -- recyle
                ELSE
                    count := count + 1;                    -- increment
                END IF;
            END IF;
        END IF;

        q <= count;      -- output count

    END PROCESS;
END vhd1;

```

#### 14V.4 Mod-100 binary counter

```
ENTITY mod100 IS
PORT (
    clock, enable, w      :IN BIT;
    q                      :OUT INTEGER RANGE 0 TO 99;
    pulse                  :OUT BIT);
END mod100;

ARCHITECTURE vhd1 OF mod100 IS
BEGIN
    PROCESS (clock)
        VARIABLE count      :INTEGER RANGE 0 TO 99;
    BEGIN
        IF (clock'EVENT AND clock = '0') THEN          -- on NGT
            IF (enable = '1') THEN                      -- enabled?
                IF (count = 99) THEN
                    count := 0;                          -- recycle
                ELSE
                    count := count + 1;                  -- increment
                END IF;
            END IF;
        END IF;

        q <= count;                                     -- output count

        -- control pulse width of output
        IF (w = '0' AND count >= 95) THEN pulse <= '1';
        ELSIF (w = '1' AND count >= 90) THEN pulse <= '1';
        ELSE pulse <= '0';
        END IF;

    END PROCESS;
END vhd1;
```

## 14V.5 Stepper motor sequence controller

```
ENTITY half_step IS
PORT (
    step, cw, go          :IN BIT;
    q                     :OUT BIT_VECTOR (3 DOWNT0 0));
END half_step;

ARCHITECTURE vhd1 OF half_step IS
BEGIN
PROCESS (step)
VARIABLE stepper          :BIT_VECTOR (3 DOWNT0 0);
BEGIN

    IF (step'EVENT AND step = '1') THEN
        IF (go = '1' AND cw = '0') THEN
            -- enabled for CCW steps
            CASE stepper IS -- define CCW sequence
                WHEN "0101" => stepper := "0100";
                WHEN "0100" => stepper := "0110";
                WHEN "0110" => stepper := "0010";
                WHEN "0010" => stepper := "1010";
                WHEN "1010" => stepper := "1000";
                WHEN "1000" => stepper := "1001";
                WHEN "1001" => stepper := "0001";
                WHEN "0001" => stepper := "0101";
                WHEN OTHERS => stepper := "0101";
            END CASE;

            ELSIF (go = '1' AND cw = '1') THEN
                -- enabled for CW steps
                CASE stepper IS -- define CW sequence
                    WHEN "0101" => stepper := "0001";
                    WHEN "0001" => stepper := "1001";
                    WHEN "1001" => stepper := "1000";
                    WHEN "1000" => stepper := "1010";
                    WHEN "1010" => stepper := "0010";
                    WHEN "0010" => stepper := "0110";
                    WHEN "0110" => stepper := "0100";
                    WHEN "0100" => stepper := "0101";
                    WHEN OTHERS => stepper := "0101";
                END CASE;
            END IF;
        END IF;

        q <= stepper; -- output count
    END PROCESS;
END vhd1;
```

## 14V.6 Variable frequency divider

```
ENTITY divider IS
PORT (
    freq_in          :IN BIT;
    m                :IN BIT_VECTOR (1 DOWNTO 0);
    freq_out         :OUT BIT);
END divider;

ARCHITECTURE vhdl OF divider IS
BEGIN
    PROCESS (freq_in)
        VARIABLE count :INTEGER RANGE 0 TO 24;
                        -- buried counter
    BEGIN

        IF (freq_in'EVENT AND freq_in = '1') THEN
            -- determine if at selected terminal state
            IF (m = "00" AND count = 4) THEN
                count := 0;
                freq_out <= '1';
            ELSIF (m = "01" AND count = 9) THEN
                count := 0;
                freq_out <= '1';
            ELSIF (m = "10" AND count = 19) THEN
                count := 0;
                freq_out <= '1';
            ELSIF (m = "11" AND count = 24) THEN
                count := 0;
                freq_out <= '1';
            ELSE
                count := count + 1; -- incr.
                freq_out <= '0';
            END IF;
        END IF;

    END PROCESS;
END vhdl;
```

## 14V.7 Digital lock

```
ENTITY lock IS
PORT (enter      :IN BIT;
      data       :IN INTEGER RANGE 0 TO 15;
      unlock     :OUT BIT;
      ready      :OUT BIT);
END lock;

ARCHITECTURE vhd1 OF lock IS
CONSTANT comb1   :INTEGER RANGE 0 TO 15 := 7;
CONSTANT comb2   :INTEGER RANGE 0 TO 15 := 15;
CONSTANT comb3   :INTEGER RANGE 0 TO 15 := 10;
CONSTANT comb4   :INTEGER RANGE 0 TO 15 := 2;
      -- define desired lock combination
BEGIN
PROCESS (enter)
TYPE lock_state IS (start, statel, state2, state3, done);
VARIABLE sm      : lock_state;
BEGIN
    IF (sm = done) THEN unlock <= '1'; -- unlocked
    ELSE unlock <= '0'; -- locked
    END IF;
    IF (sm = start) THEN ready <= '1'; -- ready
    ELSE ready <= '0';
    END IF;
    IF (enter'EVENT AND enter = '1') THEN
        CASE sm IS
            WHEN start => -- beginning state
                IF (data = comb1) THEN sm := statel;
                ELSE sm := start; -- wrong number
                END IF;
            WHEN statel => -- 1st number ok
                IF (data = comb2) THEN sm := state2;
                ELSE sm := start; -- wrong number
                END IF;
            WHEN state2 => -- 2nd number ok
                IF (data = comb3) THEN sm := state3;
                ELSE sm := start; -- wrong number
                END IF;
            WHEN state3 => -- 3rd number ok
                IF (data = comb4) THEN sm := done;
                ELSE sm := start; -- wrong number
                END IF;
            WHEN done=> sm := start; -- 4th number ok
        END CASE;
    END IF;
END PROCESS;
END vhd1;
```

## 14V.8 Programmable frequency divider

```
ENTITY divide_by IS
PORT (
    freq_in      :IN BIT;
    b            :IN INTEGER RANGE 0 TO 255;
    freq_out     :OUT BIT
);
END divide_by;

ARCHITECTURE vhd1 OF divide_by IS
BEGIN
    PROCESS (freq_in)
        VARIABLE divider :INTEGER RANGE 0 TO 255;
        -- variable modulus counter

    BEGIN
        IF (freq_in'EVENT AND freq_in='1') THEN
            IF divider <= 1 THEN                -- reload
                divider := b;
            ELSE
                divider := divider - 1;        -- decr.
            END IF;
        END IF;

        IF divider <= 1 THEN                    -- detect state 1
            freq_out <= '1';
        ELSE
            freq_out <= '0';
        END IF;

    END PROCESS;
END vhd1;
```

## 14V.9 State machine

```

ENTITY state IS
PORT (
    clock, r, s, t      :IN BIT;
    q                    :OUT BIT_VECTOR (2 DOWNTO 0)
);
END state;

ARCHITECTURE vhd1 OF state IS
BEGIN
    PROCESS (clock)
        VARIABLE sm      :BIT_VECTOR (2 DOWNTO 0);
    BEGIN
        IF (clock'EVENT AND clock = '1') THEN
            CASE sm IS
                -- define sequence
                WHEN "001" => sm := "111";
                WHEN "111" => -- conditional
                    IF (t = '1') THEN
                        sm := "110";
                    ELSE
                        sm := "001";
                    END IF;
                WHEN "110" => sm := "100";
                WHEN "100" => sm := "011";
                WHEN "011" => -- conditional
                    IF (r = '0' AND s = '0') THEN
                        sm := "111";
                    ELSIF (r = '0' AND s = '1') THEN
                        sm := "100";
                    ELSE
                        sm := "011";
                    END IF;
                WHEN OTHERS => sm := "001";
                -- self-correcting & starting
            END CASE;
        END IF;

        q <= sm; -- output state machine
    END PROCESS;
END vhd1;


```



#### 14V.10 Variable pulse delay

```
ENTITY varypulsedelay IS
PORT (    clock      :IN BIT;
         start       :IN BIT;
         delay       :IN BIT;
         pulse       :OUT BIT );
END varypulsedelay;
ARCHITECTURE project14_10 OF varypulsedelay IS
BEGIN
PROCESS (clock, delay)
TYPE states IS (idle, one, two, three, four, five,
               six, seven, eight, nine, ten);
VARIABLE mach : states;
BEGIN
    IF (clock'EVENT AND clock = '1') THEN
        CASE mach IS
            WHEN idle => -- mach waits here
                IF (start = '1') THEN
                    mach := one;
                ELSE
                    mach := idle;
                END IF;
            WHEN one  => mach := two;
            WHEN two  => mach := three;
            WHEN three => mach := four;
            WHEN four  => mach := five;
            WHEN five  =>
                IF (delay = '0') THEN
                    mach := idle;
                ELSE
                    mach := six;
                END IF;
            WHEN six   => mach := seven;
            WHEN seven => mach := eight;
            WHEN eight => mach := nine;
            WHEN nine  => mach := ten;
            WHEN ten   => mach := idle;
        END CASE;
    END IF;
    IF (delay = '0' AND mach = five) THEN
        pulse <= '1';
    ELSIF (delay = '1' AND mach = ten) THEN
        pulse <= '1';
    ELSE
        pulse <= '0';
    END IF;
END PROCESS;
END project14_10;
```

## 14V.11 Frequency divider

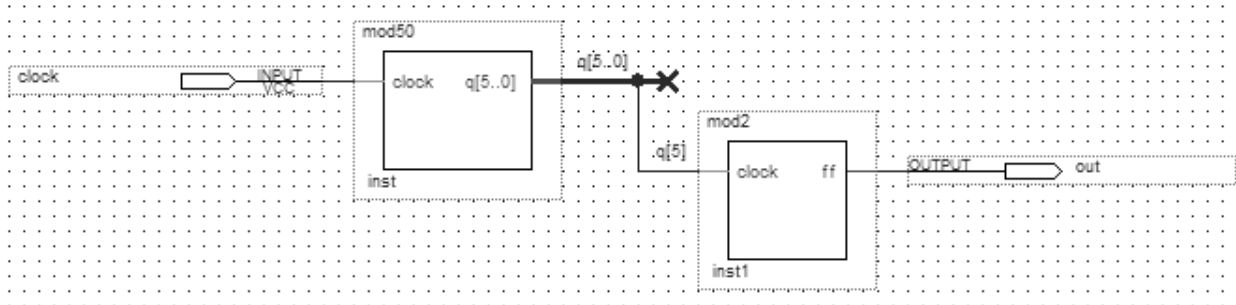

```

ENTITY mod50 IS
PORT (clock      :IN BIT;
      q          :OUT INTEGER RANGE 0 TO 49);
END mod50;
ARCHITECTURE project14_11 OF mod50 IS
BEGIN
PROCESS (clock)
VARIABLE count      :INTEGER RANGE 0 TO 49;
BEGIN
    IF (clock'EVENT AND clock = '1') THEN
        IF (count = 49) THEN count := 0;
        ELSE
            count := count + 1;
        END IF;
    END IF;
    q <= count;
END PROCESS;
END project14_11;

```

```

ENTITY mod2 IS
PORT (clock      :IN BIT;
      ff         :OUT BIT);
END mod2;
ARCHITECTURE block2 OF mod2 IS
BEGIN
PROCESS (clock)
VARIABLE flipflop   : BIT;
BEGIN
    IF (clock'EVENT AND clock = '1') THEN
        flipflop := NOT flipflop;
    END IF;
    ff <= flipflop;
END PROCESS;
END block2;

```

## 14V.12 Clock frequency divider

```
ENTITY clock_divider IS
PORT(
    clock_50MHz      :IN BIT;
    out_25kHz        :OUT INTEGER RANGE 0 TO 2047;
    out_10kHz        :OUT INTEGER RANGE 0 TO 8191
);
END clock_divider;

ARCHITECTURE vhd1 OF clock_divider IS
BEGIN
    PROCESS (clock_50MHz)
        VARIABLE mod2000    :INTEGER RANGE 0 TO 2047;
        VARIABLE mod5000    :INTEGER RANGE 0 TO 8191;
    BEGIN

        IF (clock_50MHz'EVENT AND clock_50MHz = '1') THEN
            IF mod2000 = 1999 THEN -- mod 2000
                mod2000 := 0;
            ELSE
                mod2000 := mod2000 + 1;
            END IF;

            IF mod5000 = 4999 THEN -- mod 5000
                mod5000 := 0;
            ELSE
                mod5000 := mod5000 + 1;
            END IF;
        END IF;

        out_25kHz <= mod2000;    -- use MSB for 25 kHz signal
        out_10kHz <= mod5000;    -- use MSB for 10 kHz signal

    END PROCESS;
END vhd1;
```

### 14V.13 Gray code counter

```

ENTITY gray IS
PORT (
    clock, dir          :IN BIT;
    q                   :OUT BIT_VECTOR (3 DOWNTO 0);
    index               :OUT BIT
);
END gray;

ARCHITECTURE vhd1 OF gray IS
BEGIN
    PROCESS (clock)      -- detect clock change
        VARIABLE seq     :BIT_VECTOR (3 DOWNTO 0);
        -- declare bit vector variable for state machine
    BEGIN
        IF (clock'EVENT AND clock = '1') THEN -- PGT
            IF (dir = '0') THEN -- count up
                CASE seq IS -- determine next state
                    WHEN "0000" => seq := "0001";
                    WHEN "0001" => seq := "0011";
                    WHEN "0011" => seq := "0010";
                    WHEN "0010" => seq := "0110";
                    WHEN "0110" => seq := "0111";
                    WHEN "0111" => seq := "0101";
                    WHEN "0101" => seq := "0100";
                    WHEN "0100" => seq := "1100";
                    WHEN "1100" => seq := "1101";
                    WHEN "1101" => seq := "1111";
                    WHEN "1111" => seq := "1110";
                    WHEN "1110" => seq := "1010";
                    WHEN "1010" => seq := "1011";
                    WHEN "1011" => seq := "1001";
                    WHEN "1001" => seq := "1000";
                    WHEN "1000" => seq := "0000";
                END CASE;
            ELSE -- count down
                CASE seq IS -- determine next state
                    WHEN "1000" => seq := "1001";
                    WHEN "1001" => seq := "1011";
                    WHEN "1011" => seq := "1010";
                    WHEN "1010" => seq := "1110";
                    WHEN "1110" => seq := "1111";
                    WHEN "1111" => seq := "1101";
                    WHEN "1101" => seq := "1100";
                    WHEN "1100" => seq := "0100";
                    WHEN "0100" => seq := "0101";
                    WHEN "0101" => seq := "0111";
                    WHEN "0111" => seq := "0110";
                    WHEN "0110" => seq := "0010";
                END CASE;
            END IF;
        END IF;
    END PROCESS;
END vhd1;

```

```

                                WHEN "0010" => seq := "0011";
                                WHEN "0011" => seq := "0001";
                                WHEN "0001" => seq := "0000";
                                WHEN "0000" => seq := "1000";
                                END CASE;
                                END IF;
                                END IF;
                                q <= seq;          -- output counter variable to port
                                -- produce index signal
                                IF (seq = "0000") THEN index <= '1';
                                ELSE index <= '0';
                                END IF;
                                END PROCESS;
                                END vhdl;

```

## Unit 15 Shift Register Applications

### 15.1 Waveform pattern generator

#### (a) HDL solutions

```
%      waveform pattern generator - AHDL solution      %
SUBDESIGN  pattern_gen_a
(
    clk, data[0..7]          :INPUT;
    serial_out, shift/load    :OUTPUT;
)

VARIABLE
    q[0..7]                  :DFF;          -- shift register
    control                  :MACHINE WITH STATES
        (sh/ld, s1, s2, s3, s4, s5, s6, s7);
        -- mod-8 control counter

BEGIN
    q[].clk = clk;
    control.clk = clk;
    serial_out = q7.q;

    TABLE          -- present state/next state table
        control      =>    control;
        sh/ld        =>    s1;
        s1           =>    s2;
        s2           =>    s3;
        s3           =>    s4;
        s4           =>    s5;
        s5           =>    s6;
        s6           =>    s7;
        s7           =>    sh/ld;
    END TABLE;

    IF (control == sh/ld)      THEN
        q[0..7].d = data[0..7];          -- parallel load
        shift/load = VCC;                -- shift/load pulse
    ELSE
        q[0..7].d = (GND, q[0..6].q);    -- shift data
        shift/load = GND;
    END IF;
END;
```

```

-- waveform pattern generator - VHDL solution
ENTITY pattern_gen_v IS
PORT (
    clk                      :IN BIT;
    data                    :IN BIT_VECTOR (0 TO 7);
    serial_out, shift_load  :OUT BIT
);
END pattern_gen_v;

ARCHITECTURE vhdl OF pattern_gen_v IS
BEGIN
PROCESS (clk)
    TYPE count_state IS
        (sh_ld, s1, s2, s3, s4, s5, s6, s7);
        -- enumerated data type
    VARIABLE control      :count_state;
    VARIABLE q            :BIT_VECTOR (0 TO 7);
    VARIABLE ser          :BIT;
    BEGIN
        ser := '0';
        serial_out <= q(7);

        -- define shift/load control signal
        IF (control = sh_ld) THEN shift_load <= '1';
        ELSE shift_load <= '0';
        END IF;


        IF (clk'EVENT AND clk = '1') THEN
            IF (control = sh_ld) THEN
                q := data;
                ELSE q := (ser & q(0 TO 6));
            END IF;

            -- define control sequence
            CASE control IS
                WHEN sh_ld => control := s1;
                WHEN s1   => control := s2;
                WHEN s2   => control := s3;
                WHEN s3   => control := s4;
                WHEN s4   => control := s5;
                WHEN s5   => control := s6;
                WHEN s6   => control := s7;
                WHEN s7   => control := sh_ld;
            END CASE;
        END IF;
    END PROCESS;
END vhdl;

```

## 15.1 Waveform pattern generator

### (b) LPM schematic solution

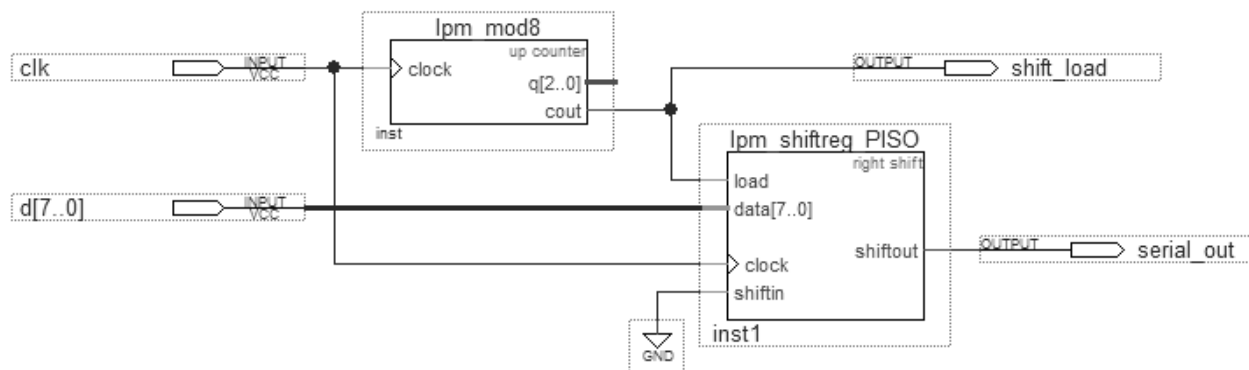

## 15.2 Serial data buffer

```

SUBDESIGN  serial_data_a          -- AHDL solution
(
    clk, ser_data                  :INPUT;
    pipo[0..7], new_data           :OUTPUT;
)

VARIABLE
    pipo[0..7]                    :DFFE;      -- D FFs with enable
    sipo[0..7]                    :DFF;
    control                       :MACHINE WITH STATES
                                   (s0, s1, s2, s3, s4, s5, s6, s7);

BEGIN
    pipo[].clk = clk;
    pipo[].ena = new_data;          -- enable pipo register
    pipo[].d = sipo[].q;            -- parallel out to parallel in
    sipo[].clk = clk;
    sipo[0..7].d = (ser_data, sipo[0..6].q); -- ser shift
    control.clk = clk;
    new_data = (control == s7);     -- time to parallel load

    TABLE                        -- present state/next state table
        control => control;
        s0      => s1;
        s1      => s2;
        s2      => s3;
        s3      => s4;
        s4      => s5;
        s5      => s6;
        s6      => s7;
        s7      => s0;
    END TABLE;
END;

```



```

ENTITY serial_data_v IS          -- VHDL solution
PORT (
    clk, ser_data                :IN BIT;
    pipo                         :OUT BIT_VECTOR (0 TO 7);
    new_data                     :OUT BIT
);
END serial_data_v;

ARCHITECTURE vhdl OF serial_data_v IS
BEGIN
PROCESS (clk)
    TYPE count_state IS (s0, s1, s2, s3, s4, s5, s6, s7);
                                -- enumerated data type

    VARIABLE control            :count_state;
    VARIABLE reg                :BIT_VECTOR (0 TO 7);
    VARIABLE sipo               :BIT_VECTOR (0 TO 7);

    BEGIN
        pipo <= reg;            -- connect buried register to port
                                -- detect data load
        IF (control = s7) THEN new_data <= '1';
        ELSE new_data <= '0';
        END IF;

        IF (clk'EVENT AND clk = '1') THEN
            sipo := (ser_data & sipo(0 TO 6));    -- shift
            CASE control IS                    -- control sequence
                WHEN s0 => control := s1;
                WHEN s1 => control := s2;
                WHEN s2 => control := s3;
                WHEN s3 => control := s4;
                WHEN s4 => control := s5;
                WHEN s5 => control := s6;
                WHEN s6 => control := s7;
                WHEN s7 => control := s0;
            END CASE;
            IF (control = s7) THEN
                reg := sipo;    -- parallel load
            END IF;
        END IF;

    END PROCESS;
END;

```

### 15.3 Barrel shifter

```

SUBDESIGN barrel_shift
(
    clk, s[2..0], ld, d[0..7]      :INPUT;
    q[0..7]                        :OUTPUT;
)
VARIABLE
    reg[0..7]                      :DFF;    -- register
BEGIN
    reg[].clk = clk;
    IF ld THEN reg[0..7].d = d[0..7];      -- parallel load
    ELSE -- shift data
        CASE s[] IS                      -- rotate s bits
            WHEN 0 => reg[0..7].d = reg[0..7].q;
            WHEN 1 => reg[0..7].d = (reg[1..7].q, reg[0].q);
            WHEN 2 => reg[0..7].d = (reg[2..7].q, reg[0..1].q);
            WHEN 3 => reg[0..7].d = (reg[3..7].q, reg[0..2].q);
            WHEN 4 => reg[0..7].d = (reg[4..7].q, reg[0..3].q);
            WHEN 5 => reg[0..7].d = (reg[5..7].q, reg[0..4].q);
            WHEN 6 => reg[0..7].d = (reg[6..7].q, reg[0..5].q);
            WHEN 7 => reg[0..7].d = (reg[7].q, reg[0..6].q);
        END CASE;
    END IF;
    q[] = reg[].q;    -- connect register to port
END;

```

```

ENTITY barrel_shift IS
PORT (clk, ld      :IN BIT;
      s            :IN BIT_VECTOR (2 DOWNTO 0);
      d            :IN BIT_VECTOR (0 TO 7);
      q            :OUT BIT_VECTOR (0 TO 7));
END barrel_shift;
ARCHITECTURE vhd1 OF barrel_shift IS
BEGIN
PROCESS (clk)
    VARIABLE reg:BIT_VECTOR (0 TO 7);    -- register
    BEGIN
        IF (clk'EVENT AND clk = '1') THEN
            IF (ld = '1') THEN reg := d;    -- parallel load
            ELSE-- shift data
                CASE s IS                -- rotate s bits
                    WHEN "000" => reg := reg;
                    WHEN "001" => reg := (reg(1 TO 7) & reg(0));
                    WHEN "010" => reg := (reg(2 TO 7) & reg(0 TO 1));
                    WHEN "011" => reg := (reg(3 TO 7) & reg(0 TO 2));
                    WHEN "100" => reg := (reg(4 TO 7) & reg(0 TO 3));
                    WHEN "101" => reg := (reg(5 TO 7) & reg(0 TO 4));
                    WHEN "110" => reg := (reg(6 TO 7) & reg(0 TO 5));
                    WHEN "111" => reg := (reg(7) & reg(0 TO 6));
                END CASE;
            END IF;
        END IF;
        q <= reg;    -- connect register to port
    END PROCESS;
END vhd1;

```

## 15.4 Mod-10 ring counter

```

SUBDESIGN  ring10          -- AHDL solution
(
    clk, clrn              :INPUT;
    q[0..9]                :OUTPUT;
)
VARIABLE
    q[0..9]                :DFF;      -- 10 bit register
    ser                    :NODE;      -- serial input signal

BEGIN
    q[].clk = clk;
    q[].clrn = clrn;           -- asynchronous clear
    IF q[0..8].q == B"11111111" THEN ser = GND;
    ELSE                      ser = VCC;
    END IF;                   -- determine feedback
    q[0..9].d = (ser, q[0..8].q);    -- shift
END;

```

```

ENTITY  ring10  IS          -- VHDL solution
PORT (
    Clk, clrn              :IN BIT;
    q                      :OUT BIT_VECTOR (0 TO 9)
);
END ring10;

ARCHITECTURE vhdl OF ring10 IS
SIGNAL  ser                :BIT;      -- serial feedback signal
BEGIN
PROCESS (clk, clrn)
    VARIABLE  r              :BIT_VECTOR (0 TO 9);
    BEGIN
        IF r(0 TO 8) = "11111111" THEN ser <= '0';
        ELSE                      ser <= '1';
        END IF;               -- determine feedback

        IF clrn = '0' THEN
            r := "0000000000";
        ELSIF (clk'EVENT AND clk = '1') THEN
            r := (ser & r(0 TO 8));    -- shift
        END IF;
        q <= r;               -- connect to output port
    END PROCESS;
END vhdl;

```

## 15.5 Mod-10 Johnson counter

```

SUBDESIGN  johnson10a                -- AHDL solution
(
    clock, reset, hold                :INPUT;
    q[0..4], zero                      :OUTPUT;
)

VARIABLE
    q[0..4]                          :DFF;        -- 5-bit reg
    ser                               :NODE;        -- feedback

BEGIN
    q[].clk = clock;
    ser = !q4;                        -- feedback function
    zero = !q0 & !q4;                -- decode 00000

    IF    reset    THEN  q[].d = B"00000";        -- reset
    ELSIF  hold    THEN  q[].d = q[].q;           -- hold
    ELSE   q[0..4].d = (ser, q[0..3].q);         -- count
    END IF;

END;

```

```

ENTITY  johnson10v  IS                -- VHDL solution
PORT (
    clock, reset, hold                :IN BIT;
    q                                  :OUT BIT_VECTOR (0 TO 4);
    zero                              :OUT BIT
);
END johnson10v;

ARCHITECTURE vhdl OF johnson10v  IS
SIGNAL  ser                               :BIT;        -- feedback
BEGIN
PROCESS (clock)
    VARIABLE  r                          :BIT_VECTOR (0 TO 4);
    BEGIN
        ser <= NOT r(4);                -- feedback function

        IF (clock'EVENT AND clock = '1') THEN
            IF (reset = '1') THEN  r := "00000";    -- reset
            ELSIF (hold = '1') THEN  r := r;        -- hold
            ELSE  r := (ser & r(0 TO 3));            -- count
            END IF;
        END IF;

        q <= r;                          -- output register
        zero <= (NOT r(0)) AND (NOT r(4));        -- decode
    END PROCESS;
END vhdl;

```

## 15.6 Mod-31 LFSR counter

```

SUBDESIGN  mod31lfsr                -- AHDL solution
(
    clock, resetn, enable           :INPUT;
    q[0..4]                         :OUTPUT;
)

VARIABLE
    q[0..4]                         :DFF;
    ser                             :NODE;

BEGIN
    q[].clk = clock;
    ser = !(q4 $ q2);                -- XNOR

    IF !resetn THEN q[].d = B"00000"; -- reset
    ELSIF !enable THEN q[].d = q[].q;  -- disable
    ELSE q[0..4].d = (ser, q[0..3].q); -- count
    END IF;

END;

```

```

ENTITY  mod31lfsr_v  IS                -- VHDL solution
PORT (
    clock, resetn, enable              :IN  BIT;
    q                                  :OUT BIT_VECTOR (0 TO 4)
);
END mod31lfsr_v;



ARCHITECTURE vhdl OF mod31lfsr_v IS
SIGNAL  ser                             :BIT;
BEGIN
PROCESS (clock)
    VARIABLE  reg                       :BIT_VECTOR (0 TO 4);
    BEGIN
        ser <= NOT (reg(4) XOR reg(2)); -- XNOR

        IF (clock'EVENT AND clock = '1') THEN
            IF (resetn = '0') THEN
                reg := "00000"; -- reset
            ELSIF (enable = '0') THEN
                reg := reg; -- disable
            ELSE reg := (ser & reg(0 TO 3)); -- count
            END IF;
        END IF;

        q <= reg; -- output count
    END PROCESS;
END vhdl;

```

15.7 Parallel data pipeline

 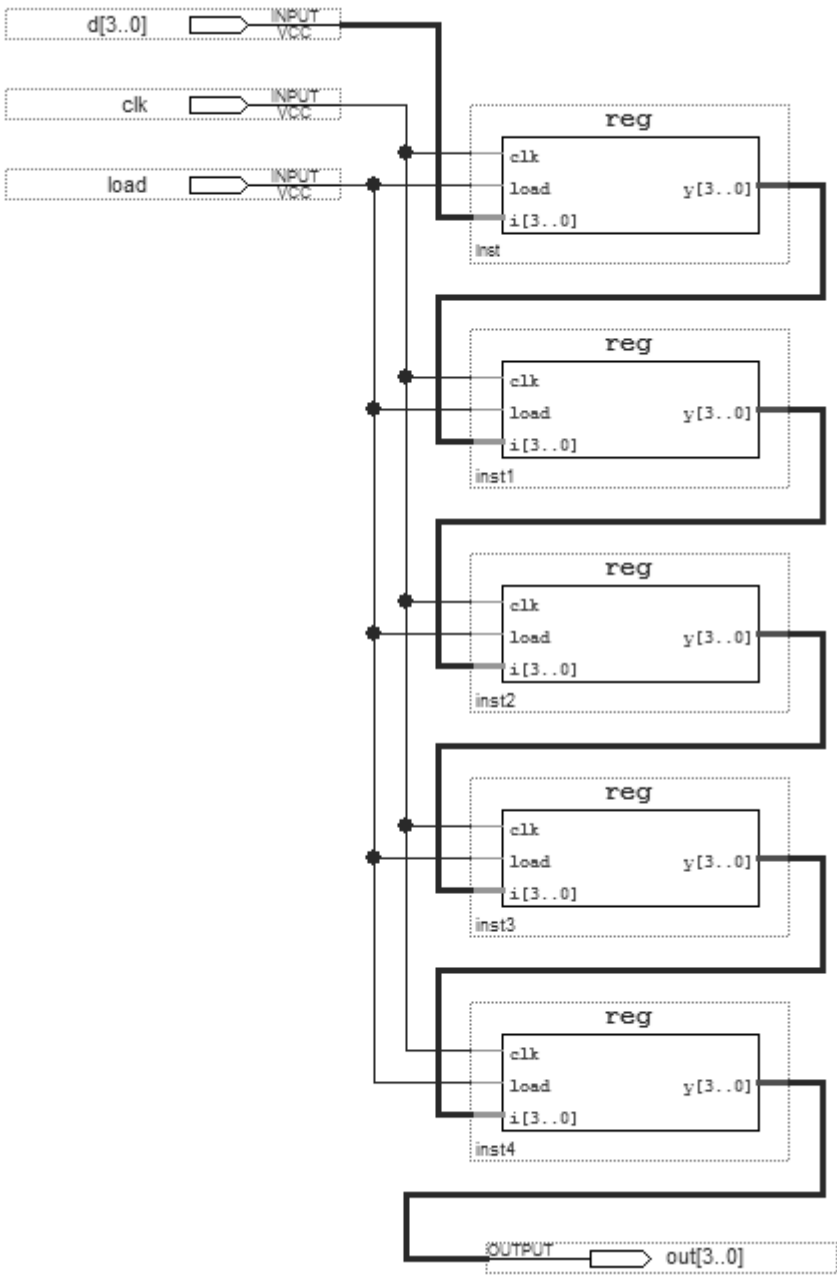

```

SUBDESIGN  reg                      -- AHDL solution
(
    clk, load, i[3..0]              :INPUT;
    y[3..0]                         :OUTPUT;
)
VARIABLE
    y[3..0]                        :DFF;      -- 4-bit reg.
BEGIN
    y[].clk = clk;

    IF  load  THEN  y[].d = i[];           -- load
    ELSE  y[3..0].d = y[3..0].q;         -- hold
    END IF;
END;

```

```

ENTITY  reg  IS
PORT (
    clk, load      :IN BIT;
    i              :IN BIT_VECTOR (3 DOWNTO 0);
    y              :OUT BIT_VECTOR (3 DOWNTO 0)
);
END reg;

ARCHITECTURE vhdl OF reg IS
BEGIN
PROCESS (clk)
    VARIABLE  reg1  :BIT_VECTOR (3 DOWNTO 0);
    BEGIN
        IF  (clk'EVENT AND clk = '1')  THEN
            IF  (load = '1')  THEN  reg1 := i;
            END IF;
        END IF;
        y <= reg1;
    END PROCESS;
END vhdl;

```

## 15.8 Special-purpose data register

```

SUBDESIGN  special_data            -- AHDL solution
(
    clk, s[1..0], i[3..0]          :INPUT;
    q[7..0]                        :OUTPUT;
)
VARIABLE
    q[7..0]                        :DFF;      -- 8-bit register
BEGIN
    q[].clk = clk;

```

```

CASE s[] IS
    WHEN 0 =>
        q[7..0].d = (q[7..4].q, i[3..0]);
    WHEN 1 =>
        q[7..0].d = (i[3..0], q[3..0].q);
    WHEN 2 =>
        q[7..0].d = (q[3..0].q, q[7..4].q);
    WHEN 3 =>
        q[7..0].d = (q0.q, q[7..1].q);
END CASE;
END;

```

```

ENTITY special_data_v IS
PORT (
    clk      :IN BIT;
    s        :IN INTEGER RANGE 0 TO 3;
    i        :IN BIT_VECTOR (3 DOWNTO 0);
    q        :OUT BIT_VECTOR (7 DOWNTO 0)
);
END special_data_v;

ARCHITECTURE vhd1 OF special_data_v IS
BEGIN
PROCESS (clk)
VARIABLE reg      :BIT_VECTOR (7 DOWNTO 0);
                -- 8-bit register
BEGIN

    IF (clk'EVENT AND clk = '1') THEN
        CASE s IS
            WHEN 0 => reg(7 DOWNTO 0) :=
                (reg(7 DOWNTO 4) & i(3 DOWNTO 0));
                -- load low nibble
            WHEN 1 => reg(7 DOWNTO 0) :=
                (i(3 DOWNTO 0) & reg(3 DOWNTO 0));
                -- load high nibble
            WHEN 2 => reg(7 DOWNTO 0) :=
                (reg(3 DOWNTO 0) & reg(7 DOWNTO 4));
                -- swap nibbles
            WHEN 3 => reg(7 DOWNTO 0) :=
                (reg(0) & reg(7 DOWNTO 1));
                -- rotate right
        END CASE;
    END IF;

    q <= reg;
                -- register to output port
END PROCESS;
END vhd1;

```



## 15.9 Shift/Rotate register

```
SUBDESIGN shift_rotate          -- AHDL solution

(
    clk, m[2..0]                :INPUT;
    ser, d[7..0]                :INPUT;
    q[7..0]                     :OUTPUT;
)

VARIABLE
    q[7..0]                     :DFF;          -- 8-bit register

BEGIN
    q[].clk = clk;

    CASE m[] IS                  -- determine control function
        WHEN 2 => q[7..0].d = d[7..0];
        -- load data
        WHEN 3 => q[7..0].d = q[7..0].q;
        -- hold data
        WHEN 4 => q[7..0].d = (ser, q[7..1].q);
        -- shift right
        WHEN 5 => q[7..0].d = (q[6..0].q, ser);
        -- shift left
        WHEN 6 => q[7..0].d = (q0.q, q[7..1].q);
        -- rotate right
        WHEN 7 => q[7..0].d = (q[6..0].q, q7.q);
        -- rotate left
        WHEN OTHERS => q[7..0].d = B"00000000";
        -- clear register with 0 or 1
    END CASE;
END;
```

```

ENTITY shift_rotate_v IS          -- VHDL solution
PORT (
    clk, ser          :IN BIT;
    m                 :IN INTEGER RANGE 0 TO 7;
    d                 :IN BIT_VECTOR (7 DOWNTO 0);
    q                 :OUT BIT_VECTOR (7 DOWNTO 0)
);
END shift_rotate_v;

ARCHITECTURE vhdl OF shift_rotate_v IS
BEGIN
    PROCESS (clk)
        VARIABLE reg      :BIT_VECTOR (7 DOWNTO 0);
                                -- 8-bit register
    BEGIN
        IF (clk'EVENT AND clk = '1') THEN
            CASE m IS          -- determine function
                WHEN 2 => reg(7 DOWNTO 0) := d(7 DOWNTO 0);
                                -- load data
                WHEN 3 => reg(7 DOWNTO 0) := reg(7 DOWNTO 0);
                                -- hold data
                WHEN 4 => reg(7 DOWNTO 0) := (ser & reg(7 DOWNTO 1));
                                -- shift right
                WHEN 5 => reg(7 DOWNTO 0) := (reg(6 DOWNTO 0) & ser);
                                -- shift left
                WHEN 6 => reg(7 DOWNTO 0) := (reg(0) & reg(7 DOWNTO 1));
                                -- rotate right
                WHEN 7 => reg(7 DOWNTO 0) := (reg(6 DOWNTO 0) & reg(7));
                                -- rotate left
                WHEN OTHERS => reg(7 DOWNTO 0) := "00000000";
                                -- clear register with 0 or 1
            END CASE;
        END IF;
        q <= reg;          -- connect register to port
    END PROCESS;
END vhdl;

```

## Unit 16 Synchronous Counter Design with Flip-Flops

### 16.1 Mod-6 synchronous counter design

Present States			Next States			Flip-flop Inputs					
$QC_n$	$QB_n$	$QA_n$	$QC_{n+1}$	$QB_{n+1}$	$QA_{n+1}$	JC	KC	JB	KB	JA	KA
0	0	0	0	0	1	0	X	0	X	1	X
0	0	1	0	1	0	0	X	1	X	X	1
0	1	0	0	1	1	0	X	X	0	1	X
0	1	1	1	0	0	1	X	X	1	X	1
1	0	0	1	0	1	X	0	0	X	1	X
1	0	1	0	0	0	X	1	0	X	X	1
1	1	0	X	X	X	X	X	X	X	X	X
1	1	1	X	X	X	X	X	X	X	X	X

QB QA

QC	00	01	11	10
0	0	0	1	0
1	X	X	X	X

**JC**

QB QA

QC	00	01	11	10
0	X	X	X	X
1	0	1	X	X

**KC**

QB QA

QC	00	01	11	10
0	0	1	X	X
1	0	0	X	X

**JB**

QB QA

QC	00	01	11	10
0	X	X	1	0
1	X	X	X	X

**KB**

QB QA

QC	00	01	11	10
0	1	X	X	1
1	1	X	X	X

**JA**

QB QA

QC	00	01	11	10
0	X	1	1	X
1	X	1	X	X

**KA**

$$JC = QB \overline{QA}$$

$$KC = QA$$

$$JB = \overline{QC} QA$$

$$KB = QA$$

$$JA = KA = 1$$

QB QA

QC	00	01	11	10
0	0	0	1	0
1	1	0	X	X

$$D_{QC} = QC \overline{QA} + QB QA$$

QB QA

QC	00	01	11	10
0	0	1	0	1
1	0	0	X	X

$$D_{QB} = QB \overline{QA} + \overline{QC} \overline{QB} QA$$

QB QA

QC	00	01	11	10
0	1	0	0	1
1	1	0	X	X

$$D_{QA} = \overline{QA}$$

## 16.2 Mod-5 synchronous, down counter design

Present States			Next States			Flip-flop Inputs					
$QX_n$	$QY_n$	$QZ_n$	$QX_{n+1}$	$QY_{n+1}$	$QZ_{n+1}$	JX	KX	JY	KY	JZ	KZ
0	0	0	1	0	0	1	X	0	X	0	X
0	0	1	0	0	0	0	X	0	X	X	1
0	1	0	0	0	1	0	X	X	1	1	X
0	1	1	0	1	0	0	X	X	0	X	1
1	0	0	0	1	1	X	1	1	X	1	X
1	0	1	X	X	X	X	X	X	X	X	X
1	1	0	X	X	X	X	X	X	X	X	X
1	1	1	X	X	X	X	X	X	X	X	X

QY QZ

QX	00	01	11	10	
0	1	0	0	0	JX
1	X	X	X	X	

QY QZ

QX	00	01	11	10	
0	X	X	X	X	KX
1	1	X	X	X	

QY QZ

QX	00	01	11	10	
0	0	0	X	X	JY
1	1	X	X	X	

QY QZ

QX	00	01	11	10	
0	X	X	0	1	KY
1	X	X	X	X	

QY QZ

QX	00	01	11	10	
0	0	X	X	1	JZ
1	1	X	X	X	

QY QZ

QX	00	01	11	10	
0	X	1	1	X	KZ
1	X	X	X	X	

$$JX = \overline{QY} \overline{QZ}$$

$$KX = 1$$

$$JY = QX$$

$$KY = \overline{QZ}$$

$$JZ = QY + QX$$

$$KZ = 1$$

QY QZ

QX	00	01	11	10
0	1	0	0	0
1	0	X	X	X

$$D_{QX} = \overline{QX} \overline{QY} \overline{QZ}$$

QY QZ

QX	00	01	11	10
0	0	0	1	0
1	1	X	X	X

$$D_{QY} = QX + QY QZ$$

QY QZ

QX	00	01	11	10
0	0	0	0	1
1	1	X	X	X

$$D_{QZ} = QX + QY \overline{QZ}$$

### 16.3 Synchronous 8421 BCD counter design

n				n+1											
QD	QC	QB	QA	QD	QC	QB	QA	JD	KD	JC	KC	JB	KB	JA	KA
0	0	0	0	0	0	0	1	0	X	0	X	0	X	1	X
0	0	0	1	0	0	1	0	0	X	0	X	1	X	X	1
0	0	1	0	0	0	1	1	0	X	0	X	X	0	1	X
0	0	1	1	0	1	0	0	0	X	1	X	X	1	X	1
0	1	0	0	0	1	0	1	0	X	X	0	0	X	1	X
0	1	0	1	0	1	1	0	0	X	X	0	1	X	X	1
0	1	1	0	0	1	1	1	0	X	X	0	X	0	1	X
0	1	1	1	1	0	0	0	1	X	X	1	X	1	X	1
1	0	0	0	1	0	0	1	X	0	0	X	0	X	1	X
1	0	0	1	0	0	0	0	X	1	0	X	0	X	X	1
1	0	1	0	X	X	X	X	X	X	X	X	X	X	X	X
1	0	1	1	X	X	X	X	X	X	X	X	X	X	X	X
1	1	0	0	X	X	X	X	X	X	X	X	X	X	X	X
1	1	0	1	X	X	X	X	X	X	X	X	X	X	X	X
1	1	1	0	X	X	X	X	X	X	X	X	X	X	X	X
1	1	1	1	X	X	X	X	X	X	X	X	X	X	X	X

QB QA					
QD QC	0 0	0 1	1 1	1 0	
0 0	0	0	0	0	
0 1	0	0	1	0	
1 1	X	X	X	X	
1 0	X	X	X	X	

$$JD = QC \overline{QB} QA$$

QB QA					
QD QC	0 0	0 1	1 1	1 0	
0 0	X	X	X	X	
0 1	X	X	X	X	
1 1	X	X	X	X	
1 0	0	1	X	X	

$$KD = QA$$

QB QA					
QD QC	0 0	0 1	1 1	1 0	
0 0	0	0	1	0	
0 1	X	X	X	X	
1 1	X	X	X	X	
1 0	0	0	X	X	

$$JC = \overline{QB} QA$$

QB QA					
QD QC	0 0	0 1	1 1	1 0	
0 0	X	X	X	X	
0 1	0	0	1	0	
1 1	X	X	X	X	
1 0	X	X	X	X	

$$KC = \overline{QB} QA$$

QB QA					
QD QC	0 0	0 1	1 1	1 0	
0 0	0	1	X	X	
0 1	0	1	X	X	
1 1	X	X	X	X	
1 0	0	0	X	X	

$$JB = \overline{QD} QA$$

QB QA					
QD QC	0 0	0 1	1 1	1 0	
0 0	X	X	1	0	
0 1	X	X	1	0	
1 1	X	X	X	X	
1 0	X	X	X	X	

$$KB = QA$$

QB QA					
QD QC	0 0	0 1	1 1	1 0	
0 0	1	X	X	1	
0 1	1	X	X	1	
1 1	X	X	X	X	
1 0	1	X	X	X	

$$JA = 1$$

QB QA					
QD QC	0 0	0 1	1 1	1 0	
0 0	X	1	1	X	
0 1	X	1	1	X	
1 1	X	X	X	X	
1 0	X	1	X	X	

$$KA = 1$$

QB QA				
QD QC	0 0	0 1	1 1	1 0
0 0	0	0	0	0
0 1	0	0	1	0
1 1	X	X	X	X
1 0	1	0	X	X

$$DQD = QD \overline{QA} + QC \overline{QB} QA$$

QB QA				
QD QC	0 0	0 1	1 1	1 0
0 0	0	1	0	1
0 1	0	1	0	1
1 1	X	X	X	X
1 0	0	0	X	X

$$DQB = QB \overline{QA} + \overline{QD} \overline{QB} QA$$

QB QA				
QD QC	0 0	0 1	1 1	1 0
0 0	0	0	1	0
0 1	1	1	0	1
1 1	X	X	X	X
1 0	0	0	X	X

$$DQC = QC \overline{QB} + QC \overline{QA} + \overline{QC} QB QA$$

QB QA				
QD QC	0 0	0 1	1 1	1 0
0 0	1	0	0	1
0 1	1	0	0	1
1 1	X	X	X	X
1 0	1	0	X	X

$$DQA = \overline{QA}$$

## 16.4 Synchronous 8421 BCD down counter design

n				n+1				JD KD		JC KC		JB KB		JA KA	
QD	QC	QB	QA	QD	QC	QB	QA	JD	KD	JC	KC	JB	KB	JA	KA
0	0	0	0	1	0	0	1	1	X	0	X	0	X	1	X
0	0	0	1	0	0	0	0	0	X	0	X	0	X	X	1
0	0	1	0	0	0	0	1	0	X	0	X	X	1	1	X
0	0	1	1	0	0	1	0	0	X	0	X	X	0	X	1
0	1	0	0	0	0	1	1	0	X	X	1	1	X	1	X
0	1	0	1	0	1	0	0	0	X	X	0	0	X	X	1
0	1	1	0	0	1	0	1	0	X	X	0	X	1	1	X
0	1	1	1	0	1	1	0	0	X	X	0	X	0	X	1
1	0	0	0	0	1	1	1	X	1	1	X	1	X	1	X
1	0	0	1	1	0	0	0	X	0	0	X	0	X	X	1
1	0	1	0	X	X	X	X	X	X	X	X	X	X	X	X
1	0	1	1	X	X	X	X	X	X	X	X	X	X	X	X
1	1	0	0	X	X	X	X	X	X	X	X	X	X	X	X
1	1	0	1	X	X	X	X	X	X	X	X	X	X	X	X
1	1	1	0	X	X	X	X	X	X	X	X	X	X	X	X
1	1	1	1	X	X	X	X	X	X	X	X	X	X	X	X

QB QA				
QD QC	0 0	0 1	1 1	1 0
0 0	1	0	0	0
0 1	0	0	0	0
1 1	X	X	X	X
1 0	X	X	X	X

$$JD = \overline{QC} \overline{QB} \overline{QA}$$

QB QA				
QD QC	0 0	0 1	1 1	1 0
0 0	X	X	X	X
0 1	X	X	X	X
1 1	X	X	X	X
1 0	1	0	X	X

$$KD = \overline{QA}$$

QB QA				
QD QC	0 0	0 1	1 1	1 0
0 0	0	0	0	0
0 1	X	X	X	X
1 1	X	X	X	X
1 0	1	0	X	X

$$JC = QD \overline{QA}$$

JC

QB QA				
QD QC	0 0	0 1	1 1	1 0
0 0	X	X	X	X
0 1	1	0	0	0
1 1	X	X	X	X
1 0	X	X	X	X

$$KC = \overline{QB} \overline{QA}$$

KC

QB QA				
QD QC	0 0	0 1	1 1	1 0
0 0	0	0	X	X
0 1	1	0	X	X
1 1	X	X	X	X
1 0	1	0	X	X

$$JB = QC \overline{QA} + QD \overline{QA}$$

JB

QB QA				
QD QC	0 0	0 1	1 1	1 0
0 0	X	X	0	1
0 1	X	X	0	1
1 1	X	X	X	X
1 0	X	X	X	X

$$KB = \overline{QA}$$

KB

QB QA				
QD QC	0 0	0 1	1 1	1 0
0 0	1	X	X	1
0 1	1	X	X	1
1 1	X	X	X	X
1 0	1	X	X	X

$$JA = 1$$

JA

QB QA				
QD QC	0 0	0 1	1 1	1 0
0 0	X	1	1	X
0 1	X	1	1	X
1 1	X	X	X	X
1 0	X	1	X	X

$$KA = 1$$

KA

QB QA				
QD QC	0 0	0 1	1 1	1 0
0 0	1	0	0	0
0 1	0	0	0	0
1 1	X	X	X	X
1 0	0	1	X	X

$$DQD = QD QA + \overline{QD} \overline{QC} \overline{QB} \overline{QA}$$

QB QA				
QD QC	0 0	0 1	1 1	1 0
0 0	0	0	0	0
0 1	0	1	1	1
1 1	X	X	X	X
1 0	1	0	X	X

$$DQC = QC QB + QC QA + QD \overline{QA}$$

QB QA				
QD QC	0 0	0 1	1 1	1 0
0 0	0	0	1	0
0 1	1	0	1	0
1 1	X	X	X	X
1 0	1	0	X	X

$$DQB = QB QA + QD \overline{QA} + QC \overline{QB} \overline{QA}$$

QB QA				
QD QC	0 0	0 1	1 1	1 0
0 0	1	0	0	1
0 1	1	0	0	1
1 1	X	X	X	X
1 0	1	0	X	X

$$DQA = \overline{QA}$$

## 16.5 Synchronous mod-11 counter

n				n+1											
QD	QC	QB	QA	QD	QC	QB	QA	JD	KD	JC	KC	JB	KB	JA	KA
0	0	0	0	0	0	0	1	0	X	0	X	0	X	1	X
0	0	0	1	0	0	1	0	0	X	0	X	1	X	X	1
0	0	1	0	0	0	1	1	0	X	0	X	X	0	1	X
0	0	1	1	0	1	0	0	0	X	1	X	X	1	X	1
0	1	0	0	0	1	0	1	0	X	X	0	0	X	1	X
0	1	0	1	0	1	1	0	0	X	X	0	1	X	X	1
0	1	1	0	0	1	1	1	0	X	X	0	X	0	1	X
0	1	1	1	1	0	0	0	1	X	X	1	X	1	X	1
1	0	0	0	1	0	0	1	X	0	0	X	0	X	1	X
1	0	0	1	1	0	1	0	X	0	0	X	1	X	X	1
1	0	1	0	0	0	0	0	X	1	0	X	X	1	0	X
1	0	1	1	X	X	X	X	X	X	X	X	X	X	X	X
1	1	0	0	X	X	X	X	X	X	X	X	X	X	X	X
1	1	0	1	X	X	X	X	X	X	X	X	X	X	X	X
1	1	1	0	X	X	X	X	X	X	X	X	X	X	X	X
1	1	1	1	X	X	X	X	X	X	X	X	X	X	X	X

QB QA  
QD QC

0 0	0	0	0	1	1	1	0
0 0	0	0	0	0			
0 1	0	0	1	0			
1 1	X	X	X	X			
1 0	X	X	X	X			

JD = QC QB QA

QB QA  
QD QC

0 0	X	X	X	X
0 1	X	X	X	X
1 1	X	X	X	X
1 0	0	0	X	1

KD = QB

QB QA  
QD QC

0 0	0	0	1	0
0 1	X	X	X	X
1 1	X	X	X	X
1 0	0	0	X	0

JC = QB QA

QB QA  
QD QC

0 0	X	X	X	X
0 1	0	0	1	0
1 1	X	X	X	X
1 0	X	X	X	X

KC = QB QA

QB QA  
QD QC

0 0	0	1	X	X
0 1	0	1	X	X
1 1	X	X	X	X
1 0	0	1	X	X

JB = QA

QB QA  
QD QC

0 0	X	X	1	0
0 1	X	X	1	0
1 1	X	X	X	X
1 0	X	X	X	1

KB = QA + QD

QB QA  
QD QC

0 0	1	X	X	1
0 1	1	X	X	1
1 1	X	X	X	X
1 0	1	X	X	0

JA =  $\overline{QB} + \overline{QD}$

QB QA  
QD QC

0 0	X	1	1	X
0 1	X	1	1	X
1 1	X	X	X	X
1 0	X	1	X	X

KA = 1



		QB QA			
QD	QC	0 0	0 1	1 1	1 0
0	0	0	0	0	0
0	1	0	0	1	0
1	1	X	X	X	X
1	0	1	1	X	0

$$DQD = QD \overline{QB} + QC \overline{QB} QA$$

		QB QA			
QD	QC	0 0	0 1	1 1	1 0
0	0	0	1	0	1
0	1	0	1	0	1
1	1	X	X	X	X
1	0	0	1	X	0

$$DQB = \overline{QB} QA + \overline{QD} QB \overline{QA}$$

		QB QA			
QD	QC	0 0	0 1	1 1	1 0
0	0	0	0	1	0
0	1	1	1	0	1
1	1	X	X	X	X
1	0	0	0	X	0


$$DQC = QC \overline{QB} + QC \overline{QA} + \overline{QC} QB QA$$

		QB QA			
QD	QC	0 0	0 1	1 1	1 0
0	0	1	0	0	1
0	1	1	0	0	1
1	1	X	X	X	X
1	0	1	0	X	0


$$DQA = \overline{QB} \overline{QA} + \overline{QD} \overline{QA}$$

## Unit 17 Decoder and Display Applications
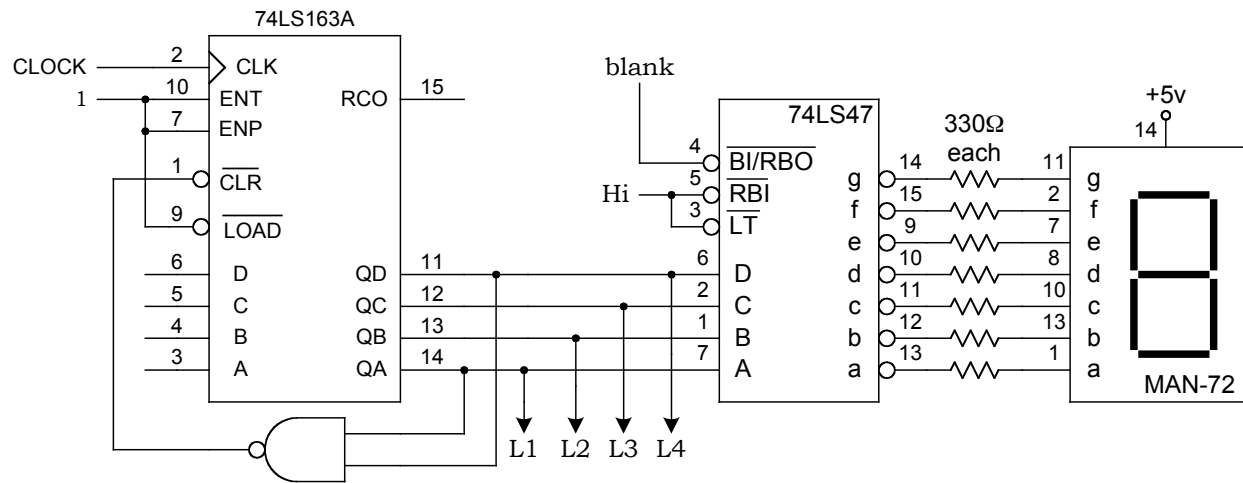
### 17.1 Modified 4-bit binary counter and display



### 17.2 Mod-16 counter and decoder

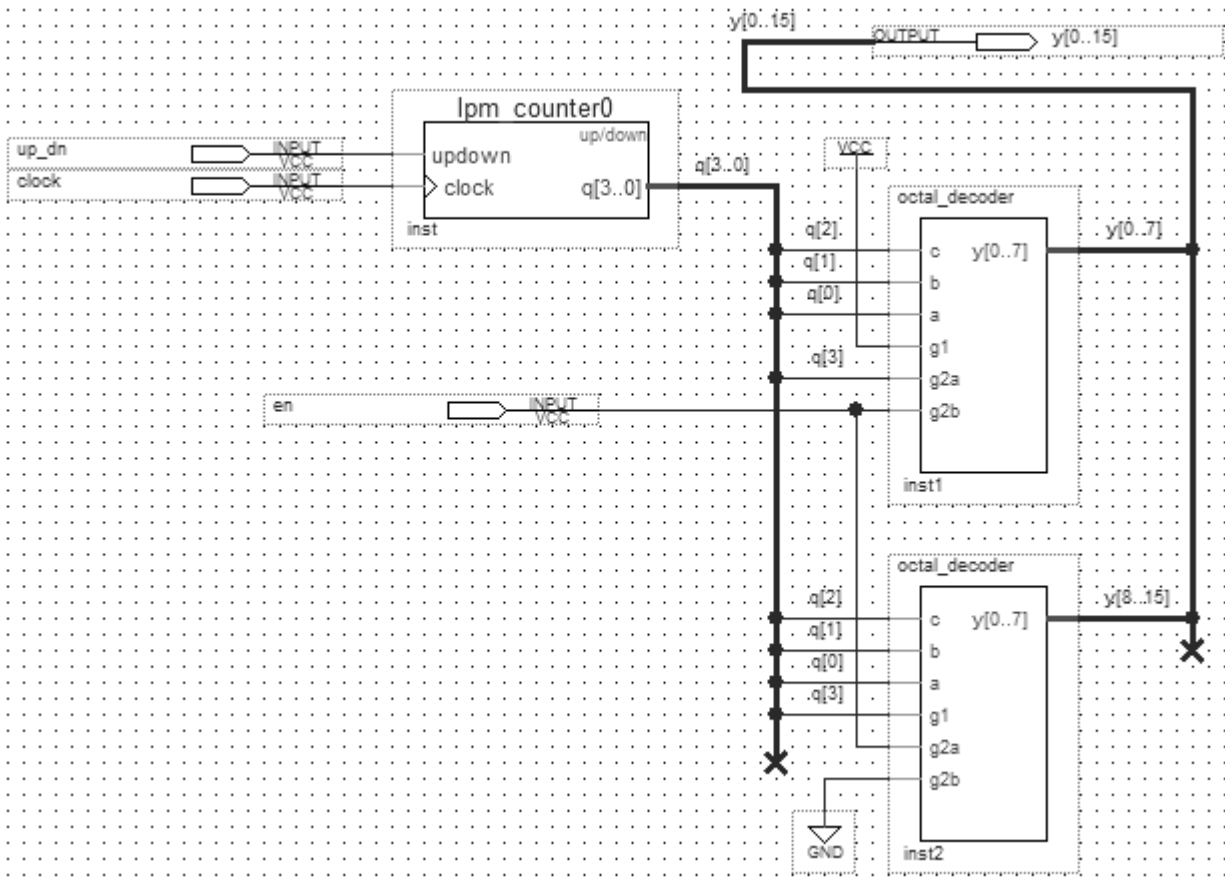

```

SUBDESIGN  octal_decoder
(c, b, a, g1, g2a, g2b           :INPUT;
 y[0..7]                          :OUTPUT;)
VARIABLE
    enable[1..3]                  :NODE;
    bin[2..0]                     :NODE;
BEGIN
    bin[] = (c, b, a);
    enable[] = (g1, g2a, g2b);
    IF enable[] == B"100" THEN
        CASE bin[] IS
            WHEN B"000" => y[] = B"01111111";
            WHEN B"001" => y[] = B"10111111";
            WHEN B"010" => y[] = B"11011111";
            WHEN B"011" => y[] = B"11101111";
            WHEN B"100" => y[] = B"11110111";
            WHEN B"101" => y[] = B"11111011";
            WHEN B"110" => y[] = B"11111101";
            WHEN B"111" => y[] = B"11111110";
        END CASE;
    ELSE
        y[] = B"11111111";
    END IF;
END;


```

```

ENTITY  octal_decoder  IS
PORT (c, b, a, g1, g2a, g2b           :IN BIT;
      y                          :OUT BIT_VECTOR (0 TO 7));
END octal_decoder;
ARCHITECTURE vhd1 OF octal_decoder IS
BEGIN
PROCESS (c, b, a, g1, g2a, g2b)
VARIABLE enable      :BIT_VECTOR (1 TO 3);
VARIABLE bin         :BIT_VECTOR (2 DOWNT0 0);
BEGIN
    bin := (c & b & a);
    enable := (g1 & g2a & g2b);
    IF (enable = "100") THEN
        CASE bin IS
            WHEN "000" => y <= B"01111111";
            WHEN "001" => y <= B"10111111";
            WHEN "010" => y <= B"11011111";
            WHEN "011" => y <= B"11101111";
            WHEN "100" => y <= B"11110111";
            WHEN "101" => y <= B"11111011";
            WHEN "110" => y <= B"11111101";
            WHEN "111" => y <= B"11111110";
        END CASE;
    ELSE
        y <= B"11111111";
    END IF;
END PROCESS;
END vhd1;

```
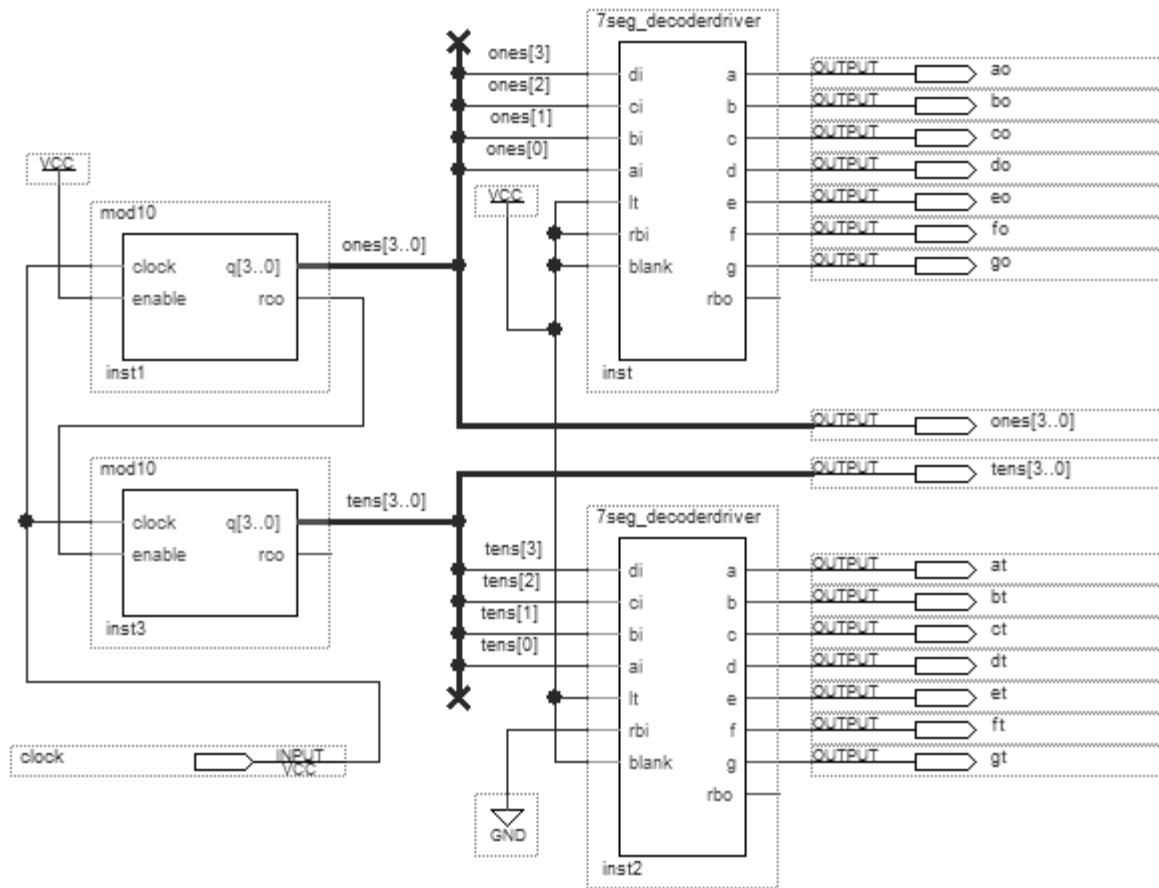
### 17.3 Mod-100 BCD counter and 7-segment display



```

SUBDESIGN mod10
(clock, enable                                :INPUT;
 q[3..0], rco                                :OUTPUT;)
VARIABLE
  counter[3..0]                                :DFF;
BEGIN
  DEFAULTS
    rco = GND;
  END DEFAULTS;
  counter[].clk = clock;
  IF enable THEN
    IF counter[].q == 9 THEN
      counter[].d = B"0000";
      rco = VCC;
    ELSE
      counter[].d = counter[].q + 1;
    END IF;
  ELSE
    counter[].d = counter[].q;
  END IF;
  q[] = counter[].q;
END;

```

```

SUBDESIGN 7seg_decoderdriver    -- common anode
(di, ci, bi, ai, lt, rbi, blank      :INPUT;
 a, b, c, d, e, f, g, rbo           :OUTPUT;)
VARIABLE
    seg[0..6]                :NODE;
    bin[3..0]                :NODE;
BEGIN
DEFAULTS
    rbo = VCC;
END DEFAULTS;
    bin[] = (di, ci, bi, ai);
    a = seg0;
    b = seg1;
    c = seg2;
    d = seg3;
    e = seg4;
    f = seg5;
    g = seg6;
    IF      (lt == GND)      THEN seg[] = B"0000000";
    ELSIF (blank == GND)    THEN seg[] = B"1111111";
    ELSIF (rbi == GND & bin[] == 0) THEN rbo = GND;
                                   seg[] = B"1111111";
    ELSE
        CASE bin[] IS      -- segments  abcdefg
            WHEN 0      => seg[] = B"0000001";
            WHEN 1      => seg[] = B"1001111";
            WHEN 2      => seg[] = B"0010010";
            WHEN 3      => seg[] = B"0000110";
            WHEN 4      => seg[] = B"1001100";
            WHEN 5      => seg[] = B"0100100";
            WHEN 6      => seg[] = B"1100000";
            WHEN 7      => seg[] = B"0001111";
            WHEN 8      => seg[] = B"0000000";
            WHEN 9      => seg[] = B"0001100";
            WHEN OTHERS => seg[] = B"1111111";
        END CASE;
    END IF;
END;

```

```

ENTITY mod10 IS
PORT (clock      :IN BIT;
      enable     :IN BIT;
      q          :OUT INTEGER RANGE 0 TO 15;
      rco        :OUT BIT);
END mod10;
ARCHITECTURE vhd1 OF mod10 IS
BEGIN
    PROCESS (clock, enable)
        VARIABLE counter :INTEGER RANGE 0 TO 15;
    BEGIN

```

```

        IF ((counter = 9) AND (enable = '1')) THEN
            rco <= '1';
        ELSE
            rco <= '0';
        END IF;
        IF (clock'EVENT AND clock = '1') THEN
            IF (enable = '1') THEN
                IF (counter = 9) THEN
                    counter := 0;
                ELSE
                    counter := counter + 1;
                END IF;
            END IF;
        END IF;
        q <= counter;
    END PROCESS;
END vhdl;

```

```

ENTITY seg_decoderdriver IS    -- common anode
PORT (di, ci, bi, ai, lt, rbi, blank      :IN BIT;
      a, b, c, d, e, f, g, rbo          :OUT BIT);
END seg_decoderdriver;
ARCHITECTURE vhdl OF seg_decoderdriver IS
BEGIN
    PROCESS (di, ci, bi, ai, lt, rbi, blank)
    VARIABLE seg      :BIT_VECTOR (0 TO 6);
    VARIABLE bin      :BIT_VECTOR (3 DOWNT0 0);
    BEGIN
        bin := (di & ci & bi & ai);
        a <= seg(0);
        b <= seg(1);
        c <= seg(2);
        d <= seg(3);
        e <= seg(4);
        f <= seg(5);
        g <= seg(6);
        IF      (lt = '0')      THEN
            seg := "0000000"; rbo <= '1';
        ELSIF (blank = '0')    THEN
            seg := "1111111"; rbo <= '1';
        ELSIF (rbi = '0' AND bin = "0000") THEN
            seg := "1111111"; rbo <= '0';
        ELSE
            CASE bin IS        -- segments  abcdefg
            WHEN "0000" => seg := "0000001"; rbo <= '1';
            WHEN "0001" => seg := "1001111"; rbo <= '1';
            WHEN "0010" => seg := "0010010"; rbo <= '1';
            WHEN "0011" => seg := "0000110"; rbo <= '1';
            WHEN "0100" => seg := "1001100"; rbo <= '1';
            WHEN "0101" => seg := "0100100"; rbo <= '1';
            WHEN "0110" => seg := "1100000"; rbo <= '1';
            WHEN "0111" => seg := "0001111"; rbo <= '1';
            WHEN "1000" => seg := "0000000"; rbo <= '1';


```

```

        WHEN "1001" => seg := "0001100"; rbo <= '1';
        WHEN OTHERS => seg := "1111111"; rbo <= '1';
    END CASE;
END IF;
END PROCESS;
END vhdl;

```
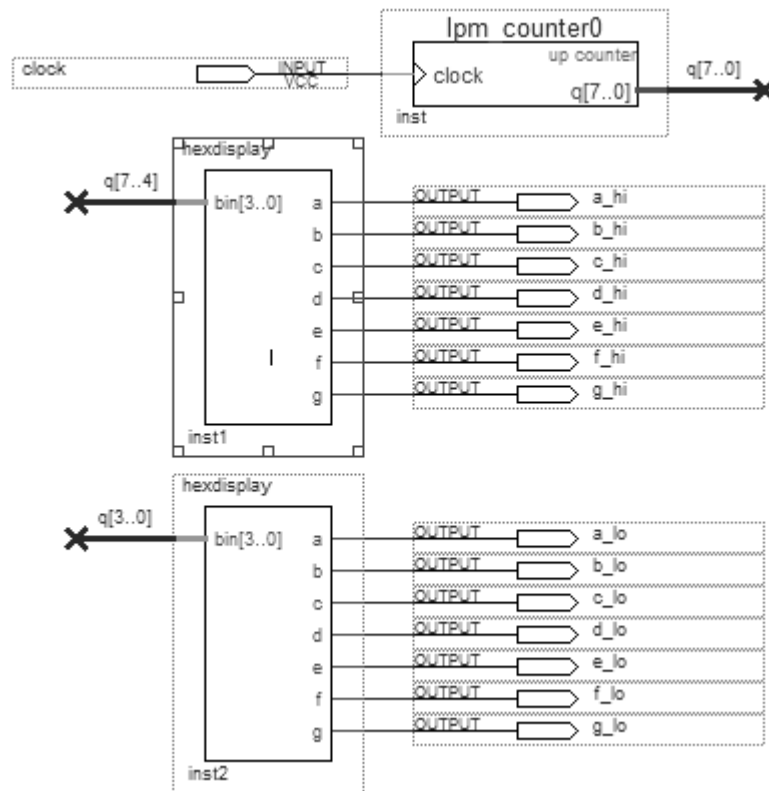
#### 17.4 Mod-256 binary counter and hex decoder/driver



```

SUBDESIGN hex_display          -- AHDL solution
(bin[3..0]                      :INPUT;
 a,b,c,d,e,f,g                 :OUTPUT;)
BEGIN
    TABLE                      -- common-anode truth table
        bin[]=>                a ,b, c, d, e, f, g;
        H"0" =>                 0, 0, 0, 0, 0, 0, 1;
        H"1" =>                 1, 0, 0, 1, 1, 1, 1;
        H"2" =>                 0, 0, 1, 0, 0, 1, 0;
        H"3" =>                 0, 0, 0, 0, 1, 1, 0;
        H"4" =>                 1, 0, 0, 1, 1, 0, 0;
        H"5" =>                 0, 1, 0, 0, 1, 0, 0;
        H"6" =>                 0, 1, 0, 0, 0, 0, 0;
        H"7" =>                 0, 0, 0, 1, 1, 1, 1;
        H"8" =>                 0, 0, 0, 0, 0, 0, 0;
        H"9" =>                 0, 0, 0, 0, 1, 0, 0;
        H"A" =>                 0, 0, 0, 1, 0, 0, 0;
        H"B" =>                 1, 1, 0, 0, 0, 0, 0;

```

```

        H"C" =>      0, 1, 1, 0, 0, 0, 1;
        H"D" =>      1, 0, 0, 0, 0, 1, 0;
        H"E" =>      0, 1, 1, 0, 0, 0, 0;
        H"F" =>      0, 1, 1, 1, 0, 0, 0;

    END TABLE;
END;
```

```

ENTITY hexdisplay IS
PORT ( bin           :IN BIT_VECTOR (3 DOWNTO 0);
      a,b,c,d,e,f,g :OUT BIT );
END hexdisplay;
ARCHITECTURE vhd1 OF hexdisplay IS
SIGNAL segments      :BIT_VECTOR (1 TO 7);
BEGIN
    PROCESS (bin)
    BEGIN
        CASE bin IS
            --      abcdefg
            WHEN X"0" => segments <= "0000001";
            WHEN X"1" => segments <= "1001111";
            WHEN X"2" => segments <= "0010010";
            WHEN X"3" => segments <= "0000110";
            WHEN X"4" => segments <= "1001100";
            WHEN X"5" => segments <= "0100100";
            WHEN X"6" => segments <= "0100000";
            WHEN X"7" => segments <= "0001111";
            WHEN X"8" => segments <= "0000000";
            WHEN X"9" => segments <= "0000100";
            WHEN X"A" => segments <= "0001000";
            WHEN X"B" => segments <= "1100000";
            WHEN X"C" => segments <= "0110001";
            WHEN X"D" => segments <= "1000010";
            WHEN X"E" => segments <= "0110000";
            WHEN X"F" => segments <= "0111000";

        END CASE;
    END PROCESS;
    a <= segments(1);
    b <= segments(2);
    c <= segments(3);
    d <= segments(4);
    e <= segments(5);
    f <= segments(6);
    g <= segments(7);
END vhd1;
```





## 17.5 BCD decoder

```
SUBDESIGN BCD_decoder
(
    bcd[3..0] :INPUT;
    state[9..0], err:OUTPUT;
)
BEGIN
    DEFAULTS
        state[] = B"0000000000";
        err = VCC;
    END DEFAULTS;
    CASE bcd[] IS
        WHEN 0 => state[0] = VCC; err = GND;
        WHEN 1 => state[1] = VCC; err = GND;
        WHEN 2 => state[2] = VCC; err = GND;
        WHEN 3 => state[3] = VCC; err = GND;
        WHEN 4 => state[4] = VCC; err = GND;
        WHEN 5 => state[5] = VCC; err = GND;
        WHEN 6 => state[6] = VCC; err = GND;
        WHEN 7 => state[7] = VCC; err = GND;
        WHEN 8 => state[8] = VCC; err = GND;
        WHEN 9 => state[9] = VCC; err = GND;
    END CASE;
END;
```

```
ENTITY BCD_decoder IS
PORT (bcd :IN INTEGER RANGE 0 TO 15;
      state :OUT BIT_VECTOR (9 DOWNT0 0);
      err :OUT BIT);
END BCD_decoder;
ARCHITECTURE vhd1 OF BCD_decoder IS
BEGIN
    PROCESS (bcd)
    BEGIN
        CASE bcd IS
            WHEN 0 => state <= "0000000001"; err <= '0';
            WHEN 1 => state <= "0000000010"; err <= '0';
            WHEN 2 => state <= "0000000100"; err <= '0';
            WHEN 3 => state <= "0000001000"; err <= '0';
            WHEN 4 => state <= "0000010000"; err <= '0';
            WHEN 5 => state <= "0000100000"; err <= '0';
            WHEN 6 => state <= "0001000000"; err <= '0';
            WHEN 7 => state <= "0010000000"; err <= '0';
            WHEN 8 => state <= "0100000000"; err <= '0';
            WHEN 9 => state <= "1000000000"; err <= '0';
            WHEN OTHERS =>
                state <= "0000000000"; err <= '1';
        END CASE;
    END PROCESS;
END vhd1;
```
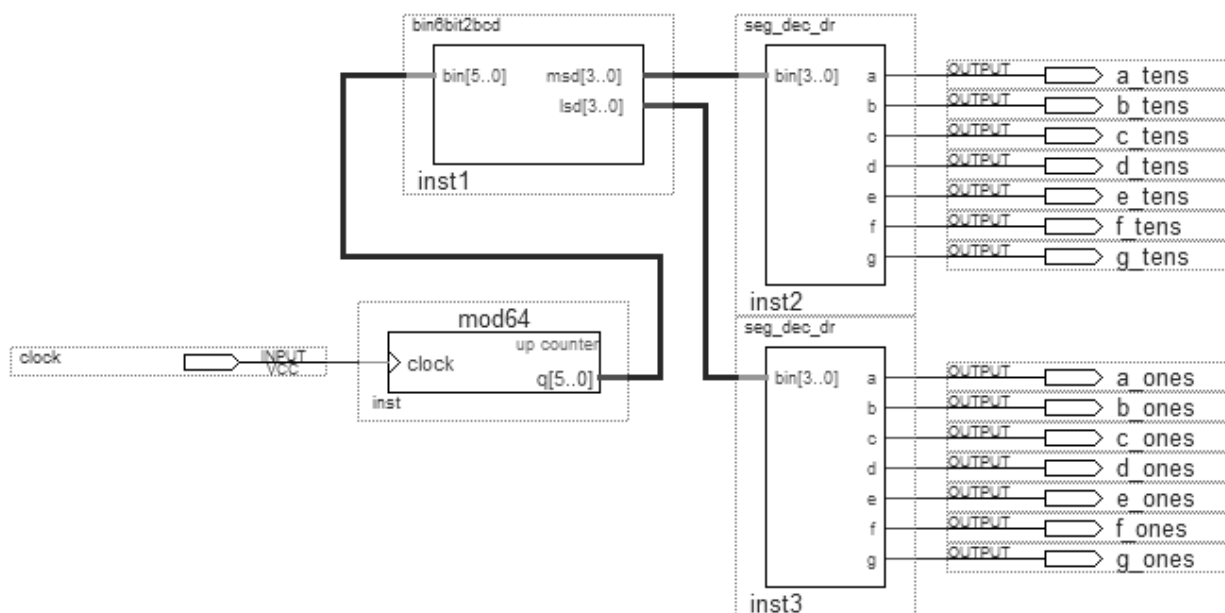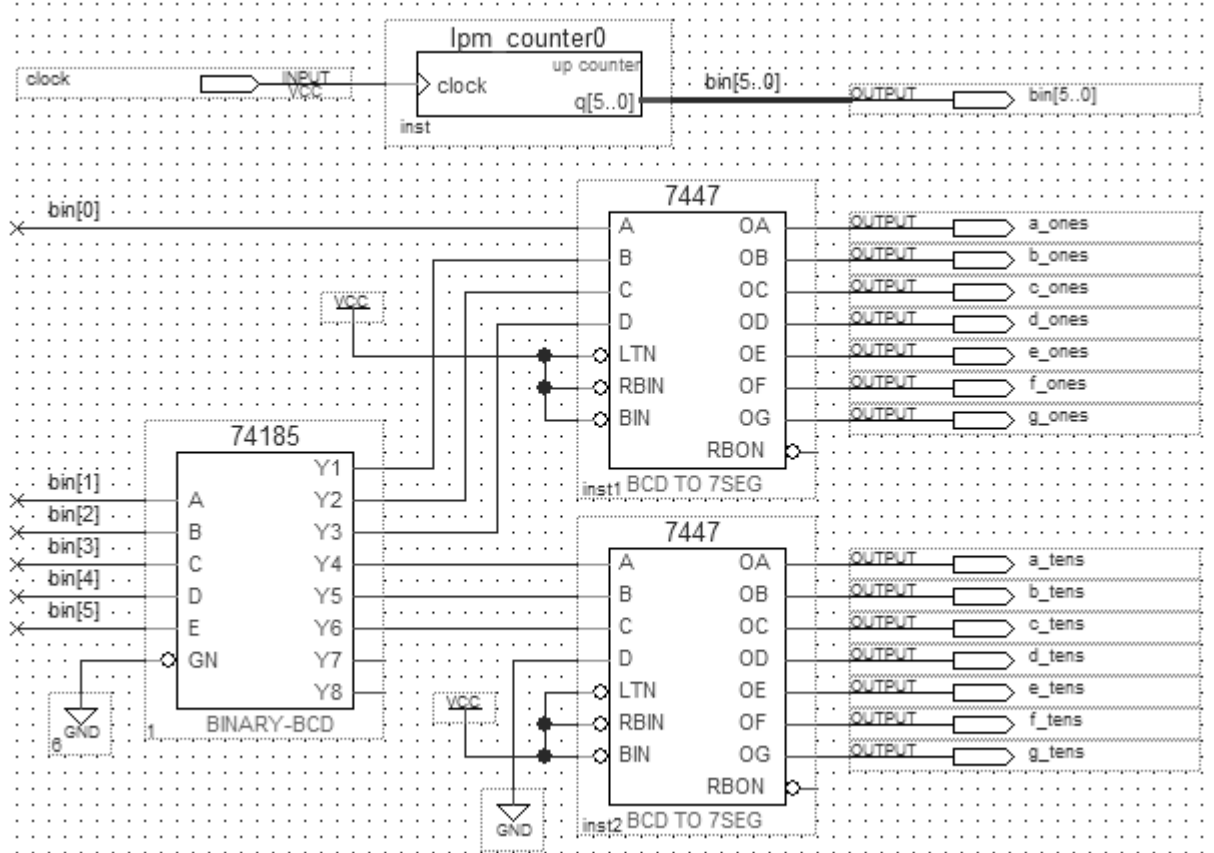
## 17.6 Mod-64 counter with binary-to-BCD converter and display



```

SUBDESIGN bin6bit2bcd
    (bin[5..0]                                :INPUT;
     msd[3..0], lsd[3..0]                    :OUTPUT;)
VARIABLE
    ones[5..0]                                :NODE;    -- to capture the ones digit
BEGIN
    lsd[3..0] = ones[3..0];                    -- output lsd BCD digit
    IF      bin[] >= 60 THEN
        msd[] = 6;                            -- set MSD value
        ones[] = bin[] - 60;                  -- calculate LSD value
    ELSIF bin[] >= 50 THEN
        msd[] = 5;                            ones[] = bin[] - 50;
    ELSIF bin[] >= 40 THEN
        msd[] = 4;                            ones[] = bin[] - 40;
    ELSIF bin[] >= 30 THEN
        msd[] = 3;                            ones[] = bin[] - 30;
    ELSIF bin[] >= 20 THEN
        msd[] = 2;                            ones[] = bin[] - 20;
    ELSIF bin[] >= 10 THEN
        msd[] = 1;                            ones[] = bin[] - 10;
    ELSE
        msd[] = 0;                            ones[] = bin[];
    END IF;
END;

```

```

SUBDESIGN seg_dec_dr    -- common anode
(   bin[3..0]            :INPUT;
   a, b, c, d, e, f, g  :OUTPUT; )
VARIABLE
    seg[7..1]            :NODE;
BEGIN
    (a, b, c, d, e, f, g) = seg[7..1];
    CASE bin[] IS        -- segments  abcdefg
        WHEN H"0"        => seg[] = B"0000001";
        WHEN H"1"        => seg[] = B"1001111";
        WHEN H"2"        => seg[] = B"0010010";
        WHEN H"3"        => seg[] = B"0000110";
        WHEN H"4"        => seg[] = B"1001100";
        WHEN H"5"        => seg[] = B"0100100";
        WHEN H"6"        => seg[] = B"1100000";
        WHEN H"7"        => seg[] = B"0001111";
        WHEN H"8"        => seg[] = B"0000000";
        WHEN H"9"        => seg[] = B"0001100";
        WHEN OTHERS      => seg[] = B"1111111";
    END CASE;
END;

```

```

ENTITY bin6bit2bcd IS
PORT (    bin          :IN INTEGER RANGE 0 TO 63;
        msd, lsd      :OUT INTEGER RANGE 0 TO 9);
END bin6bit2bcd;
ARCHITECTURE vhd1 OF bin6bit2bcd IS
BEGIN
PROCESS (bin)          -- bin change invokes process
BEGIN
    IF    bin >= 60      THEN
        msd <= 6;      -- set MSD value
        lsd <= bin - 60; -- calculate LSD value
    ELSIF bin >= 50      THEN
        msd <= 5;
        lsd <= bin - 50;
    ELSIF bin >= 40      THEN
        msd <= 4;
        lsd <= bin - 40;
    ELSIF bin >= 30      THEN
        msd <= 3;
        lsd <= bin - 30;
    ELSIF bin >= 20      THEN
        msd <= 2;
        lsd <= bin - 20;
    ELSIF bin >= 10      THEN
        msd <= 1;
        lsd <= bin - 10;
    ELSE
        msd <= 0;
        lsd <= bin;
    END IF;
END PROCESS;
END vhd1;

```

```

ENTITY seg_dec_dr IS -- common anode
PORT (bin          :IN BIT_VECTOR (3 DOWNT0 0);
      a, b, c, d, e, f, g :OUT BIT);
END seg_dec_dr;

ARCHITECTURE vhd1 OF seg_dec_dr IS
BEGIN
PROCESS (bin)
VARIABLE seg          :BIT_VECTOR (0 TO 6);
BEGIN
    a <= seg(0);
    b <= seg(1);
    c <= seg(2);
    d <= seg(3);
    e <= seg(4);
    f <= seg(5);
    g <= seg(6);

    CASE bin IS
        -- segments  abcdefg
        WHEN "0000" => seg := "0000001";
        WHEN "0001" => seg := "1001111";
        WHEN "0010" => seg := "0010010";
        WHEN "0011" => seg := "0000110";
        WHEN "0100" => seg := "1001100";
        WHEN "0101" => seg := "0100100";
        WHEN "0110" => seg := "1100000";
        WHEN "0111" => seg := "0001111";
        WHEN "1000" => seg := "0000000";
        WHEN "1001" => seg := "0001100";
        WHEN OTHERS => seg := "1111111";
    END CASE;
END PROCESS;
END vhd1;

```

## 17.7 Memory decoder

```

SUBDESIGN mem_decode
(a[15..0], memr, memw           :INPUT;
 cs[5..0]                       :OUTPUT;)
BEGIN
If (memr == GND & memw == VCC) # (memr == VCC & memw == GND) THEN
  IF      a[] >= H"0000" & a[] <= H"03FF" THEN cs[] = B"111110";
  ELSIF a[] >= H"0400" & a[] <= H"07FF" THEN cs[] = B"111101";
  ELSIF a[] >= H"0800" & a[] <= H"0BFF" THEN cs[] = B"111011";
  ELSIF a[] >= H"0C00" & a[] <= H"0FFF" THEN cs[] = B"110111";
  ELSIF a[] >= H"E800" & a[] <= H"EBFF" THEN cs[] = B"101111";
  ELSIF a[] >= H"EC00" & a[] <= H"FFFF" THEN cs[] = B"011111";
  ELSE
    cs[] = B"111111";
  END IF;
ELSE
  cs[] = B"111111";
END IF;
END;

```

```

ENTITY mem_decode IS
PORT (a           :IN INTEGER RANGE 0 TO 65535;
      memr, memw  :IN BIT;
      cs          :OUT BIT_VECTOR (5 DOWNT0 0) );
END mem_decode;
ARCHITECTURE vhd1 OF mem_decode IS
SIGNAL mem_en      :BIT;
BEGIN
mem_en <= memr XOR memw;
PROCESS (a, mem_en)
BEGIN
  IF mem_en = '1' THEN
    IF      a >= 16#0000# AND a <= 16#03FF# THEN
      cs <= "111110";
    ELSIF a >= 16#0400# AND a <= 16#07FF# THEN
      cs <= "111101";
    ELSIF a >= 16#0800# AND a <= 16#0BFF# THEN
      cs <= "111011";
    ELSIF a >= 16#0C00# AND a <= 16#0FFF# THEN
      cs <= "110111";
    ELSIF a >= 16#E800# AND a <= 16#EBFF# THEN
      cs <= "101111";
    ELSIF a >= 16#EC00# AND a <= 16#FFFF# THEN
      cs <= "011111";
    ELSE
      cs <= "111111";
    END IF;
  ELSE
    cs <= "111111";
  END IF;
END PROCESS;
END vhd1;

```

## 17.8 State decoder

```

SUBDESIGN  state_decoder          -- AHDL solution
(
    in[6..0]      :INPUT;
    y[9..1]       :OUTPUT;      )

BEGIN
    DEFAULTS
        y[] = B"000000000";      -- default inactive
    END DEFAULTS;
    TABLE          -- selected states to decode
        in[] =>    y[];
        10  =>    B"000000001";
        20  =>    B"000000010";
        30  =>    B"000000100";
        40  =>    B"000001000";
        50  =>    B"000010000";
        60  =>    B"000100000";
        70  =>    B"001000000";
        80  =>    B"010000000";
        90  =>    B"100000000";
    END TABLE;
END;

```

```


ENTITY  state_decoder  IS          -- VHDL solution
PORT (
    input      :IN INTEGER RANGE 0 TO 99;
    y          :OUT BIT_VECTOR (9 DOWNT0 1)      );
END state_decoder;

ARCHITECTURE  vhdl  OF  state_decoder  IS
BEGIN
    PROCESS (input)                -- invoke on input change
    BEGIN
        CASE  input  IS          -- decoded states
            WHEN  10      =>      y <= "000000001";
            WHEN  20      =>      y <= "000000010";
            WHEN  30      =>      y <= "000000100";
            WHEN  40      =>      y <= "000001000";
            WHEN  50      =>      y <= "000010000";
            WHEN  60      =>      y <= "000100000";
            WHEN  70      =>      y <= "001000000";
            WHEN  80      =>      y <= "010000000";
            WHEN  90      =>      y <= "100000000";
            WHEN  OTHERS  =>      y <= "000000000";
        END CASE;
    END PROCESS;
END vhdl;

```

## Unit 18 Encoder Applications

### 18.1 Encoder and display

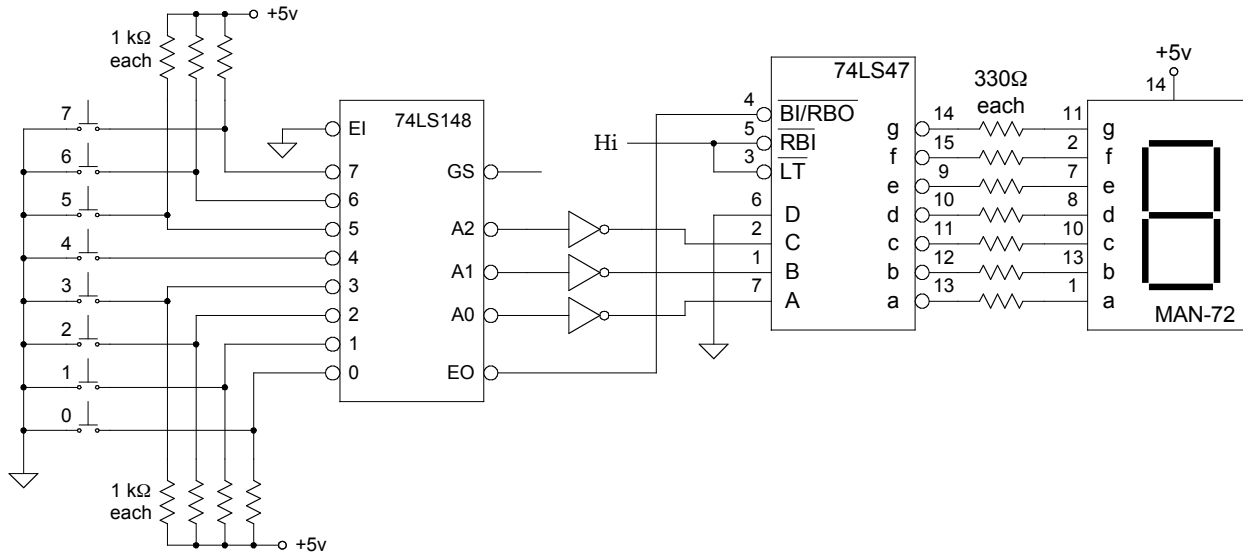

### 18.2 HDL 74148 encoder

```

SUBDESIGN  encoder_ahdl          -- AHDL solution
(
    in[7..0], ei                  :INPUT;
    a[2..0], gs, eo               :OUTPUT;
)

BEGIN
IF !ei THEN                        -- active-low enable
    TABLE
        -- priority encoder with inverted outputs
        in[]          =>  a[], gs, eo;
        B"11111111"   =>  B"111", VCC, GND;
        B"11111110"   =>  B"111", GND, VCC;
        B"1111110X"   =>  B"110", GND, VCC;
        B"111110XX"   =>  B"101", GND, VCC;
        B"11110XXX"   =>  B"100", GND, VCC;
        B"1110XXXX"   =>  B"011", GND, VCC;
        B"110XXXXX"   =>  B"010", GND, VCC;
        B"10XXXXXX"   =>  B"001", GND, VCC;
        B"0XXXXXXX"   =>  B"000", GND, VCC;
    END TABLE;
ELSE a[] = B"111"; gs = VCC; eo = VCC;    -- disabled
END IF;
END;

```



```

ENTITY encoder_vhdl IS          -- VHDL solution
PORT (
    input      :IN BIT_VECTOR (7 DOWNTO 0);
    ei         :IN BIT;
    a          :OUT BIT_VECTOR (2 DOWNTO 0);
    gs, eo     :OUT BIT
);
END encoder_vhdl;


ARCHITECTURE vhd1 OF encoder_vhdl IS
BEGIN
PROCESS (input, ei)
BEGIN

    IF ei = '0' THEN            -- active-low enable
        -- check highest priority input first
        IF      input(7) = '0' THEN
            a <= "000"; gs <= '0'; eo <= '1';
        ELSIF   input(6) = '0' THEN
            a <= "001"; gs <= '0'; eo <= '1';
        ELSIF   input(5) = '0' THEN
            a <= "010"; gs <= '0'; eo <= '1';
        ELSIF   input(4) = '0' THEN
            a <= "011"; gs <= '0'; eo <= '1';
        ELSIF   input(3) = '0' THEN
            a <= "100"; gs <= '0'; eo <= '1';
        ELSIF   input(2) = '0' THEN
            a <= "101"; gs <= '0'; eo <= '1';
        ELSIF   input(1) = '0' THEN
            a <= "110"; gs <= '0'; eo <= '1';
        ELSIF   input(0) = '0' THEN
            a <= "111"; gs <= '0'; eo <= '1';
        ELSE
            -- no input
            a <= "111"; gs <= '1'; eo <= '0';
        END IF;
    ELSE
        -- disabled
        a <= "111"; gs <= '1'; eo <= '1';
    END IF;

END PROCESS;
END vhd1;

```

### 18.3 Variable self-stopping counter

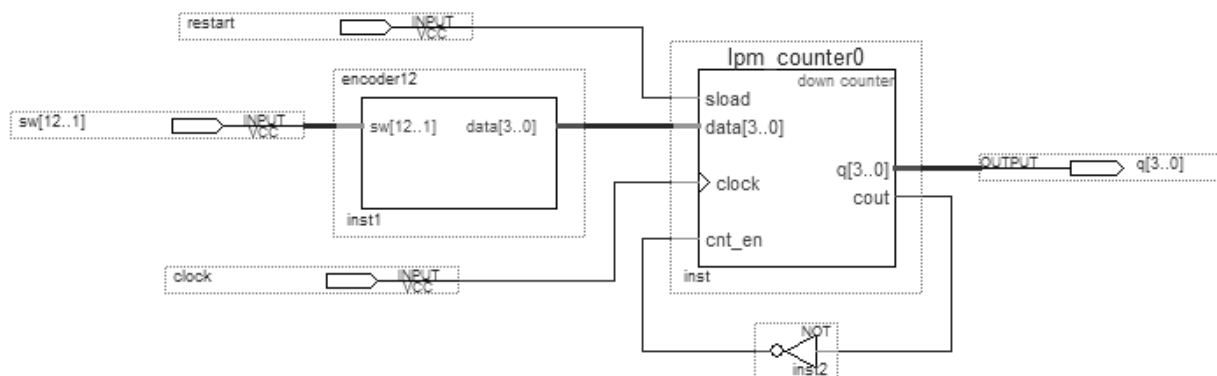

```

SUBDESIGN  encoder12
(
    sw[12..1]      :INPUT;
    data[3..0]     :OUTPUT;
)
BEGIN
    TABLE
        sw[]      =>  data[];
--          CBA987654321
    B"111111111111" =>  B"0000";
    B"111111111110" =>  B"0001";
    B"111111111110X" =>  B"0010";
    B"111111111110XX" =>  B"0011";
    B"1111111110XXX" =>  B"0100";
    B"111111110XXXX" =>  B"0101";
    B"11111110XXXXXX" =>  B"0110";
    B"111110XXXXXXX" =>  B"0111";
    B"11110XXXXXXX"  =>  B"1000";
    B"1110XXXXXXX"   =>  B"1001";
    B"110XXXXXXX"    =>  B"1010";
    B"10XXXXXXX"     =>  B"1011";
    B"0XXXXXXX"      =>  B"1100";
    END TABLE;
END;

```


```

ENTITY encoder12 IS
PORT (      sw              :IN BIT_VECTOR (12 DOWNT0 1);
        data              :OUT INTEGER RANGE 0 TO 15 );
END encoder12;

ARCHITECTURE vhd1 OF encoder12 IS
BEGIN
data <=
    12 WHEN sw(12) = '0' ELSE
    11 WHEN sw(11) = '0' ELSE
    10 WHEN sw(10) = '0' ELSE
    9 WHEN sw(9) = '0' ELSE
    8 WHEN sw(8) = '0' ELSE
    7 WHEN sw(7) = '0' ELSE
    6 WHEN sw(6) = '0' ELSE
    5 WHEN sw(5) = '0' ELSE
    4 WHEN sw(4) = '0' ELSE
    3 WHEN sw(3) = '0' ELSE
    2 WHEN sw(2) = '0' ELSE
    1 WHEN sw(1) = '0' ELSE
    0 ;
END vhd1;

```

#### 18.4 BCD encoder

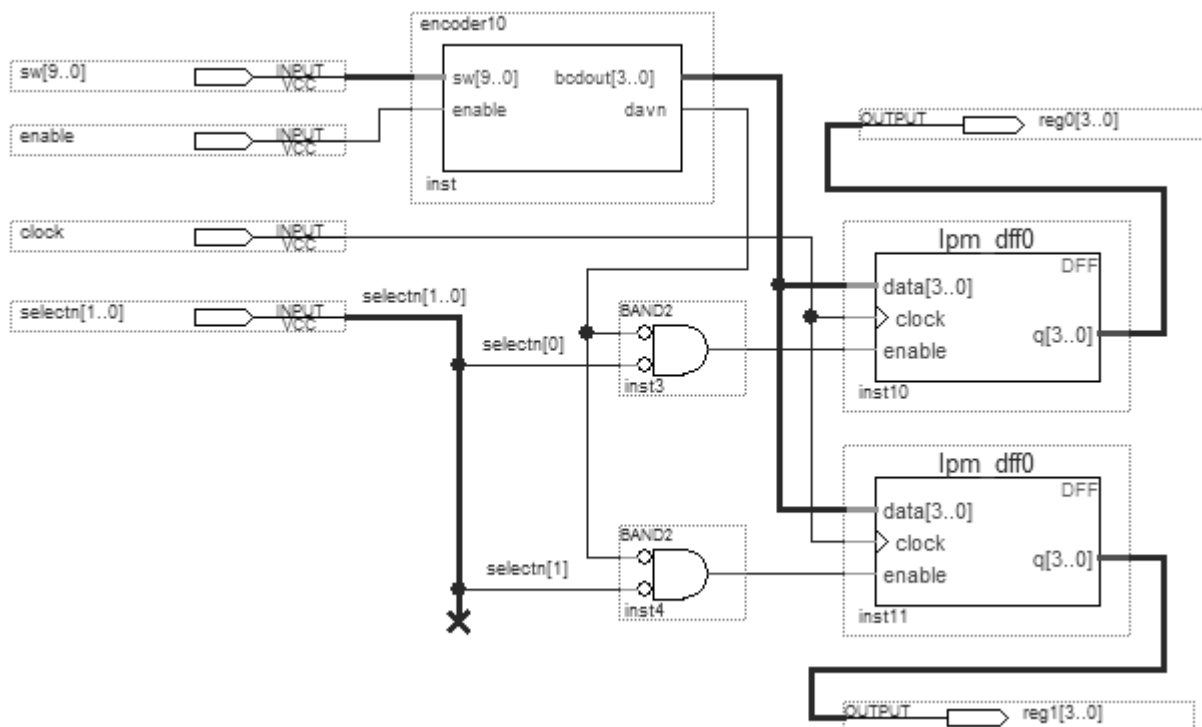

```

SUBDESIGN  encoder10
(
    sw[9..0], enable      :INPUT;
    bcdout[3..0], davn     :OUTPUT;
)
BEGIN
    TABLE
        sw[], enable      =>      bcdout[], davn;
        B"XXXXXXXXXX", 0   =>      B"0000", 1;
        B"111111111", 1   =>      B"0000", 1;
        B"111111110", 1   =>      B"0000", 0;
        B"11111110X", 1   =>      B"0001", 0;
        B"1111110XX", 1   =>      B"0010", 0;
        B"111110XXX", 1   =>      B"0011", 0;
        B"11110XXXX", 1   =>      B"0100", 0;
        B"1110XXXXX", 1   =>      B"0101", 0;
        B"110XXXXXX", 1   =>      B"0110", 0;
        B"10XXXXXXXX", 1   =>      B"0111", 0;
        B"0XXXXXXXX", 1   =>      B"1000", 0;
        B"0XXXXXXXX", 1   =>      B"1001", 0;
    END TABLE;
END;

```


```

ENTITY  encoder10  IS
PORT (      sw      :IN BIT_VECTOR (9 DOWNTO 0);
          enable     :IN BIT;
          bcdout     :OUT BIT_VECTOR (3 DOWNTO 0);
          davn       :OUT BIT );
END encoder10;

ARCHITECTURE vhd1 OF encoder10 IS
BEGIN
    davn <= '1' WHEN (enable = '0' OR sw = "111111111")
           ELSE '0';
    bcdout <=
        "0000" WHEN enable = '0' ELSE
        "1001" WHEN sw(9) = '0' ELSE
        "1000" WHEN sw(8) = '0' ELSE
        "0111" WHEN sw(7) = '0' ELSE
        "0110" WHEN sw(6) = '0' ELSE
        "0101" WHEN sw(5) = '0' ELSE
        "0100" WHEN sw(4) = '0' ELSE
        "0011" WHEN sw(3) = '0' ELSE
        "0010" WHEN sw(2) = '0' ELSE
        "0001" WHEN sw(1) = '0' ELSE
        "0000";
END vhd1;

```

## 18.5 Scanning encoder

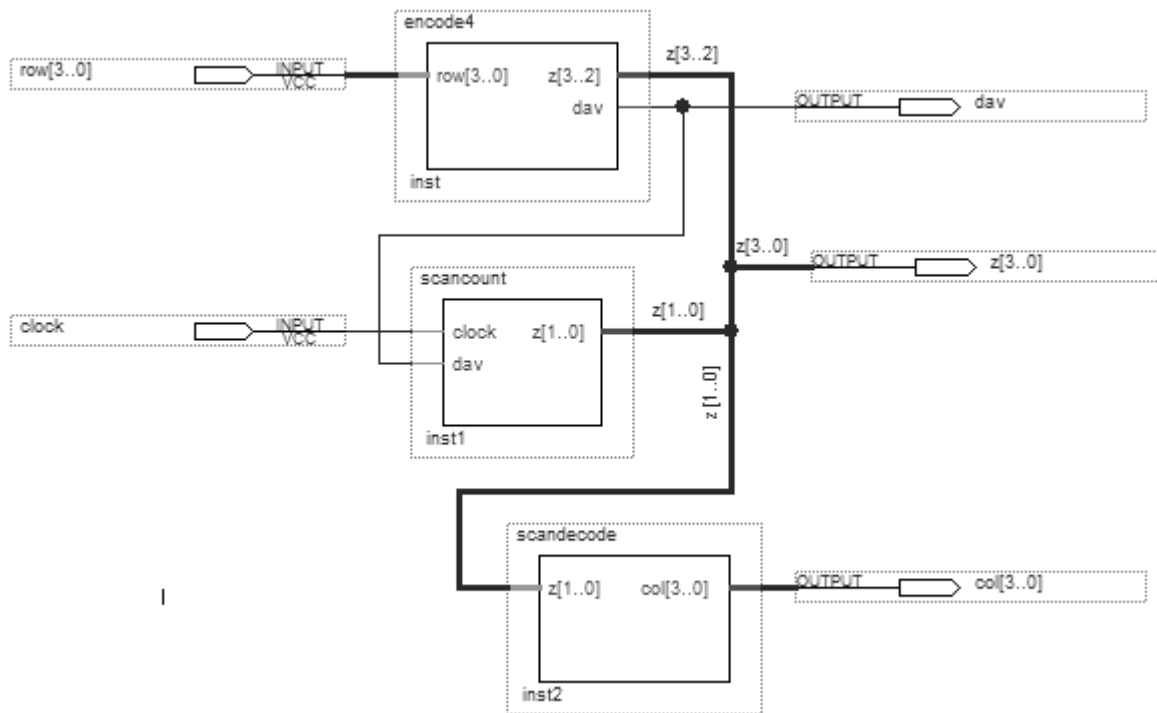

```

SUBDESIGN encode4
(
    row[3..0]          :INPUT;
    z[3..2]            :OUTPUT;
    dav                :OUTPUT;
)
BEGIN
    TABLE
        row[] =>      z[], dav;
        B"1111"      =>  B"00", 0;
        B"1110"      =>  B"00", 1;
        B"110X"      =>  B"01", 1;
        B"10XX"      =>  B"10", 1;
        B"0XXX"      =>  B"11", 1;
    END TABLE;
END;

```

```

SUBDESIGN scancount
(
    clock, dav          :INPUT;
    z[1..0]            :OUTPUT;
)
VARIABLE
    z[1..0]            :DFF;
BEGIN
    z[].clk = clock;

    IF (dav == GND) THEN
        z[].d = z[].q + 1;
    ELSE
        z[].d = z[].q;
    END IF;
END;

```

```

SUBDESIGN scandecode
(
    z[1..0]            :INPUT;
    col[3..0]          :OUTPUT;
)
BEGIN
    CASE z[] IS
        WHEN 0          =>  col[] = B"1110";
        WHEN 1          =>  col[] = B"1101";
        WHEN 2          =>  col[] = B"1011";
        WHEN 3          =>  col[] = B"0111";
    END CASE;
END;

```

```

ENTITY encode4 IS
PORT (row      :IN BIT_VECTOR (3 DOWNTO 0);
      z        :OUT BIT_VECTOR (3 DOWNTO 2);
      dav      :OUT BIT);
END encode4;
ARCHITECTURE vhd1 OF encode4 IS
BEGIN
z <=  "00" WHEN row(0) = '0' ELSE
      "01" WHEN row(1) = '0' ELSE
      "10" WHEN row(2) = '0' ELSE
      "11" WHEN row(3) = '0' ELSE
      "00";
dav <= '0' WHEN row = "1111" ELSE '1';
END;

```

```

ENTITY scancount IS
PORT (clock, dav      :IN BIT;
      z              :OUT INTEGER RANGE 0 TO 3);
END scancount;
ARCHITECTURE vhd1 OF scancount IS
BEGIN
PROCESS (clock)
VARIABLE count :INTEGER RANGE 0 TO 3;
BEGIN
    IF (clock'EVENT AND clock = '1') THEN
        IF (dav = '0') THEN
            count := count + 1;
        END IF;
    END IF;
    z <= count;
END PROCESS;
END;

```


```

ENTITY scandecode IS
PORT (z      :IN INTEGER RANGE 0 TO 3;
      col    :OUT BIT_VECTOR (3 DOWNTO 0));
END scandecode;
ARCHITECTURE vhd1 OF scandecode IS
BEGIN
PROCESS (z)
BEGIN
    CASE z IS
        WHEN 0    => col <= "1110";
        WHEN 1    => col <= "1101";
        WHEN 2    => col <= "1011";
        WHEN 3    => col <= "0111";
    END CASE;
END PROCESS;
END;


```

## Unit 19 Multiplexer Applications

### 19.1 Serial data word generator

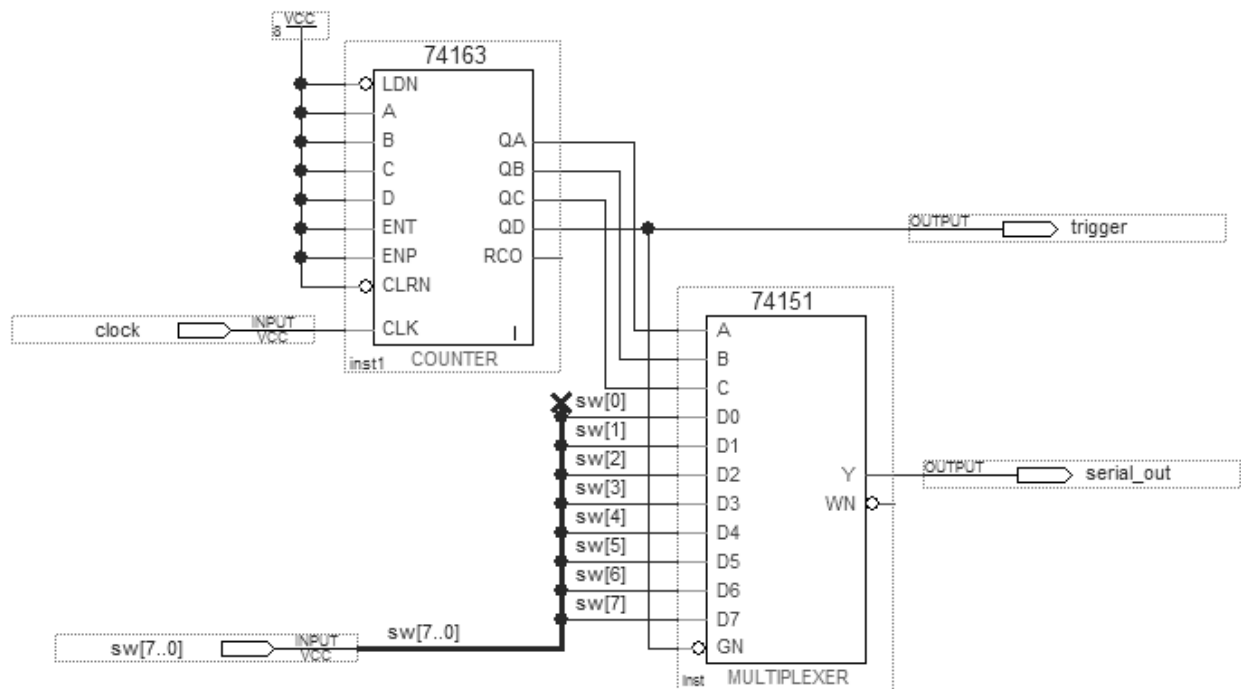


### 19.2 Prime number detector

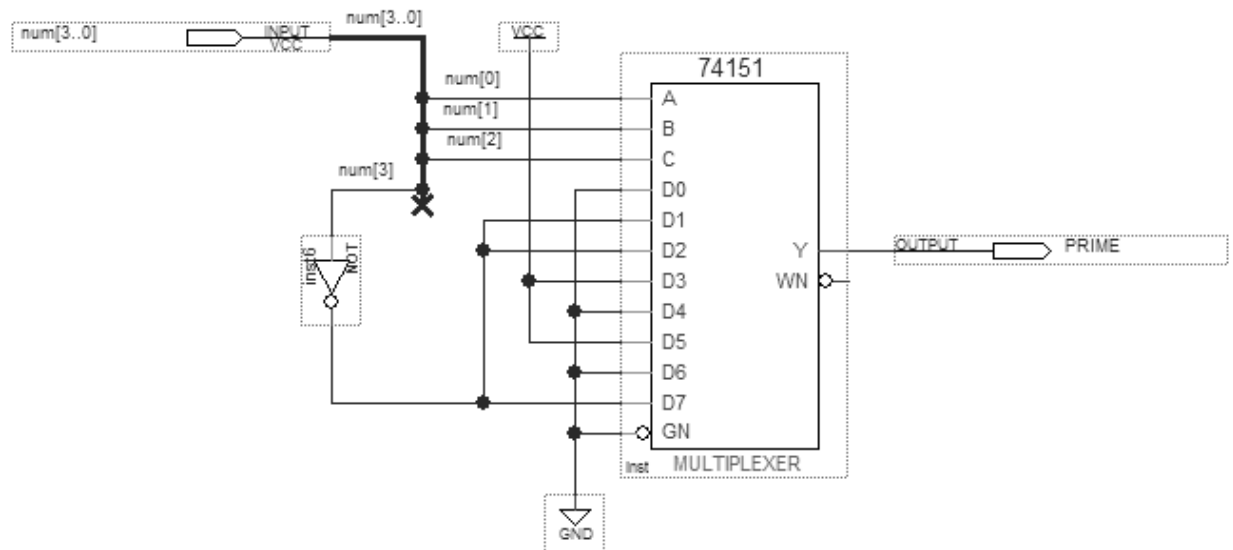




### 19.3 Variable frequency divider

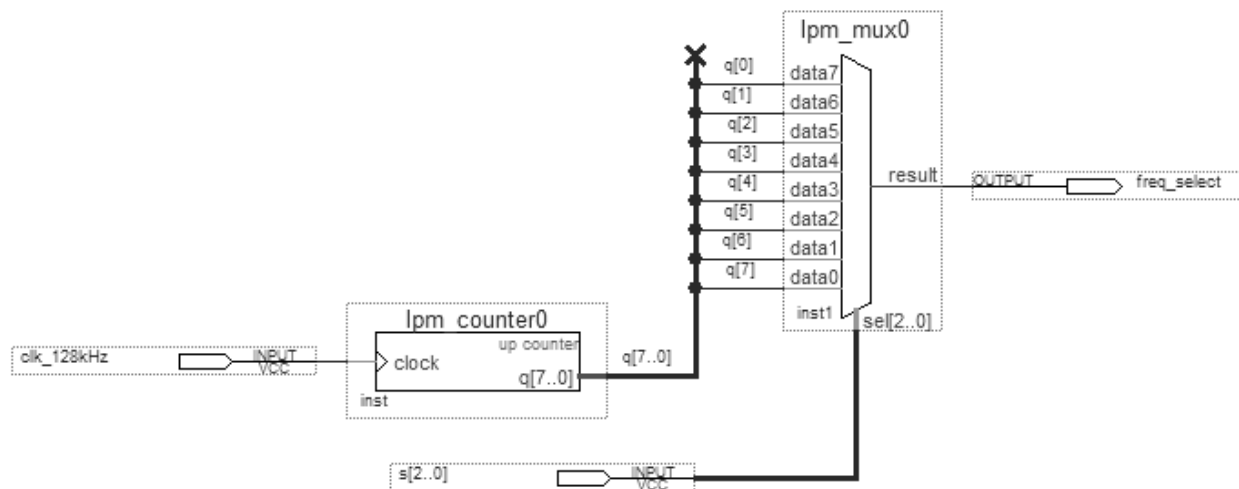

### 19.4 Multiplexed BCD display

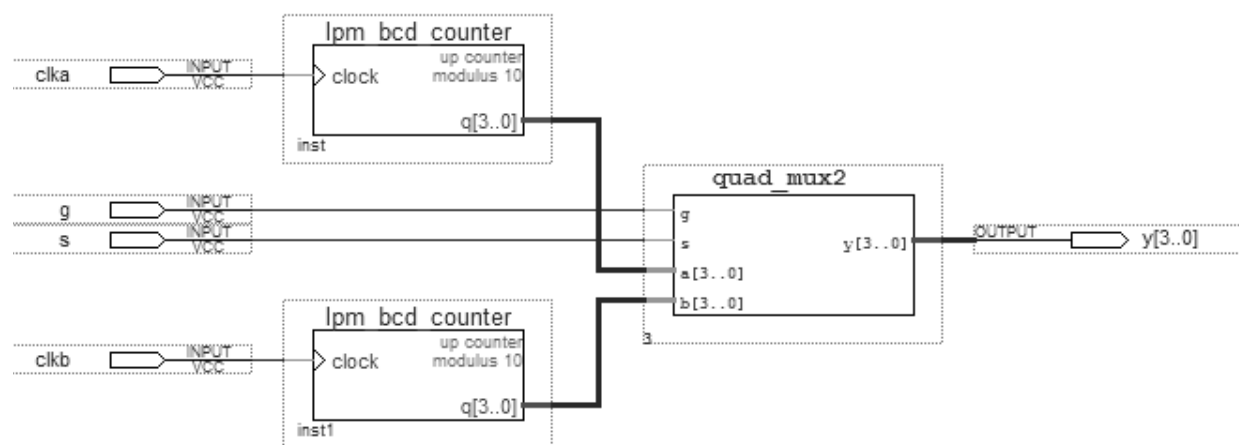

```

SUBDESIGN      quad_mux2
(g, s, a[3..0], b[3..0])      :INPUT;
y[3..0]        :OUTPUT;
BEGIN
    IF g THEN
        CASE s IS
            WHEN 0 => y[] = a[];
            WHEN 1 => y[] = b[];
        END CASE;
    ELSE y[] = H"F";
    END IF;
END;

```

```

ENTITY quad_mux2 IS
PORT (      g, s : IN BIT;
        a, b : IN BIT_VECTOR (3 DOWNT0 0);
        y      : OUT BIT_VECTOR (3 DOWNT0 0) );
END quad_mux2;

ARCHITECTURE vhd1 OF quad_mux2 IS
BEGIN
    PROCESS (g, s, a, b)
    BEGIN
        IF g = '1' THEN
            CASE s IS
                WHEN '0' => y <= a;
                WHEN '1' => y <= b;
            END CASE;
        ELSE y <= "1111";
        END IF;
    END PROCESS;
END vhd1;

```

## 19.5 Quad, 3-channel MUX

```

SUBDESIGN quad_mux3 -- AHDL solution
(
    s[1..0], a[3..0], b[3..0], c[3..0] :INPUT;
    y[3..0] :OUTPUT;
)

BEGIN
    CASE s[] IS -- input channel select
        WHEN 0 => y[] = 0; -- disabled
        WHEN 1 => y[] = a[]; -- channel A
        WHEN 2 => y[] = b[]; -- channel B
        WHEN 3 => y[] = c[]; -- channel C
    END CASE;
END;

```


```

ENTITY quad_mux3 IS
    PORT (
        s      :IN INTEGER RANGE 0 TO 3;
        a, b, c :IN BIT_VECTOR (3 DOWNTO 0);
        y      :OUT BIT_VECTOR (3 DOWNTO 0)
    );
END quad_mux3;

ARCHITECTURE vhd1 OF quad_mux3 IS
BEGIN
    PROCESS (s, a, b, c)
    BEGIN
        CASE s IS
            WHEN 0 => y <= "0000";
            WHEN 1 => y <= a;
            WHEN 2 => y <= b;
            WHEN 3 => y <= c;
        END CASE;
    END PROCESS;
END vhd1;

```

## 19.6 Alarm system

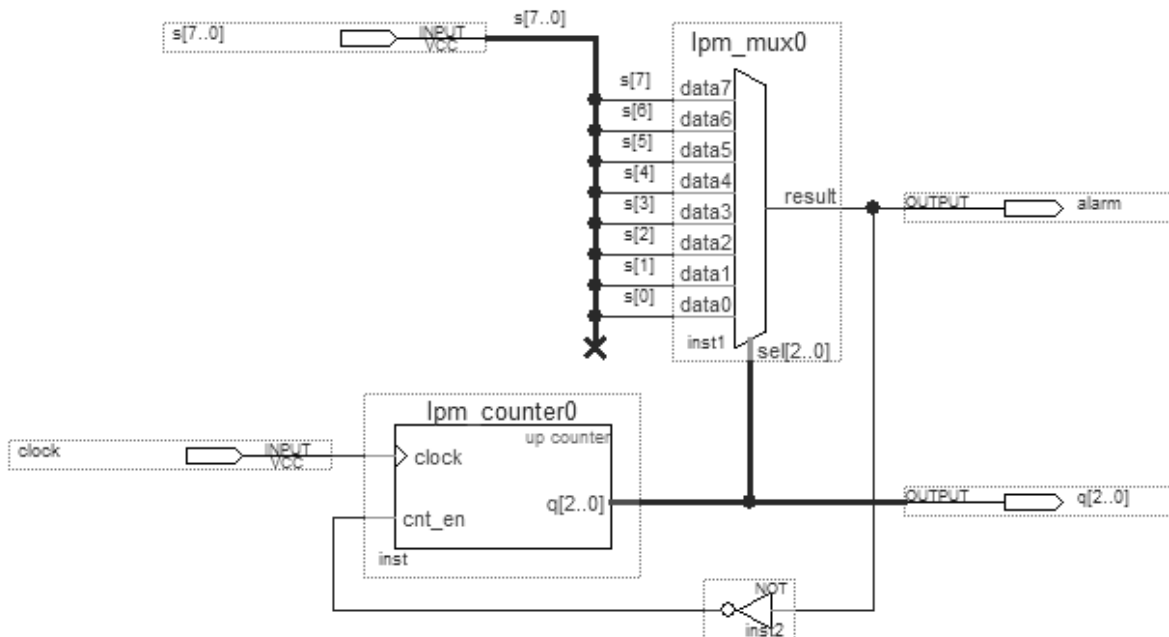

## 19.7 16-channel, 1-bit MUX

```
SUBDESIGN mux16chan      -- AHDL solution
(
    d[15..0]              :INPUT;
    sel[3..0]             :INPUT;
    y                     :OUTPUT;
)

BEGIN
    CASE sel[] IS        -- select input channel
        WHEN 0 => y = d[0];
        WHEN 1 => y = d[1];
        WHEN 2 => y = d[2];
        WHEN 3 => y = d[3];
        WHEN 4 => y = d[4];
        WHEN 5 => y = d[5];
        WHEN 6 => y = d[6];
        WHEN 7 => y = d[7];
        WHEN 8 => y = d[8];
        WHEN 9 => y = d[9];
        WHEN 10 => y = d[10];
        WHEN 11 => y = d[11];
        WHEN 12 => y = d[12];
        WHEN 13 => y = d[13];
        WHEN 14 => y = d[14];
        WHEN 15 => y = d[15];
    END CASE;
END;
```

```

ENTITY mux16chan IS      -- VHDL solution
PORT (
    d          :IN BIT_VECTOR (15 DOWNT0 0);
    sel        :IN INTEGER RANGE 0 TO 15;
    y          :OUT BIT );
END mux16chan;

ARCHITECTURE vhd1 OF mux16chan IS
BEGIN

PROCESS (d, sel)        -- monitor inputs
    BEGIN


        CASE sel IS      -- select input channel
            WHEN 0 => y <= d(0);
            WHEN 1 => y <= d(1);
            WHEN 2 => y <= d(2);
            WHEN 3 => y <= d(3);
            WHEN 4 => y <= d(4);
            WHEN 5 => y <= d(5);
            WHEN 6 => y <= d(6);
            WHEN 7 => y <= d(7);
            WHEN 8 => y <= d(8);
            WHEN 9 => y <= d(9);
            WHEN 10 => y <= d(10);
            WHEN 11 => y <= d(11);
            WHEN 12 => y <= d(12);
            WHEN 13 => y <= d(13);
            WHEN 14 => y <= d(14);
            WHEN 15 => y <= d(15);
        END CASE;

    END PROCESS;
END vhd1;


```

## Unit 20 Demultiplexer Applications

### 20.1 Clock DMUX

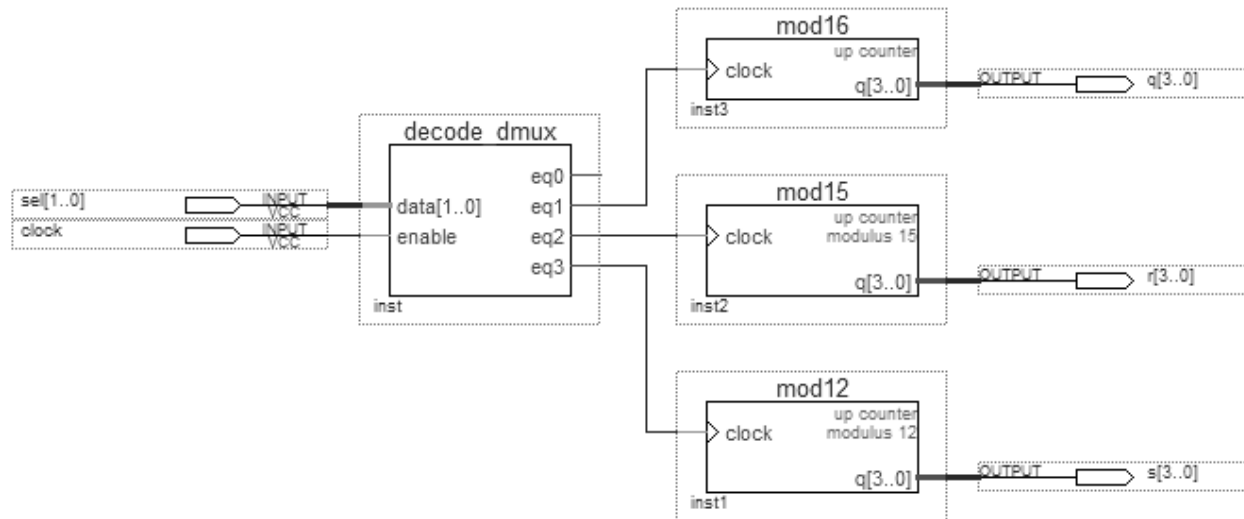

### 20.2 BCD counter demultiplexer

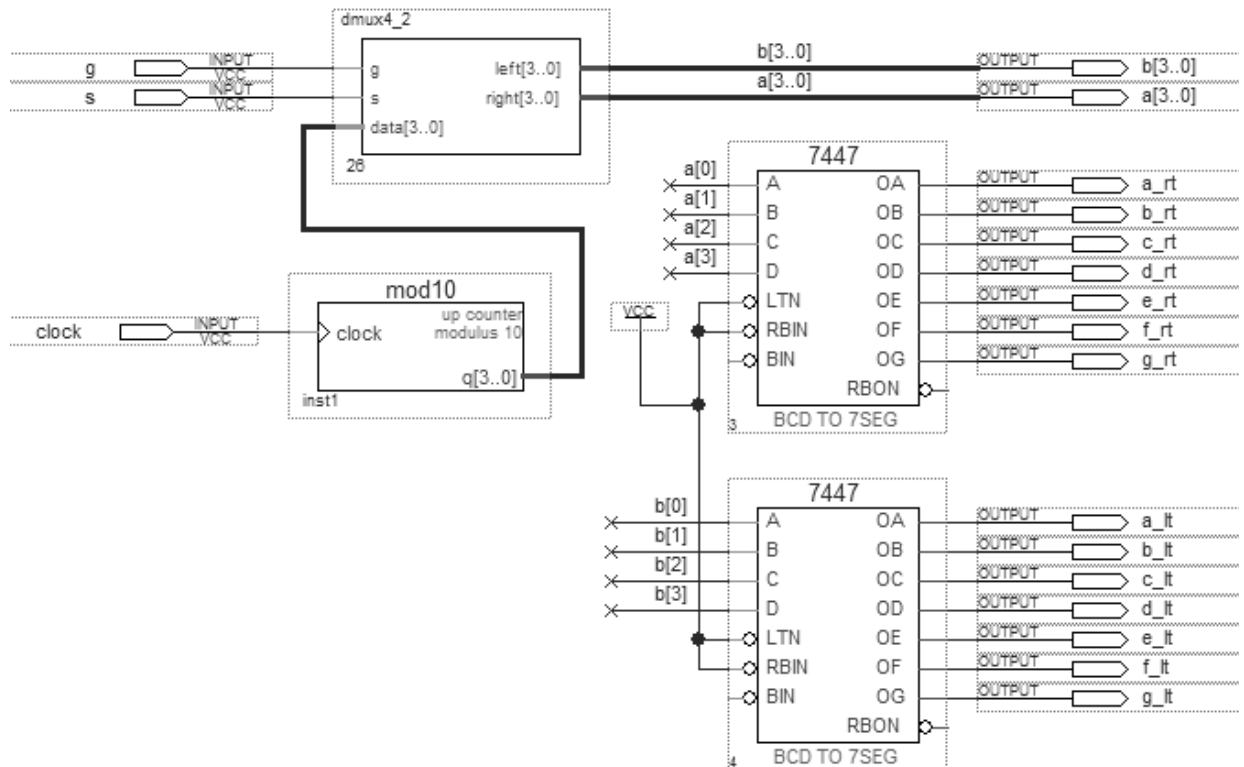

```

SUBDESIGN  dmux4_2
(
    g, s, data[3..0]           :INPUT;
    left[3..0], right[3..0]    :OUTPUT;
)
BEGIN
    DEFAULTS
        left[] = H"F";
        right[] = H"F";
    END DEFAULTS;
    IF !g THEN
        CASE s IS
            WHEN 0 => left[] = data[];
            WHEN 1 => right[] = data[];
        END CASE;
    END IF;
END;

```


```

ENTITY dmux4_2 IS
PORT (
    g, s           :IN BIT;
    data           :IN BIT_VECTOR (3 DOWNTO 0);
    left, right    :OUT BIT_VECTOR (3 DOWNTO
0) );
END dmux4_2;

ARCHITECTURE vhd1 OF dmux4_2 IS
BEGIN
    PROCESS (g, s, data)
    BEGIN
        IF g = '1' THEN
            left <= "1111";  right <= "1111";
        ELSIF s = '0' THEN
            left <= data;    right <= "1111";
        ELSE
            left <= "1111";  right <= data;
        END IF;
    END PROCESS;
END vhd1;

```

## 20.3 Alarm indicator

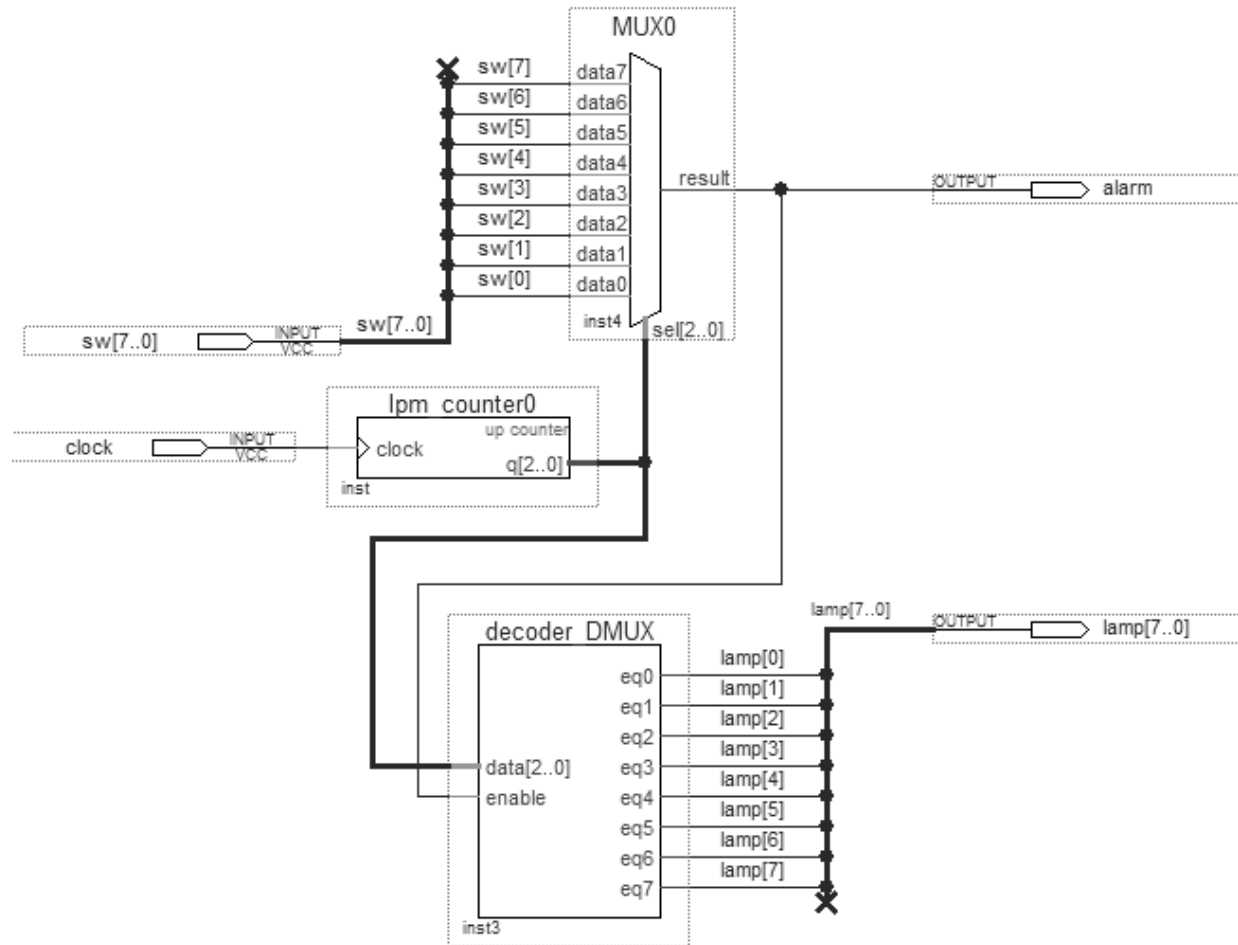

## 20.4 8-channel, 1-bit DMUX

```

SUBDESIGN demux_ahdl      -- AHDL solution
(
    sel[2..0]              :INPUT;
    data, en               :INPUT;
    y[7..0]                :OUTPUT;
)

BEGIN
    DEFAULTS
        y[] = B"00000000";
        -- inactive outputs are low
    END DEFAULTS;

```



```

        IF en THEN -- active-high enable
            CASE sel[] IS -- select output channel
                WHEN 0 => y[0] = data;
                WHEN 1 => y[1] = data;
                WHEN 2 => y[2] = data;
                WHEN 3 => y[3] = data;
                WHEN 4 => y[4] = data;
                WHEN 5 => y[5] = data;
                WHEN 6 => y[6] = data;
                WHEN 7 => y[7] = data;
            END CASE;
        END IF;
    END;

```

```

ENTITY demux_vhdl IS -- VHDL solution
PORT (
    sel :IN BIT_VECTOR (2 DOWNTO 0);
    data, en :IN BIT;
    y :OUT BIT_VECTOR (7 DOWNTO 0)
);
END demux_vhdl;

ARCHITECTURE vhd1 OF demux_vhdl IS
BEGIN
    PROCESS (data, sel, en)
    BEGIN

        IF en = '1' THEN -- active-high enable


            CASE sel IS -- select output channel
                WHEN "000" => y <= "0000000" & data;
                -- concatenate output bit vector
                WHEN "001" => y <= "000000" & data & '0';
                WHEN "010" => y <= "00000" & data & "00";
                WHEN "011" => y <= "0000" & data & "000";
                WHEN "100" => y <= "000" & data & "0000";
                WHEN "101" => y <= "00" & data & "00000";
                WHEN "110" => y <= '0' & data & "000000";
                WHEN "111" => y <= data & "0000000";
            END CASE;

            ELSE y <= "00000000"; -- disabled output
            END IF;

        END PROCESS;
    END vhd1;

```

## 20.5 2-channel data transmitter

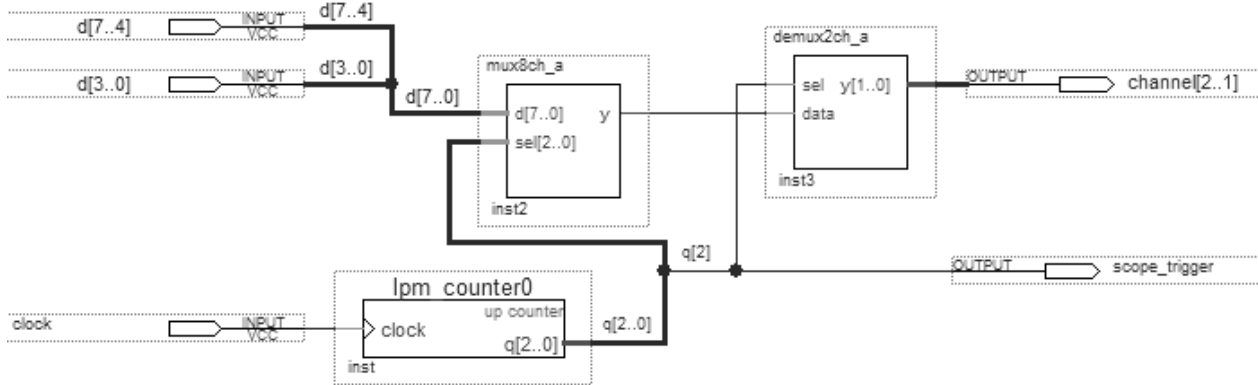

```


SUBDESIGN mux8ch_a
(d[7..0]      :INPUT;
 sel[2..0]    :INPUT;
 y            :OUTPUT;)
BEGIN
    CASE sel[] IS
        WHEN 0 => y = d[0];
        WHEN 1 => y = d[1];
        WHEN 2 => y = d[2];
        WHEN 3 => y = d[3];
        WHEN 4 => y = d[4];
        WHEN 5 => y = d[5];
        WHEN 6 => y = d[6];
        WHEN 7 => y = d[7];
    END CASE;
END;

```

```

SUBDESIGN demux2ch_a
(sel, data    :INPUT;
 y[1..0]      :OUTPUT;)
BEGIN
    DEFAULTS
        y[] = B"00";
    END DEFAULTS;
    CASE sel IS
        WHEN 0 => y[0] = data;
        WHEN 1 => y[1] = data;
    END CASE;
END;

```

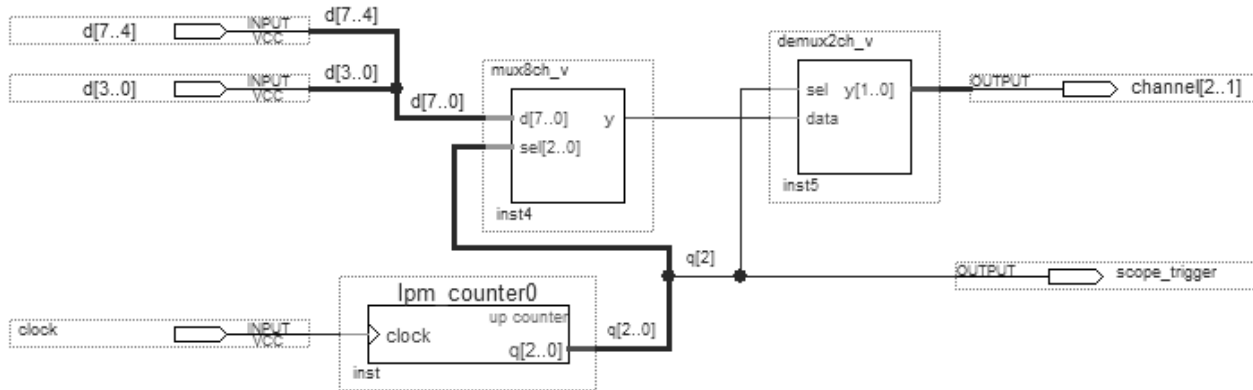

```

ENTITY mux8ch_v IS
PORT (d      :IN BIT_VECTOR (7 DOWNTO 0);
      sel    :IN INTEGER RANGE 0 TO 7;
      y      :OUT BIT);
END mux8ch_v;
ARCHITECTURE vhd1 OF mux8ch_v IS
BEGIN
    PROCESS (d, sel)
    BEGIN
        CASE sel IS
            WHEN 0 => y <= d(0);
            WHEN 1 => y <= d(1);
            WHEN 2 => y <= d(2);
            WHEN 3 => y <= d(3);
            WHEN 4 => y <= d(4);
            WHEN 5 => y <= d(5);
            WHEN 6 => y <= d(6);
            WHEN 7 => y <= d(7);
        END CASE;
    END PROCESS;
END vhd1;

```


```

ENTITY demux2ch_v IS
PORT (sel, data :IN BIT;
      y         :OUT BIT_VECTOR (1 DOWNTO 0));
END demux2ch_v;
ARCHITECTURE vhd1 OF demux2ch_v IS
BEGIN
    PROCESS (sel, data)
    BEGIN
        CASE sel IS
            WHEN '0' => y <= ('0' & data);
            WHEN '1' => y <= (data & '0');
        END CASE;
    END PROCESS;
END vhd1;

```

## Unit 21 Magnitude Comparator Applications

### 21.1 Count detector

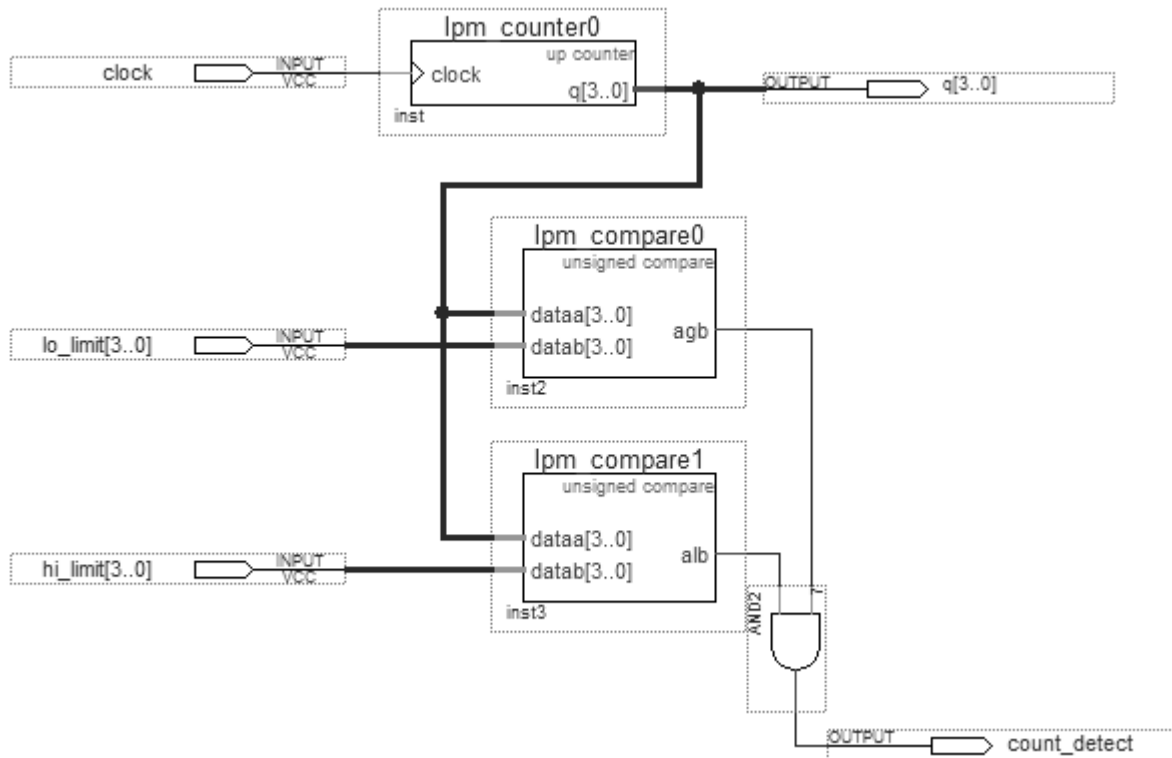

### 21.2 Adjustable range detector

```

SUBDESIGN range_detect                                -- AHDL solution
(value[4..0], r[1..0]                                :INPUT;
ltr, gtr, rng                                         :OUTPUT;)
VARIABLE
    lo_value[4..0]                                    :node;
    hi_value[4..0]                                    :node;
BEGIN
    DEFAULTS
        ltr = GND;
        gtr = GND;
        rng = GND;
    END DEFAULTS;
    CASE r[] IS
        -- set range limits
        WHEN 0 => lo_value[] = 16; hi_value[] = 16;
        WHEN 1 => lo_value[] = 15; hi_value[] = 17;
        WHEN 2 => lo_value[] = 14; hi_value[] = 18;
        WHEN 3 => lo_value[] = 13; hi_value[] = 19;
    END CASE;

```

```

-- determine active output
IF      value[] < lo_value[] THEN ltr = VCC;
ELSIF   value[] > hi_value[] THEN gtr = VCC;
ELSE                                         rng = VCC;
END IF;
END;
```


```

ENTITY range_detect IS          -- VHDL solution
PORT (      value              :IN INTEGER RANGE 0 TO 31;
          r                    :IN BIT_VECTOR (1 DOWNTO 0);
          ltr, gtr, rng        :OUT BIT      );
END range_detect;


ARCHITECTURE vhdl OF range_detect IS
SIGNAL      lo_value           :INTEGER RANGE 0 TO 31;
SIGNAL      hi_value           :INTEGER RANGE 0 TO 31;
BEGIN
  PROCESS (value, r)
  BEGIN
    CASE r IS
      -- set range limits
      WHEN "00" => lo_value <= 16; hi_value <= 16;
      WHEN "01" => lo_value <= 15; hi_value <= 17;
      WHEN "10" => lo_value <= 14; hi_value <= 18;
      WHEN "11" => lo_value <= 13; hi_value <= 19;
    END CASE;

    -- determine active output
    IF      value < lo_value THEN
      ltr <= '1'; gtr <= '0'; rng <= '0';
    ELSIF   value > hi_value THEN
      ltr <= '0'; gtr <= '1'; rng <= '0';
    ELSE
      ltr <= '0'; gtr <= '0'; rng <= '1';
    END IF;
  END PROCESS;
END vhdl;
```

### 21.3 Variable modulus counter

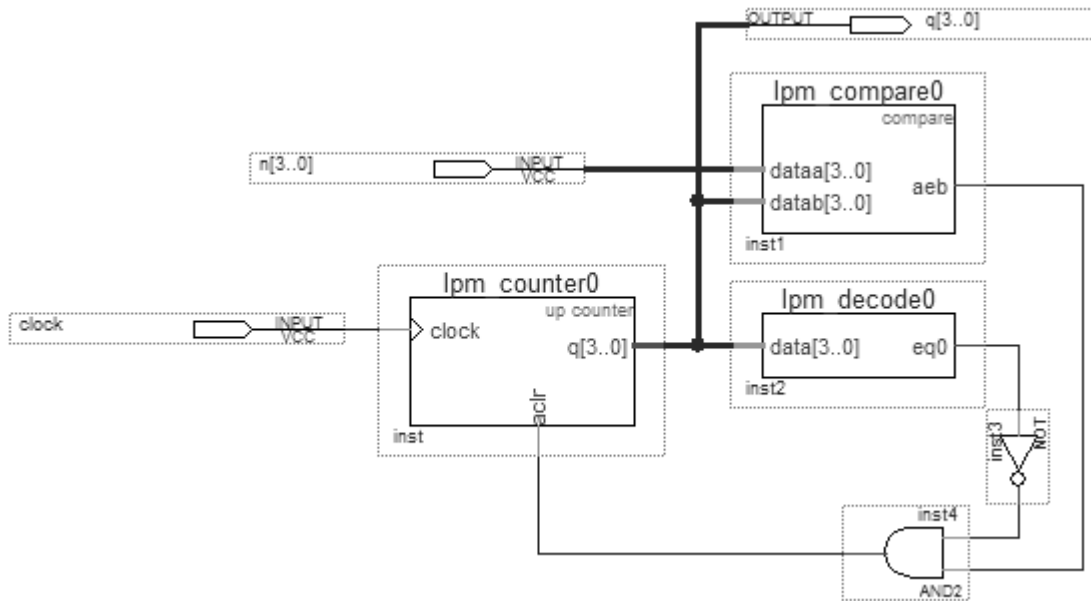

### 21.4 Variable self-stopping counter

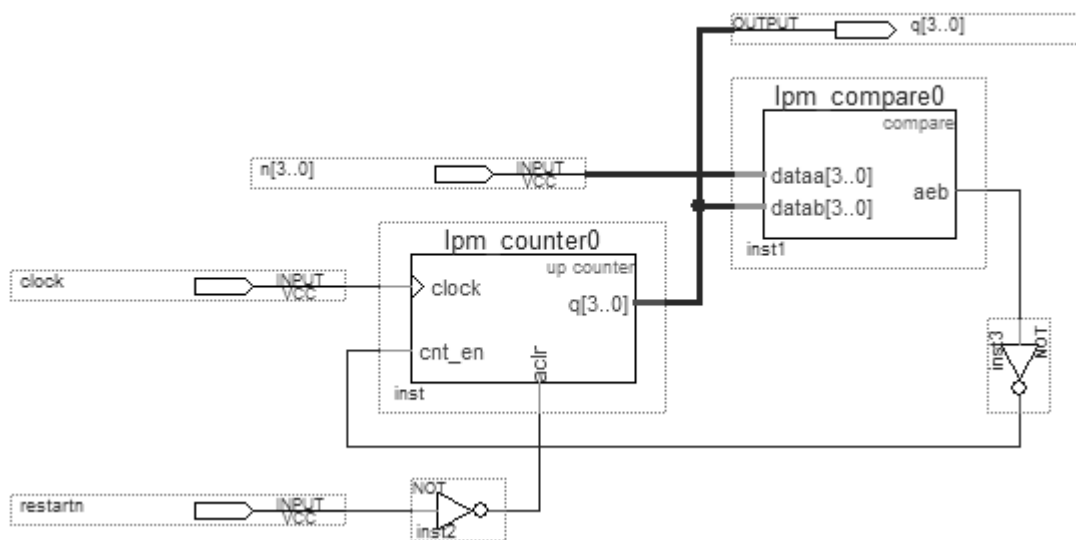

## 21.5 Number selector

```
SUBDESIGN  num_select          -- AHDL solution
(
    f, a[3..0], b[3..0]        :INPUT;
    y[3..0]                    :OUTPUT;
)

VARIABLE
    agtb                        :NODE;    -- buried node

BEGIN

    agtb = a[] > b[];           -- hi if a>b

    y[] = a[] & !(f $ agtb) # b[] & (f $ agtb);
        -- MUX function to select a or b input
        -- XNOR selects a & XOR selects b

END;
```

```
ENTITY  num_select IS          -- VHDL solution
PORT (    f          :IN BIT;
          a, b        :IN INTEGER RANGE 0 TO 15;
          y            :OUT INTEGER RANGE 0 TO 15    );
END num_select;

ARCHITECTURE vhdl OF num_select IS
SIGNAL    agtb        :BIT;
SIGNAL    sel_a        :BIT;

BEGIN

    agtb <= '1'        WHEN (a > b) ELSE '0';
        -- hi if a>b

    sel_a <= '1' WHEN ((f XOR agtb) = '0') ELSE '0';
        -- determine when to select input a

    y <= a WHEN (sel_a = '1') ELSE b;
        -- MUX function selects a or b input


END vhdl;
```

## Unit 22 Digital/Analog and Analog/Digital Conversion

### 22.1 Digital-to-analog converter (see Fig. 22-1)

#### Digital to Analog Conversion

Hex input	Decimal in	Analog out
0	0	0.00
1	1	0.01
2	2	0.02
3	3	0.03
4	4	0.04
8	8	0.08
A	10	0.10
F	15	0.15
10	16	0.16
1C	28	0.28
20	32	0.32
33	51	0.51
40	64	0.64
64	100	1.00
80	128	1.28
99	153	1.53
A5	165	1.65
D2	210	2.10
E7	231	2.31
FF	255	2.55

 




## 22.2 Analog-to-digital converter (see Fig. 22-2)

WARNING: Do not exceed 5.0 V on analog input!

### Analog to Digital Conversion

Analog in	Decimal out	Hex out
0.000	0	0
0.100	5	5
0.400	20	14
0.500	26	19
0.515	26	1A
0.530	27	1B
0.750	38	26
0.950	49	30
1.000	51	33
1.500	77	4C
1.800	92	5C
2.000	102	66
2.500	128	80
3.000	154	99
3.500	179	B3
3.750	192	C0
4.000	205	CC
4.320	221	DD
4.500	230	E6
5.000	255	FF

 

### 22.3 Free-running ADC with span adjust (see Fig. 22-3)

resolution = 15 mV

full-scale voltage = 15 mV  $\times$  255 = 3.825 V


$V_{REF} = 256 \times 15 \text{ mV} = 3.84 \text{ V}$

adjust pot to  $V_{REF}/2 = 3.84 \text{ V} \div 2 = 1.92 \text{ V}$


$[R_2/(R_1+R_2)][5 \text{ V}] = 0.5 \text{ V} \rightarrow \text{use } R_2=1.1 \text{ k}\Omega \text{ \& } R_1 = 10 \text{ k}\Omega$

#### Analog to Digital Conversion

Analog in	Decimal out	Hex out
0.000	0	0
0.100	0	0
0.400	0	0
0.500	0	0
0.515	1	1
0.530	2	2
0.750	17	10
0.950	30	1D
1.000	33	21
1.500	67	42
1.800	87	56
2.000	100	64
2.500	133	85
3.000	167	A6
3.500	200	C8
3.750	217	D8
4.000	233	E9
4.320	255	FE
4.500	255	FF
5.000	255	FF

 

## 22.4 Digital voltmeter

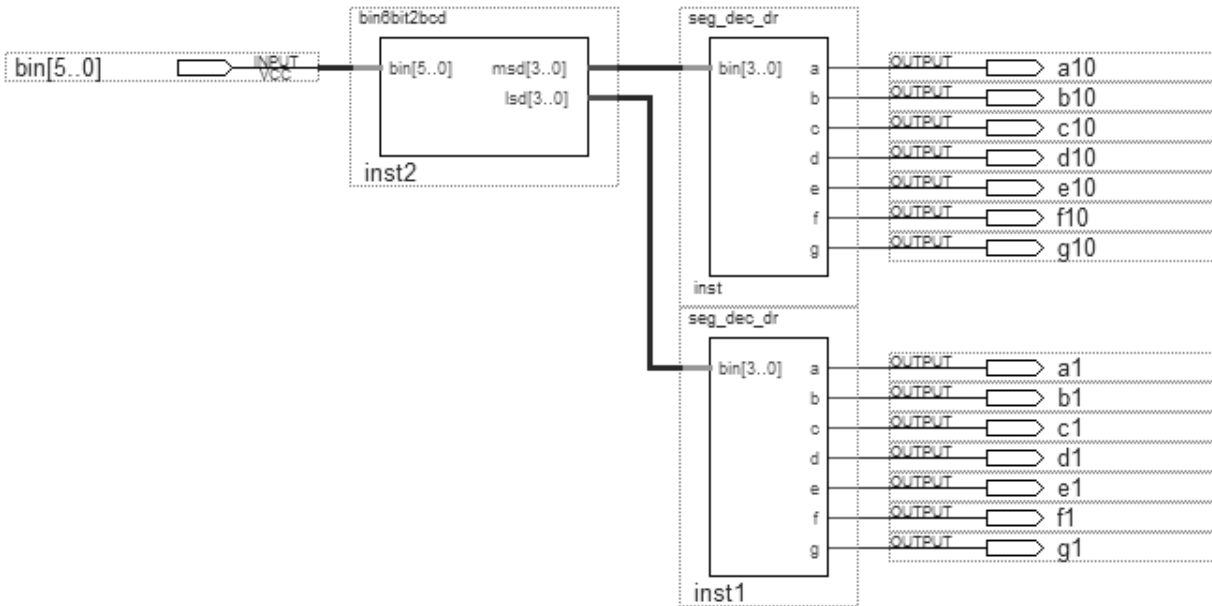

```

SUBDESIGN bin6bit2bcd
    (bin[5..0] :INPUT;
     msd[3..0], lsd[3..0] :OUTPUT;)
VARIABLE
    ones[5..0] :NODE;    -- to capture the ones digit
BEGIN
    lsd[3..0] = ones[3..0];    -- output lsd BCD digit
    IF bin[] >= 60 THEN
        msd[] = 6;    -- set MSD value
        ones[] = bin[] - 60;    -- calculate LSD value
    ELSIF bin[] >= 50 THEN
        msd[] = 5;    ones[] = bin[] - 50;
    ELSIF bin[] >= 40 THEN
        msd[] = 4;    ones[] = bin[] - 40;
    ELSIF bin[] >= 30 THEN
        msd[] = 3;    ones[] = bin[] - 30;
    ELSIF bin[] >= 20 THEN
        msd[] = 2;    ones[] = bin[] - 20;
    ELSIF bin[] >= 10 THEN
        msd[] = 1;    ones[] = bin[] - 10;
    ELSE
        msd[] = 0;    ones[] = bin[];
    END IF;
END;


```

```

ENTITY bin6bit2bcd IS
PORT (    bin           :IN INTEGER RANGE 0 TO 63;
        msd, lsd       :OUT INTEGER RANGE 0 TO 9);
END bin6bit2bcd;
ARCHITECTURE vhd1 OF bin6bit2bcd IS
BEGIN
PROCESS (bin)          -- bin change invokes process
BEGIN
    IF    bin >= 60      THEN
        msd <= 6;      -- set MSD value
        lsd <= bin - 60; -- calculate LSD value
    ELSIF bin >= 50      THEN
        msd <= 5;
        lsd <= bin - 50;
    ELSIF bin >= 40      THEN
        msd <= 4;
        lsd <= bin - 40;
    ELSIF bin >= 30      THEN
        msd <= 3;
        lsd <= bin - 30;
    ELSIF bin >= 20      THEN
        msd <= 2;
        lsd <= bin - 20;
    ELSIF bin >= 10      THEN
        msd <= 1;
        lsd <= bin - 10;
    ELSE
        msd <= 0;
        lsd <= bin;
    END IF;
END PROCESS;
END vhd1;

```

## 22.5 Digitized sine-wave generator

 

```
-- AHDL solution
SUBDESIGN data_gen
(
    q[5..0]    :INPUT;
    d[7..0]    :OUTPUT;
)

BEGIN
-- D/A input values at
-- 10 degree increments

    TABLE
    q[] => d[];
    0   => 150;
    1   => 167;
    2   => 184;
    3   => 200;
    4   => 214;
    5   => 227;
    6   => 237;
    7   => 244;
    8   => 248;
    9   => 250;
    10  => 248;
    11  => 244;
    12  => 237;
```

```
    13  => 227;
    14  => 214;
    15  => 200;
    16  => 184;
    17  => 167;
    18  => 150;
    19  => 133;
    20  => 116;
    21  => 100;
    22  => 86;
    23  => 73;
    24  => 63;
    25  => 56;
    26  => 52;
    27  => 50;
    28  => 52;
    29  => 56;
    30  => 63;
    31  => 73;
    32  => 86;
    33  => 100;
    34  => 116;
    35  => 133;
    END TABLE;
END;
```

```

ENTITY data_gen IS          -- VHDL solution
PORT (      q              :IN INTEGER RANGE 0 TO 35;
          d              :OUT INTEGER RANGE 0 TO 255    );
END data_gen;


ARCHITECTURE vhdl OF data_gen IS
BEGIN
    -- D/A input values at 10 degree increments

    WITH q      SELECT
    d    <=      150 WHEN 0,
              167 WHEN 1,
              184 WHEN 2,
              200 WHEN 3,
              214 WHEN 4,
              227 WHEN 5,
              237 WHEN 6,
              244 WHEN 7,
              248 WHEN 8,
              250 WHEN 9,
              248 WHEN 10,
              244 WHEN 11,
              237 WHEN 12,
              227 WHEN 13,
              214 WHEN 14,
              200 WHEN 15,
              184 WHEN 16,
              167 WHEN 17,
              150 WHEN 18,
              133 WHEN 19,
              116 WHEN 20,
              100 WHEN 21,
              86  WHEN 22,
              73  WHEN 23,
              63  WHEN 24,
              56  WHEN 25,
              52  WHEN 26,
              50  WHEN 27,
              52  WHEN 28,
              56  WHEN 29,
              63  WHEN 30,
              73  WHEN 31,
              86  WHEN 32,
              100 WHEN 33,
              116 WHEN 34,
              133 WHEN 35;

END vhdl;

```
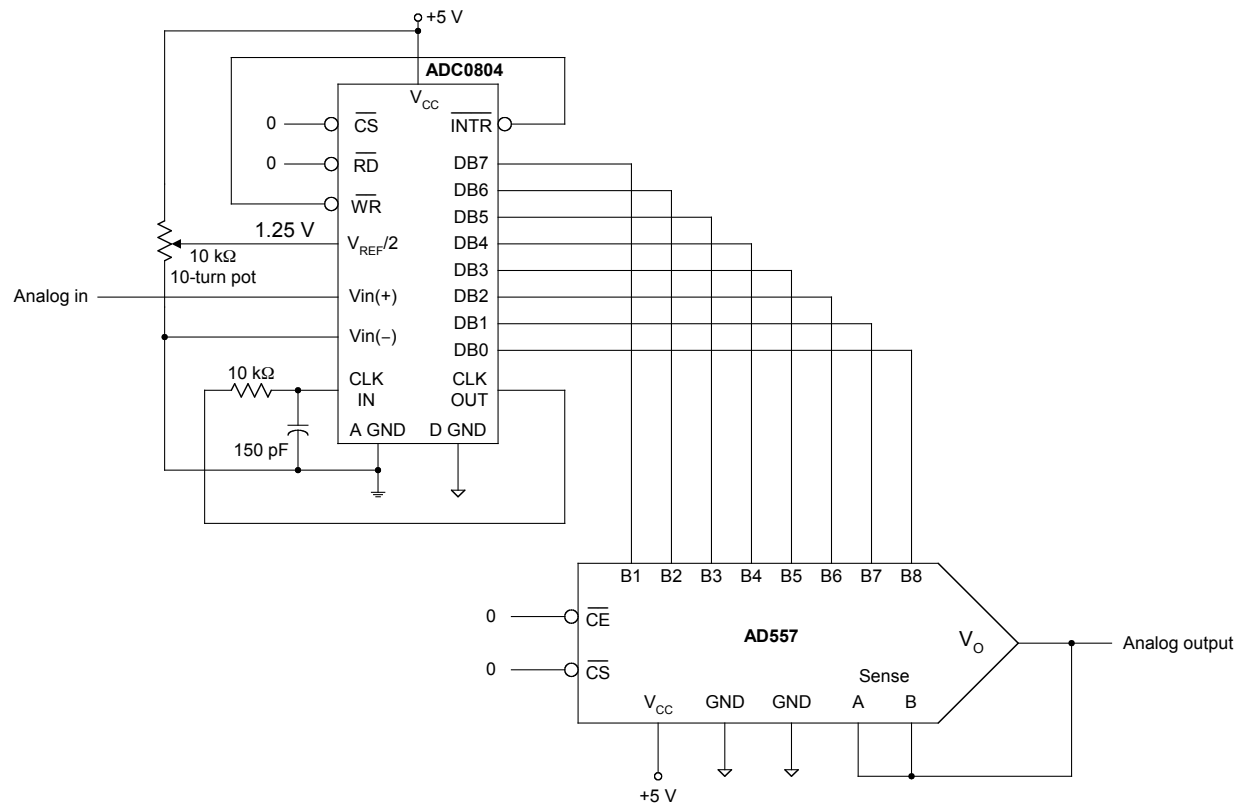
## 22.6 Reconstructing a digitized signal



$$V_{REF} = 2.5 \text{ V} \rightarrow V_{REF}/2 = 1.25 \text{ V}$$


Analog-out should approximate the analog-in voltage

Analog-out will be ragged with stairstep output

At higher frequencies, analog in will overrun conversion time of A/D converter (aliasing)


## Unit 23 Memory Systems

### 23.1 RAM memory chip

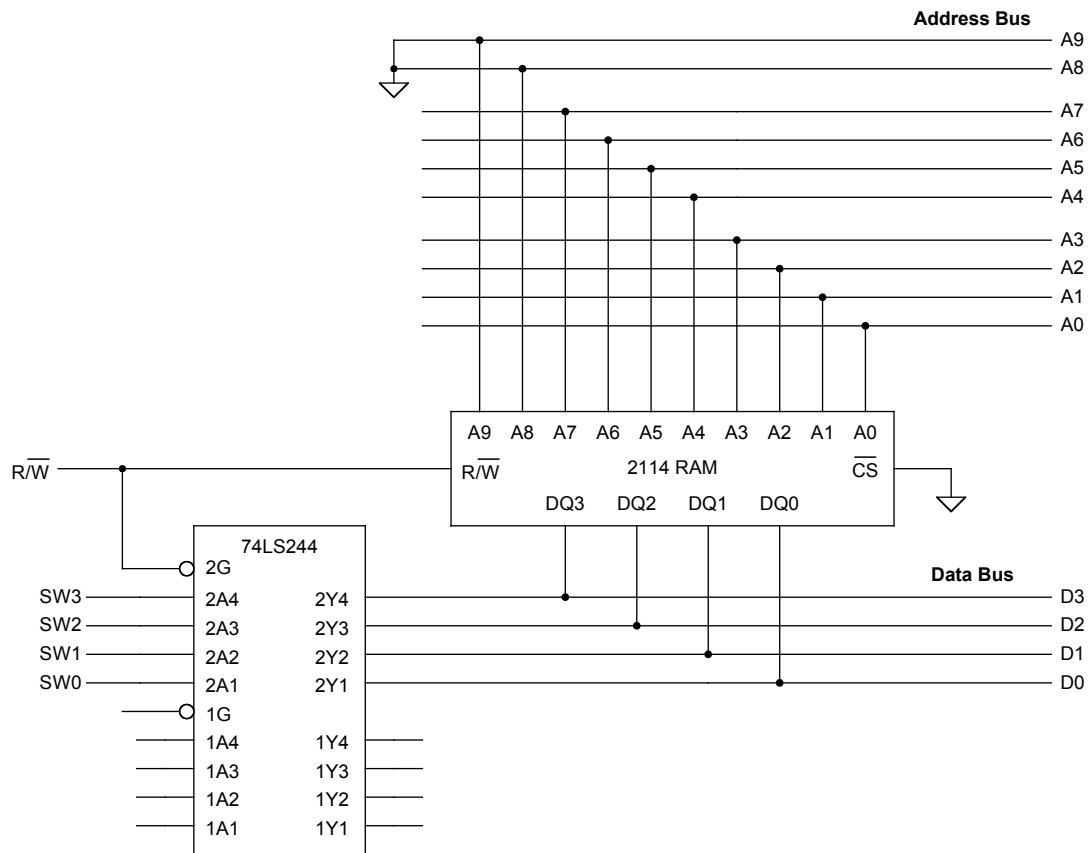




## 23.2 Memory word-size expansion

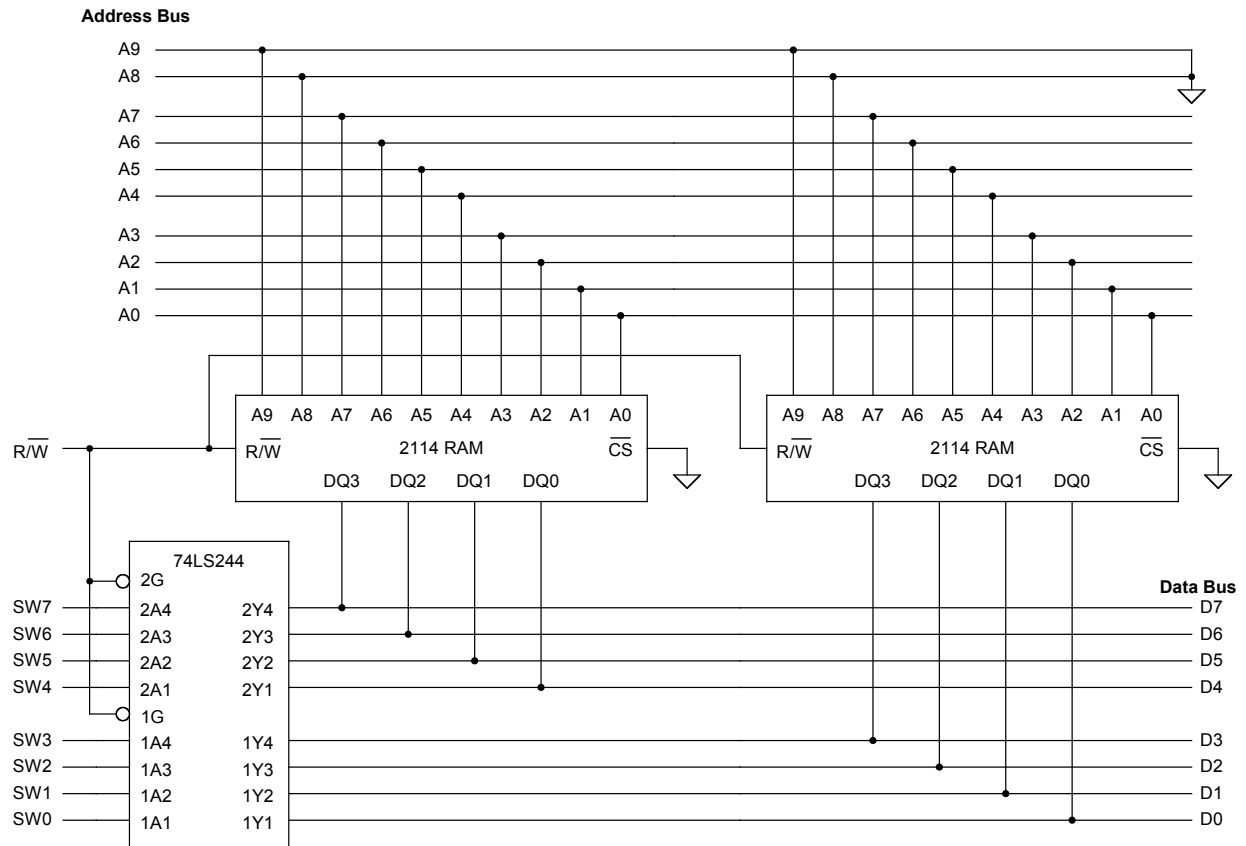

### 23.3 Memory capacity expansion

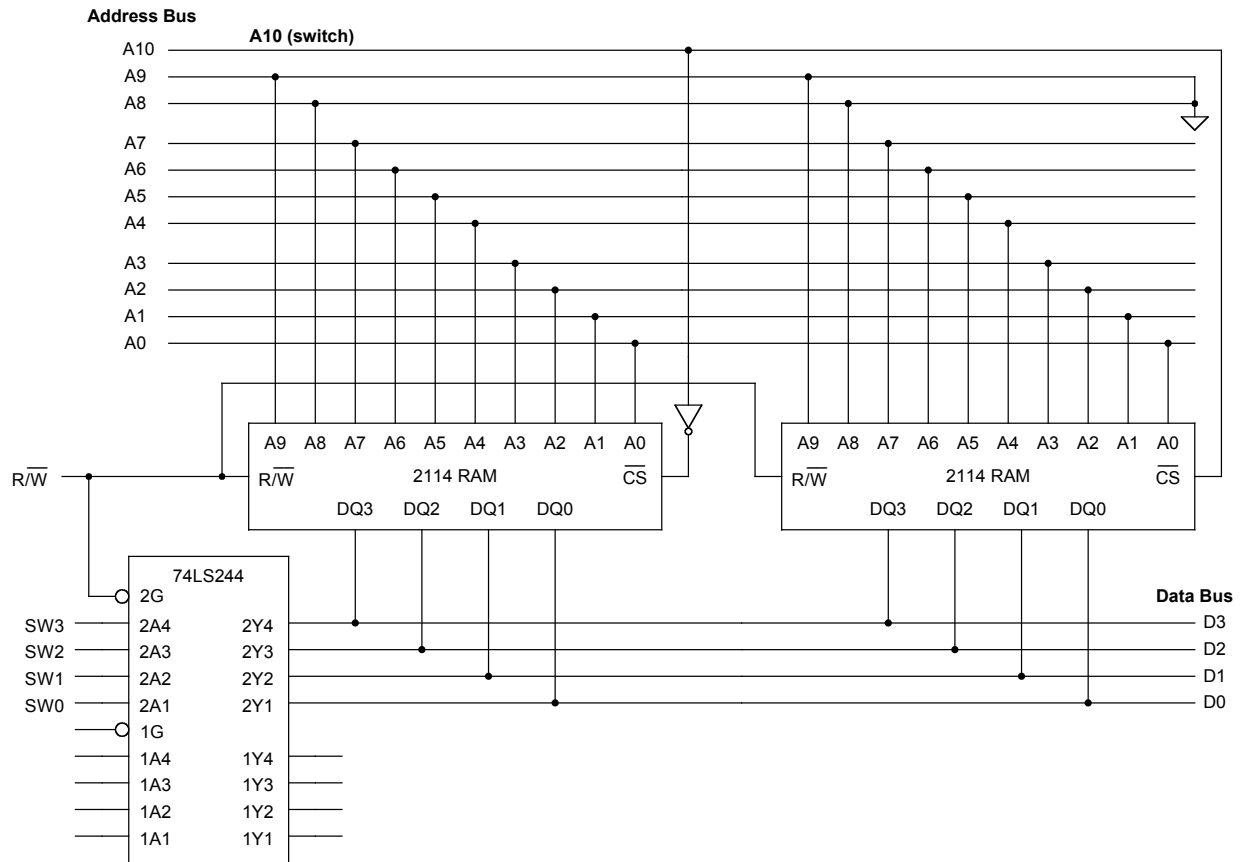


## 23.4 Memory address decoding

```
SUBDESIGN mem2k_decode
(
    a[15..0]      :INPUT;
    cs[1..0]      :OUTPUT;
)
BEGIN
    IF      a[] >= H"1800" AND a[] <= H"1BFF"      THEN
        cs[] = B"10";
    ELSIF a[] >= H"6800" AND a[] <= H"6BFF"      THEN
        cs[] = B"01";
    ELSE
        cs[] = B"11";
    END IF;
END;
```


```
ENTITY mem2k_decode IS
PORT (
    a      :IN INTEGER RANGE 0 TO 65535;
    cs     :OUT BIT_VECTOR (1 DOWNTO 0)
);
END mem2k_decode;

ARCHITECTURE memory_decoder OF mem2k_decode IS
BEGIN
    PROCESS (a)
    BEGIN
        IF      a >= 16#1800# AND a <= 16#1BFF# THEN
            cs <= "10";
        ELSIF a >= 16#6800# AND a <= 16#6BFF# THEN
            cs <= "01";
        ELSE
            cs <= "11";
        END IF;
    END PROCESS;
END memory_decoder;
```

Maxplus2 or MSI chip solution:

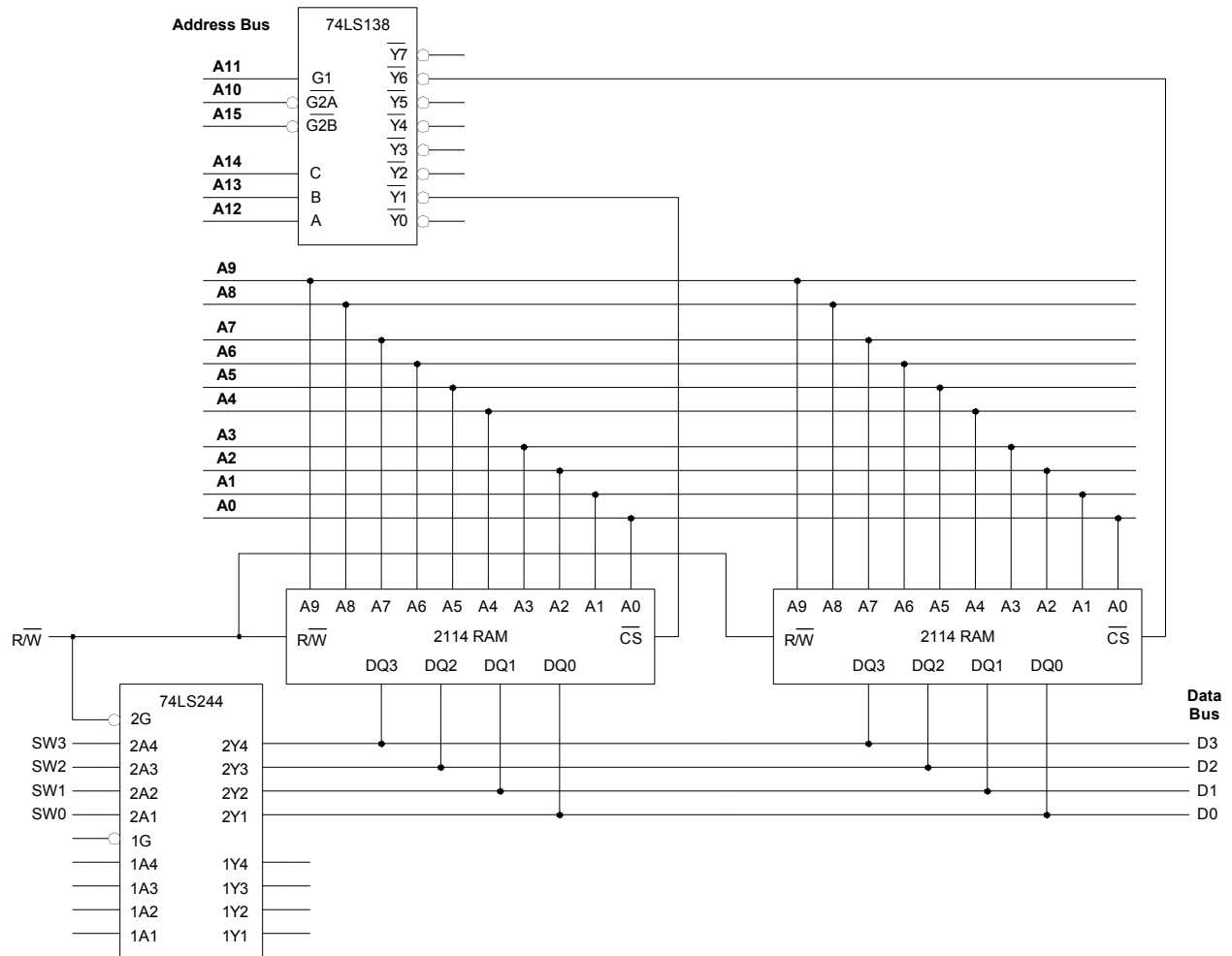
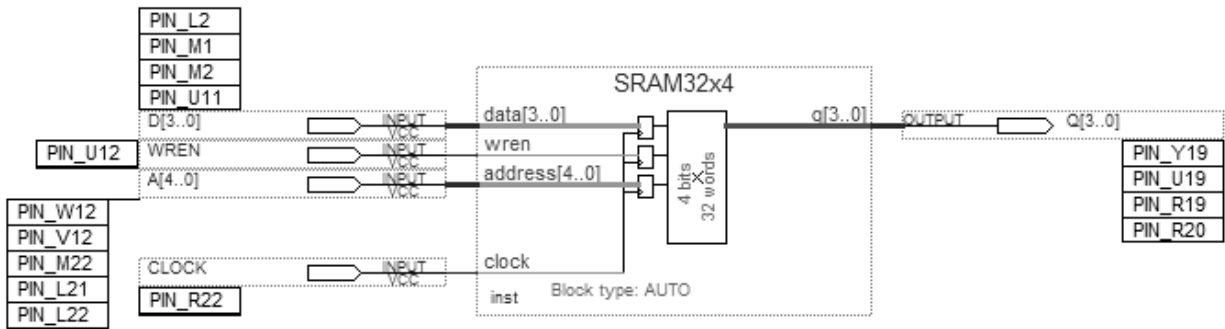
### 23.5 Embedded SRAM memory (DE1 pin assignments shown)



### 23.6 DE1/DE2 SRAM memory chip (DE1 pin assignments shown)

