

Section 2-10 How Can We Check...?

P 2.10-1 The circuit shown in Figure P 2.10-1 is used to test the CCVS. Your lab partner claims that this measurement shows that the gain of the CCVS is -20 V/A instead of $+20 \text{ V/A}$. Do you agree? Justify your answer.

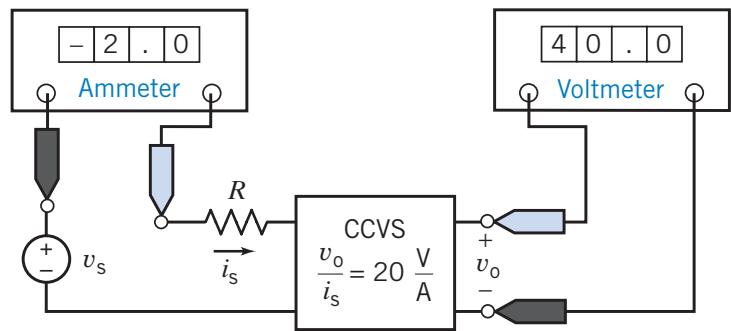


Figure P 2.10-1

Solution:

$v_o = 40 \text{ V}$ and $i_s = -(-2) = 2 \text{ A}$. (Notice that the ammeter measures $-i_s$ rather than i_s .)

$$\text{So } \frac{v_o}{i_s} = \frac{40}{2} = 20 \frac{\text{V}}{\text{A}}$$

Your lab partner is wrong.

P 2.10-2 The circuit of Figure P 2.10-2 is used to measure the current in the resistor. Once this current is known, the resistance can be calculated as $R = \frac{v_s}{i}$. The circuit is constructed using a voltage source with $v_s = 12 \text{ V}$ and a $25\text{-}\Omega$, $1/2\text{-W}$ resistor. After a puff of smoke and an unpleasant smell, the ammeter indicates that $i = 0 \text{ A}$. The resistor must be bad. You have more $25\text{-}\Omega$, $1/2\text{-W}$ resistors. Should you try another resistor? Justify your answer.

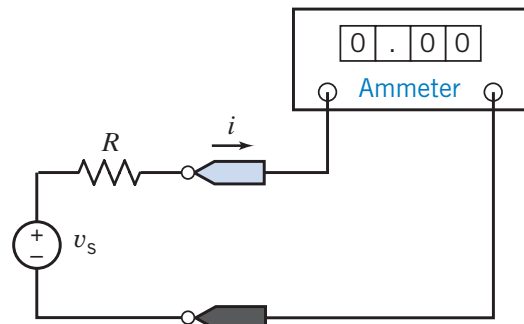


Figure P 2.10-2

Hint: $1/2\text{-W}$ resistors are able to safely dissipate one $1/2 \text{ W}$ of power. These resistors may fail if required to dissipate more than $1/2 \text{ watt}$ of power.

Solution:

We expect the resistor current to be $i = \frac{v_s}{R} = \frac{12}{25} = 0.48 \text{ A}$. The power absorbed by this resistor will be $P = i v_s = (0.48)(12) = 5.76 \text{ W}$.

A half watt resistor can't absorb this much power. You should not try another resistor.