

Solutions Manual for
RF Microelectronics

Second Edition

Behzad Razavi



Upper Saddle River, NJ • Boston • Indianapolis • San Francisco
New York • Toronto • Montreal • London • Munich • Paris • Madrid
Capetown • Sydney • Tokyo • Singapore • Mexico City

The author and publisher have taken care in the preparation of this book, but make no expressed or implied warranty of any kind and assume no responsibility for errors or omissions. No liability is assumed for incidental or consequential damages in connection with or arising out of the use of the information or programs contained herein.

Visit us on the Web: informIT.com/ph

Copyright © 2012 Pearson Education, Inc.

This work is protected by United States copyright laws and is provided solely for the use of instructors in teaching their courses and assessing student learning. Dissemination or sale of any part of this work (including on the World Wide Web) will destroy the integrity of the work and is not permitted. The work and materials from it should never be made available to students except by instructors using the accompanying text in their classes. All recipients of this work are expected to abide by these restrictions and to honor the intended pedagogical purposes and the needs of other instructors who rely on these materials.

ISBN-13: 978-0-13-285738-3

ISBN-10: 0-13-285738-3


RF Microelectronics, Second Edition

Errata


Behzad Razavi

- Prob. 2.3, second line should read: consider the cascade of identical ...
- Fig. 3.10 should be changed as shown below:


AM

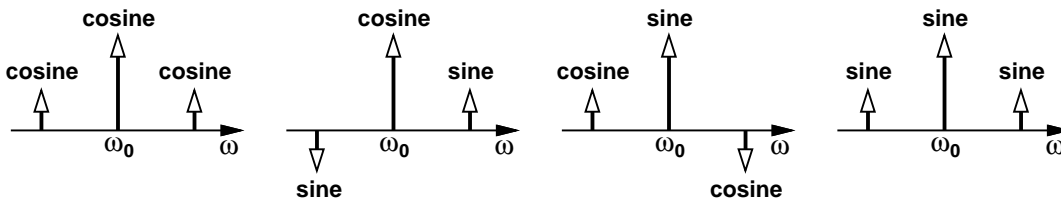

NBFM

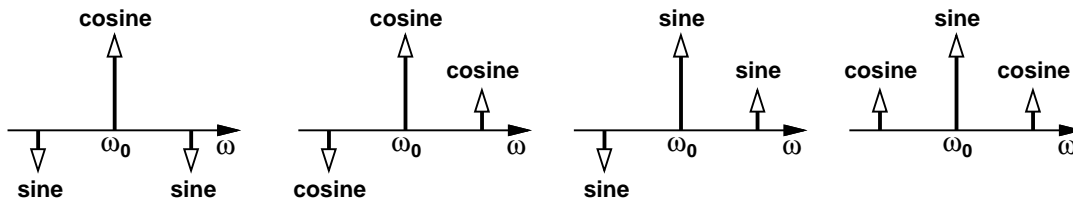

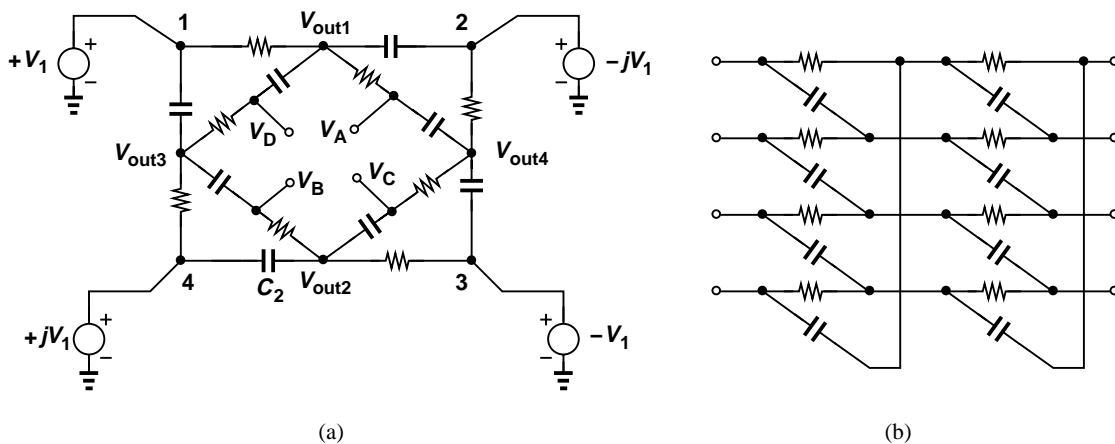- Fig. 4.81(a) should be changed as shown below:




- Example 4.36, the first sentence in solution should read: We have $V_{out1} = (1/2)(1 - j)V_1$ and ...
- Example 5.5, third line in solution: Since it is desired that $R_{in} = R_S$,

- Example 6.21, last three lines of solution: Note that $V_{n2}(f)$ is typically very large because M_2 and M_3 are relatively small.
- Example 7.6, Eq. (7.33) should read:


$$C_{eq} = \frac{C_1 + \dots + C_{4(N-1)}}{[4(N-1)]^2} \quad (1)$$

Eq. (7.125) in Problem 7.3 must also be corrected as above.


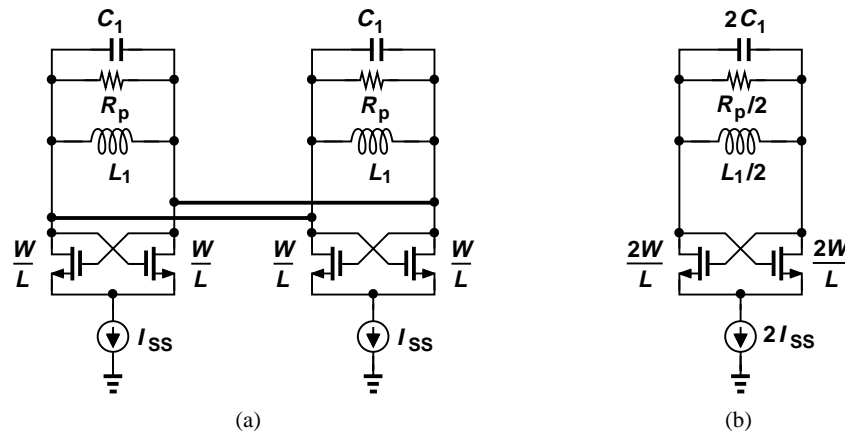
- p. 488, the sentence below Eq. (7.114) should read $Z_{1d} = R_{tot}/2$ and $Y_{1d} = C_{tot}s/2$.
- Prob. 7.10, Assume the inductance is about 9 times that of one spiral.
- Fig. 8.84 (b) should be changed as follows:



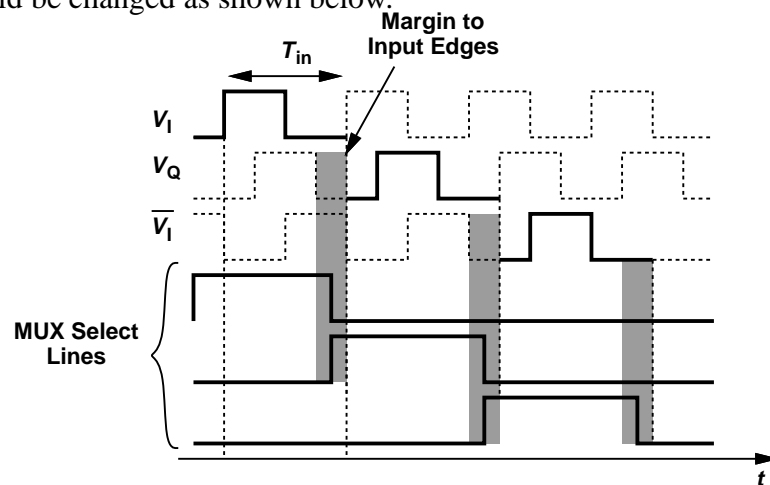- Fig. 11.45 should be changed as shown below.



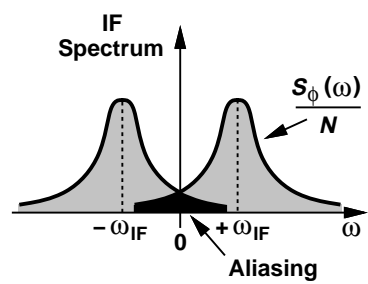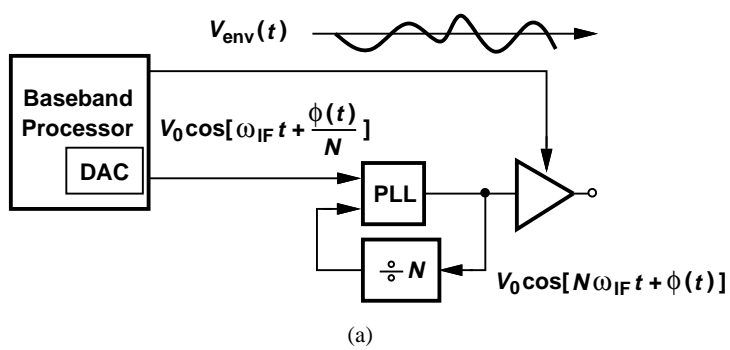
- Fig. 12.53(b) should be changed as shown below.



(a)

(b)

2-1 Solu:

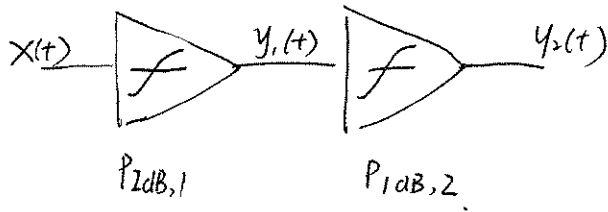

$$y_1(t) = \alpha_1 x(t) + \alpha_2 x^2(t) + \alpha_3 x^3(t)$$

$$y_2(t) = \beta_1 y_1(t) + \beta_2 y_1^2(t) + \beta_3 y_1^3(t)$$

then.

$$y_2(t) = \beta_1 [\alpha_1 x(t) + \alpha_2 x^2(t) + \alpha_3 x^3(t)] + \beta_2 [\alpha_1 x(t) + \alpha_2 x^2(t) + \alpha_3 x^3(t)]^2 + \beta_3 [\alpha_1 x(t) + \alpha_2 x^2(t) + \alpha_3 x^3(t)]^3$$

Considering only the first - and third - order terms,

$$y_2(t) = \alpha_1 \beta_1 x(t) + (\alpha_3 \beta_1 + 2\alpha_1 \alpha_2 \beta_2 + \alpha_1^3 \beta_3) x^3(t) + \dots$$

$$= [\alpha_1 \beta_1 + \frac{3}{4} (\alpha_3 \beta_1 + 2\alpha_1 \alpha_2 \beta_2 + \alpha_1^3 \beta_3) A_{in,1dB}^2] x(t) + \dots$$

$$P_{1dB,1} : A_{in,1dB} = \sqrt{0.145 \left| \frac{\alpha_1}{\alpha_3} \right|} ; P_{1dB,2} : A_{in,2,1dB} = \sqrt{0.145 \left| \frac{\beta_1}{\beta_3} \right|}$$

$$P_{1dB} \Rightarrow 20 \log \left| \alpha_1 \beta_1 + \frac{3}{4} (\alpha_3 \beta_1 + 2\alpha_1 \alpha_2 \beta_2 + \alpha_1^3 \beta_3) A_{in,1dB}^2 \right| = 20 \log |\alpha_1 \beta_1| - 1dB$$

$$A_{in,1dB} = \sqrt{0.145 \left| \frac{\alpha_1 \beta_1}{\alpha_3 \beta_1 + 2\alpha_1 \alpha_2 \beta_2 + \alpha_1^3 \beta_3} \right|}$$

Represented by the P_{1dB} of first and second stage.

$$\frac{1}{A_{in,1dB}^2} = \frac{1}{0.145} \left| \frac{\alpha_3}{\alpha_1} + \frac{2\alpha_2 \beta_2}{\beta_1} + \frac{\alpha_1^2 \beta_3}{\beta_1} \right|$$

$$= \left| \frac{1}{A_{in,1dB}^2} + \frac{2}{0.145} \frac{\alpha_2 \beta_2}{\beta_1} + \frac{\alpha_1^2}{A_{in,2,1dB}^2} \right|$$

2.2 solve:

assuming -3 dBm A_1 at 2.42 GHz
 -35 dBm A_2 at 2.43 GHz .

$$\text{IM product} : \frac{3}{4} \delta_3 A_1^2 A_2$$

$$-3 \text{ dBm} \Rightarrow A_1 = \sqrt{2.50 \cdot 10^{-0.3} \times 10^{-3}} = 223.9 \text{ mV}$$

$$-35 \text{ dBm} \Rightarrow A_2 = \sqrt{2.50 \times 10^{-3.5} \times 10^{-3}} = 5.6 \text{ mV}$$


We can write at LNA output:

$$20 \lg |\delta_1 \cdot A_{\text{sig}}| - 20 \text{ dB} = 20 \lg \left| \frac{3}{4} \delta_3 A_1^2 A_2 \right|$$

$$\Rightarrow \lg |\delta_1 \cdot A_{\text{sig}}| = \lg \left| \frac{30}{4} \delta_3 A_1^2 A_2 \right|$$

$$\text{IIP}_3 = \sqrt{\frac{4}{3} \left| \frac{\delta_1}{\delta_3} \right|} = \sqrt{\frac{4}{3} \cdot \frac{30}{4} \cdot \frac{A_1^2 \cdot A_2}{A_{\text{sig}}}} = 9.43 \text{ Vp}$$
$$= 29.5 \text{ dBm}$$

f 2.3 solve:

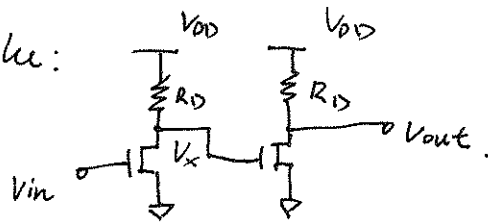

$$I_D = K \cdot (V_{GS} - V_T)^2$$

$$V_{out} = V_{DD} - K \cdot R_D (V_x - V_T)^2$$

$$V_x = V_{DD} - K \cdot R_D (V_{in} - V_T)^2$$

$$V_{out} = V_{DD} - K \cdot R_D [V_{DD} - K \cdot R_D (V_{in} - V_T)^2 - V_T]^2$$

$$= V_{DD} - K \cdot R_D [(V_{DD} - V_T) - K \cdot R_D (V_{in} - V_T)^2]^2$$

$$= V_{DD} - K \cdot R_D [(V_{DD} - V_T)^2 + K^2 R_D^2 (V_{in} - V_T)^4 - 2 K R_D (V_{DD} - V_T) (V_{in} - V_T)^2]$$

1st order of V_{in}

$$\Rightarrow [4 \cdot (V_{DD} - V_T) \cdot K \cdot R_D V_T - 4 K^2 R_D^2 \cdot V_T^3] \cdot V_{in}$$

3rd order of V_{in}

$$\Rightarrow [-4 K^2 R_D^2 V_T] \cdot V_{in}^3$$

$$A_{IP3} = \sqrt{\frac{4}{3} \cdot \frac{4 \cdot (V_{DD} - V_T) K \cdot R_D V_T - 4 K^2 R_D^2 V_T^3}{4 K^2 R_D^2 V_T}}$$

2.4. Solu.

$$y(t) = \partial_1 X(t) + \partial_2 X^2(t) + \partial_3 X^3(t) + \partial_4 X^4(t) + \partial_5 X^5(t)$$

$$1^\circ \cos^3 \omega t = \frac{3}{4} \cos \omega t + \frac{1}{4} \cos 3\omega t$$

$$2^\circ \cos^2 \omega t = \frac{1 + \cos 2\omega t}{2}$$

$$3^\circ \cos^4 \omega t = \frac{1 + \cos^2 2\omega t + 2\cos 2\omega t}{2^2}$$

$$4^\circ \cos^5 \omega t = \left(\frac{3}{4} \cos \omega t + \frac{1}{4} \cos 3\omega t \right) \cdot \left(\frac{1 + \cos 2\omega t}{2} \right)$$

$$= \left(\frac{3}{8} \cos \omega t + \frac{1}{8} \cos 3\omega t + \frac{3}{8} \cos \omega t \cdot \cos 2\omega t \right)$$

$$\parallel \quad \parallel \quad \parallel$$

$$+ \frac{1}{8} \cos 3\omega t \cdot \cos 2\omega t$$

$$\frac{3}{16} [\cos \omega t + \cos 3\omega t] \quad \parallel$$

$$\frac{1}{16} [\cos \omega t + \cos 5\omega t]$$

1st order $\Rightarrow \partial_1 A + \frac{3}{4} \partial_3 A^3 + \left(\frac{3}{8} + \frac{3}{16} + \frac{1}{16} \right) \partial_5 A^5$

3rd order $\Rightarrow \frac{1}{4} \partial_3 A^3 + \left(\frac{1}{8} + \frac{3}{16} \right) \partial_5 A^5$

(1) P1dB $\Rightarrow 20 \lg |\partial_1 + \frac{3}{4} \partial_3 A^2 + \frac{5}{8} \partial_5 A^4| = 20 \lg |\partial_1| - 1 \text{ dB}$

$$\Rightarrow A_{in, 1 \text{ dB}} = \sqrt{\frac{0.8 \cdot (0.5625 \partial_3^2 - 0.27175 \partial_1 \cdot \partial_5) \pm 0.6 \partial_3}{\partial_5}}$$

(2) IIP3 doesn't change.

$$A_{IIP3} = \sqrt{\frac{4}{3} \left| \frac{\partial_1}{\partial_3} \right|}$$

2.5(a) Solu: $A_{sig} = \frac{0.1mV}{\times 0.7943} \Leftarrow -2dB = 10^{-0.1} = 0.7943$

$A_2 = 10mV \times 0.1413 \Leftarrow -17dB = 10^{-0.85} = 0.1413$

$A_3 = 10mV \times 0.0141 \Leftarrow -37dB = 10^{-1.85} = 0.0141$

at the output of amplifier:

$$20 \lg |\sigma_1 \cdot A_{sig}| - 20dB = 20 \lg \left| \frac{3}{4} \sigma_3 \cdot A_2^3 \cdot A_3 \right|$$

$$\Rightarrow |\sigma_1 \cdot 0.07943m| = \left| \frac{3}{4} \sigma_3 \cdot 1.413m^2 \cdot 0.141m \right|$$

$$\therefore A_{IIP3} = \sqrt{\frac{\frac{3}{4} \cdot 1.413m^2 \cdot 0.141}{0.07943} \cdot \frac{4}{3}} = 5.95mV_p = -34.5dBm$$

Neglect the nonlinearity of BPF.

(b). $y_1(t) = \sigma_1 x(t) + \sigma_3 x^3(t)$

$y_2(t) = \beta_1 y_1(t) + \beta_2 y_1^3(t)$

Only considering the first and third order:

$$y_2(t) = \sigma_1 \beta_1 x(t) + (\sigma_3 \beta_1 + \sigma_1^3 \beta_3) x^3(t) + \dots$$

$$\therefore A_{zP3} = \sqrt{\frac{\frac{4}{3} \left| \frac{\sigma_1 \beta_1}{\sigma_3 \beta_1 + \sigma_1^3 \beta_3} \right|}{}}$$

$$\frac{1}{A_{zP3}^2} = \frac{1}{A_{zP3,1}^2} + \frac{\sigma_1^2}{A_{zP3,2}^2}$$

$$\Rightarrow \frac{1}{A_{zP3}^2} = \frac{1}{500m^2} + \frac{10}{5.95m^2}$$

$$\Rightarrow A_{zP3} = 1.875mV_p$$

2.6 Solu:

Let $x(t)$ be a random signal (wide-sense stationary process)

Auto correlation function: $R_x(\tau) = E[x(t) \cdot x(t+\tau)]$

Let me prove that: $S_x(f) = \int_{-\infty}^{\infty} R_x(\tau) e^{-j2\pi f\tau} d\tau$

$$\text{Proof: } X_T(f) \triangleq \int_{-T/2}^{T/2} x(t) e^{-j2\pi ft} dt$$

$$S_T(f) \triangleq E\left[\frac{1}{T} |X_T(f)|^2\right]$$

$$S_x(f) = \lim_{T \rightarrow \infty} S_T(f)$$

$$E[|X_T(f)|^2] = E\left[\int_{-T/2}^{T/2} x(t) e^{-j2\pi ft} dt\right]^2$$

$$= E\left[\int_{-T/2}^{T/2} x(t) e^{-j2\pi ft} dt \cdot \int_{-T/2}^{T/2} x(\tau) e^{-j2\pi f\tau} d\tau\right]$$

$$= E\left[\int_{-T/2}^{T/2} \int_{-T/2}^{T/2} x(t)x(\tau) e^{-j2\pi f(t-\tau)} dt d\tau\right]$$

$$= \int_{-T/2}^{T/2} \int_{-T/2}^{T/2} E[x(t)x(\tau)] e^{-j2\pi f(t-\tau)} dt d\tau$$

$$= \int_{-T/2}^{T/2} \int_{-T/2}^{T/2} R_x(t-\tau) e^{-j2\pi f(t-\tau)} dt d\tau$$

$$= \int_{-T}^T (T-|\tau|) R_x(\tau) e^{-j2\pi f\tau} d\tau$$

$$E\left[\frac{1}{T} |X_T(f)|^2\right] = \int_{-T}^T \left(1 - \frac{|\tau|}{T}\right) R_x(\tau) e^{-j2\pi f\tau} d\tau$$

Therefore: $S_x(f) = \lim_{T \rightarrow \infty} E\left[\frac{1}{T} |X_T(f)|^2\right] = \int_{-\infty}^{\infty} R_x(\tau) e^{-j2\pi f\tau} d\tau$

2.7. Solu:

$$\text{Assume } y(t) = \delta_1 x(t) + \delta_2 x^2(t) + \delta_3 x^3(t).$$

$$x(t) = V_0 \cos \omega_0 t.$$

$$\text{3rd - harmonic : } \frac{\delta_3 V_0^3}{4} = V_3$$


$$\Rightarrow \delta_3 = \frac{4V_3}{V_0^3}$$

$$A_{in, 1dB} = \sqrt{0.145 \left| \frac{\delta_1}{\delta_3} \right|}$$

$$= \sqrt{0.145 \cdot \left| \frac{\delta_1}{4V_3/V_0^3} \right|}$$

$$= \sqrt{\frac{0.145}{4} \left| \frac{\delta_1 V_0^3}{V_3} \right|}$$

12.8 soln:

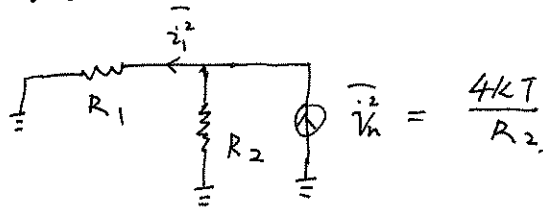

$$\begin{aligned} P_{R_1} &= i_1^2 \cdot R_1 \\ &= \left(\sqrt{\frac{4kT}{R_2}} \cdot \frac{R_2}{R_1 + R_2} \right)^2 \cdot R_1 \\ &= \frac{4kT}{(R_1 + R_2)^2} \cdot R_1 R_2 \end{aligned}$$


$$\therefore P_{R_1} = P_{R_2}$$

So it proves that the noise power delivered by R_1 to R_2 is equal to that delivered by R_2 to R_2 at the same temperature.

\therefore If it is not the truth, the energy would not be conserved.

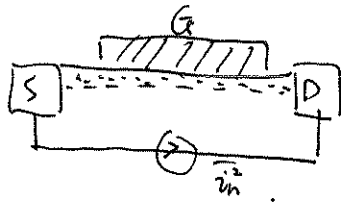2.9 Solu:

Why the channel thermal noise of a MOSFET is model by a current source bw. S & D, rather than G & D.



Firstly, from the figure we can find the channel resistor is between source & drain. As a result, it is reasonable to model the noise by a current source between source and drain.

Secondly, MOSFET has the function of transconductance. It's easy to transfer the current source from between S & D to the voltage source at the gate.

2.10 Solu:



Proof: transconductance : g_m .

Assume the transistor is in saturation region.

For small-signal analysis, $v_1 = 0$

$$I_D = \sqrt{\overline{i_n^2}} = \sqrt{4KT\gamma g_m}$$


At the same time, for voltage source model.

$$I_D = v_{in} \cdot g_m = \sqrt{4KT\gamma \cdot g_m}$$

$$\Rightarrow v_{in} = \sqrt{\frac{4KT\gamma}{g_m}}$$

$$\Rightarrow \overline{v_n^2} = \frac{4KT\gamma}{g_m}$$

2.11 Solu:

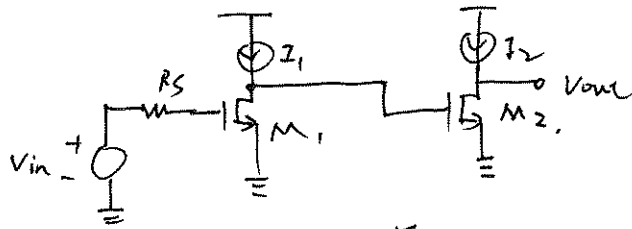

$$NF_1 = 1 + \frac{r}{g_{m1}R_S} \quad (2.122)$$


$$NF_2 = 1 + \frac{r}{g_{m2}r_{o1}} ; \quad A_{p1} = \frac{P_{out,av,1}}{P_{in,av,1}} = \frac{V_{in}^2 \cdot A_{v1}^2 \cdot \frac{1}{4r_{o1}}}{V_{in}^2 \cdot \frac{1}{4R_S}}$$

$$\therefore NF_{tot} = 1 + (NF_1 - 1) + \frac{NF_2 - 1}{A_{p1}} = g_{m1}^2 \cdot r_{o1} \cdot R_S$$

$$= 1 + \frac{r}{g_{m1}R_S} + \frac{r}{g_{m2} \cdot r_{o1}} \bigg/ g_{m1}^2 r_{o1} R_S$$


$$= 1 + \frac{r}{g_{m1}R_S} + \frac{r}{g_{m1}^2 r_{o1}^2 g_{m2} \cdot R_S}$$

2.12. Solu:

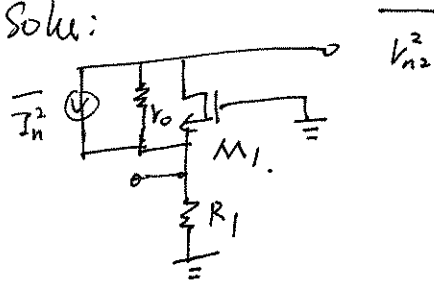

assume I_n is ideal, and neglect the noise of R_1 .

Proof:

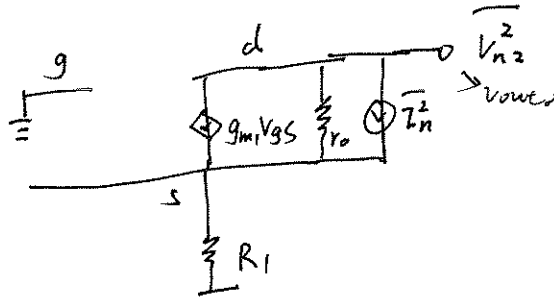

For small-signal analysis,

$$g_m(-v_s) + \frac{v_{out} - v_s}{r_o} + I_n = \frac{v_s}{R_1}$$

Because we cannot find any loop for the current through R_1 ,


$$v_s = 0$$

$$\Rightarrow \frac{v_{out}}{r_o} = -I_n$$

$$v_{out} = -I_n \cdot r_o$$

$$\therefore \overline{v_{n2}^2} = \overline{I_{n2}^2} \cdot r_o^2$$

2.13. Solu:

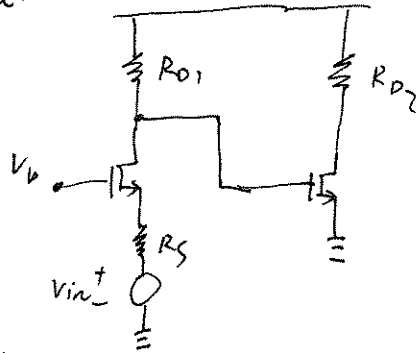

Neglect. transistor cap.
flicker noise.
CLM.
body effect.

For 1st stage:

$$R_{in1} = \frac{1}{g_{m1}}, \quad R_{h2} = \infty,$$

$$\overline{V_{n1}^2} = 4kTR_{D1} + \frac{4kT\gamma}{g_{m1}} \left(\frac{R_{D1}}{\frac{1}{g_{m1}} + R_S} \right)^2 \leftarrow \text{unloaded output noise.}$$

For 2nd stage:

$$\overline{V_{n2}^2} = 4kTR_{D2} + 4kT\gamma \cdot g_{m2} \cdot R_{D2}^2.$$


We now substitute these values in Eq. (2.126)

$$NF_{tot} = 1 + \frac{4kTR_{D1} + \frac{4kT\gamma}{g_{m1}} \left(\frac{R_{D1}}{\frac{1}{g_{m1}} + R_S} \right)^2}{\left(\frac{1}{\frac{1}{g_{m1}} + R_S} \right)^2 (g_{m1} \cdot R_{D1})^2} \cdot \frac{1}{4kTR_S} + \frac{4kTR_{D2} + 4kT\gamma \cdot g_{m2} \cdot R_{D2}^2}{\left(\frac{1}{\frac{1}{g_{m1}} + R_S} \right)^2 (g_{m1} \cdot R_{D1})^2 \cdot (g_{m2} \cdot R_{D2})^2} \cdot \frac{1}{4kTR_S}.$$

This result is different from the CS + CG configuration because, the first stage's NF and input impedance are different, which affect the NF_{tot}.

2.14. Solve:


Consider C.M.

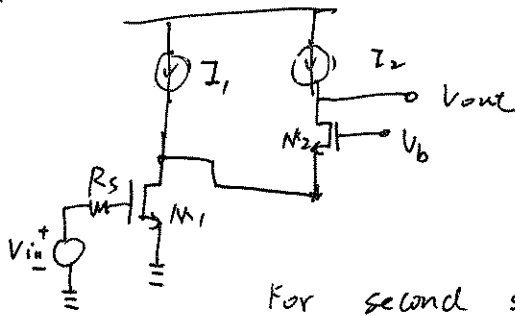

$$\overline{V_{n1}^2} = \frac{4KT\gamma}{g_{m1}} \cdot (g_{m1}r_{o1})^2$$

$$= 4KT\gamma \cdot g_{m1}r_{o1}^2$$

For second stage:

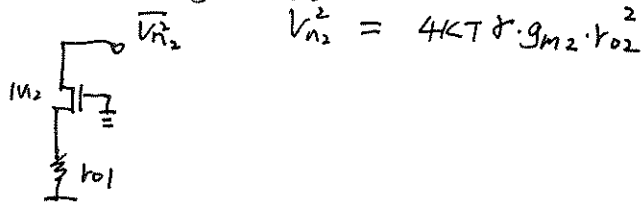


$$\overline{V_{n2}^2} = 4KT\gamma \cdot g_{m2} \cdot r_{o2}^2$$

We now substitute these values in Eq. (126).


$$NF_{tot} = 1 + \frac{4KT\gamma \cdot g_{m1}r_{o1}^2}{(g_{m1}r_{o1})^2} \cdot \frac{1}{4KTR_s}$$

$$+ \frac{4KT\gamma g_{m2}r_{o2}^2}{(g_{m1}r_{o1})^2 \cdot \left(\frac{1}{\frac{g_{m2}}{1} + r_{o1}}\right)^2 \cdot (g_{m2}r_{o2} + 1)^2} \cdot \frac{1}{4KTR_s}$$

Note:

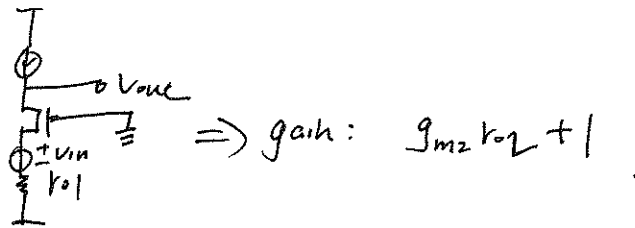

2.15 solve:

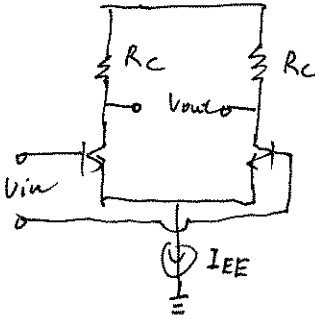

IP3.

$$\tanh x = x - \frac{x^3}{3} + \frac{2x^5}{15} - \dots$$

$$V_{out} = -2R_c I_{EE} \tanh \left[\frac{V_{in}}{2V_T} \right]$$

Only consider the first and third order.

$$V_{out} = -2R_c I_{EE} \left(\frac{V_{in}}{2V_T} - \frac{1}{3} \left(\frac{V_{in}}{2V_T} \right)^3 \right)$$

$$A_{in, IP3} = \sqrt{\frac{4}{3} \left| \frac{\partial^2}{\partial^3} \right|}$$

$$= \sqrt{\frac{4}{3} \cdot \frac{\frac{1}{2V_T}}{\frac{1}{3} \left(\frac{1}{2V_T} \right)^3}}$$

$$= 4V_T = 4 \frac{kT}{q} = 4 \times 26mV = 104mV$$